



دانشگاه سمنان

Semnan University  
Faculty of Mechanical Engineering

دانشکده مهندسی مکانیک



دانشکده مهندسی مکانیک


تمرین درس مبانی برق ۱

نام و شماره دانشجویی:


**INTRODUCTION TO ELECTRICAL  
ENGINEERING EXERCISES**

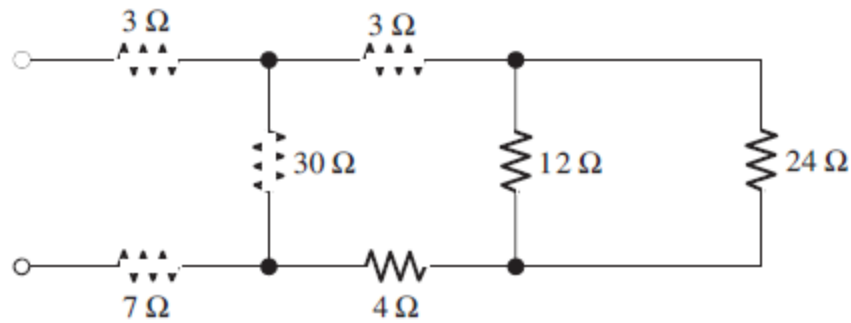**Chapter 2 – Resistive Circuits**

**\*P2.1.** Reduce each of the networks shown in Figure P2.1 to a single equivalent resistance by combining resistances in series and parallel.




(a)

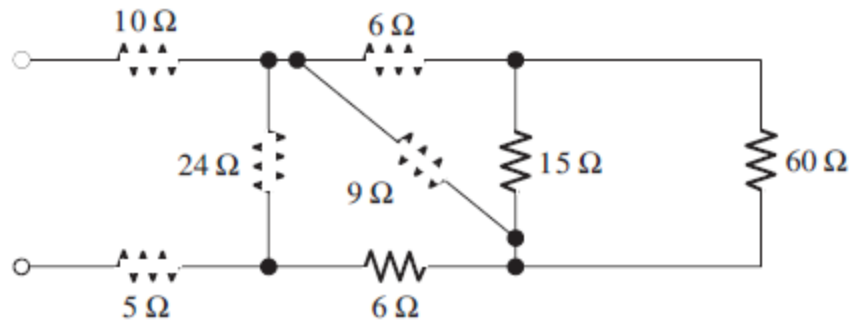


(b)

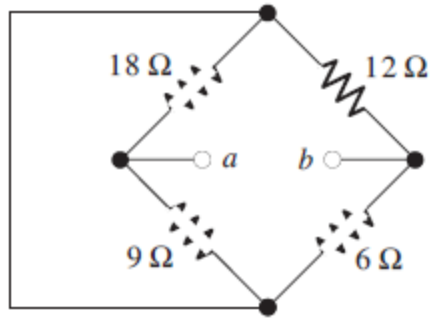
\*P2.3. Find the equivalent resistance looking into terminals  $a$  and  $b$  in Figure P2.3.



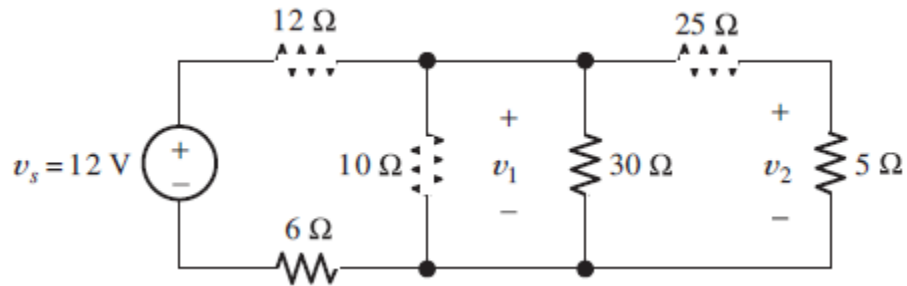
\*P2.24. Find the voltages  $v_1$  and  $v_2$  for the circuit shown in Figure P2.24 by combining resistances in series and parallel.



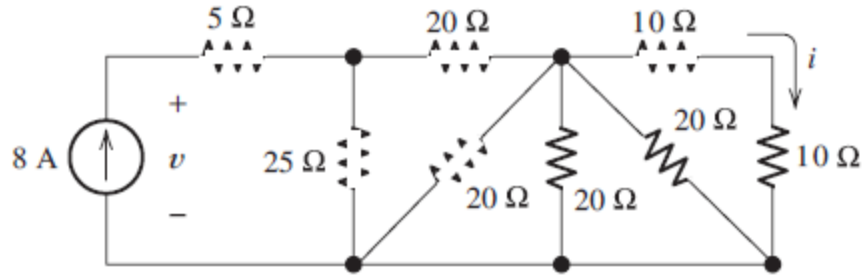
\*P2.25. Find the values of  $v$  and  $i$  in Figure P2.25.



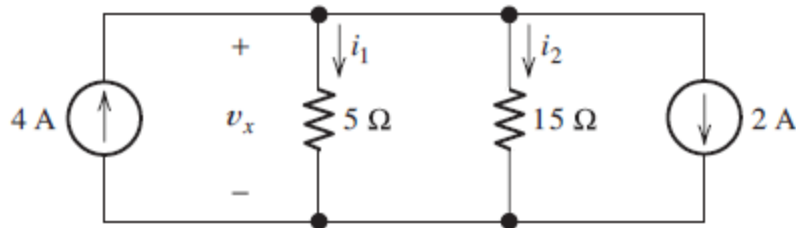
- \*P2.34.** Find the values of  $i_1$  and  $i_2$  in Figure P2.34. Find the power for each element in the circuit, and state whether each is absorbing or delivering energy. Verify that the total power absorbed equals the total power delivered.



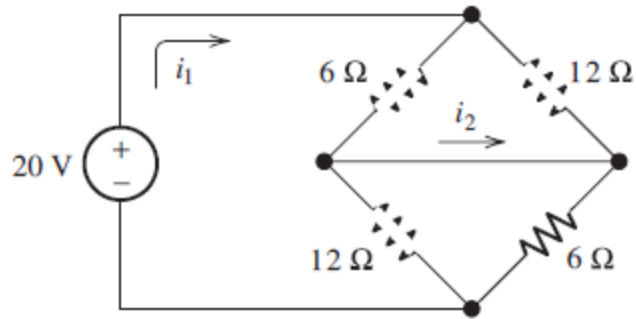\*P2.35. Find the values of  $i_1$  and  $i_2$  in Figure P2.35.




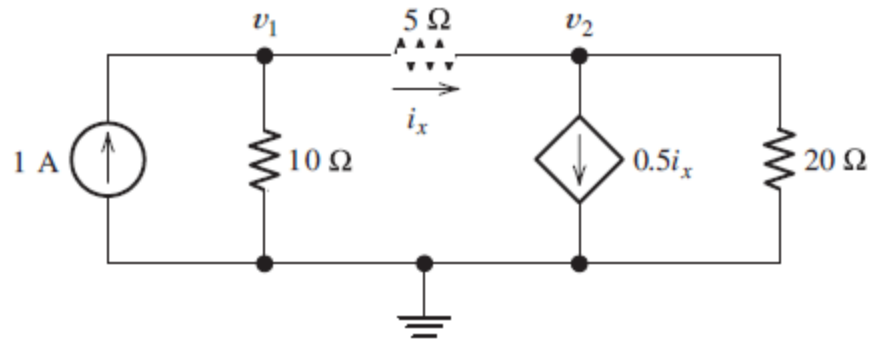\*P2.56. Solve for the values of the node voltages shown in Figure P2.56. Then, find the value of  $i_x$ .






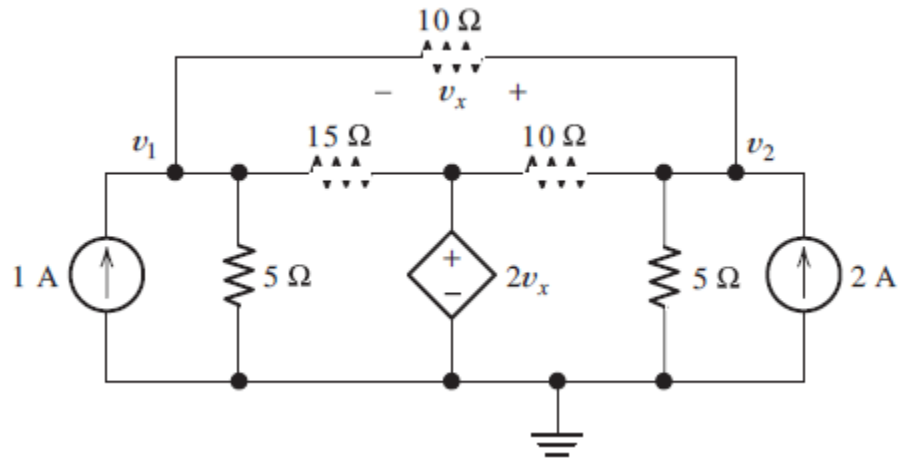\*P2.57. Solve for the node voltages shown in Figure P2.57.



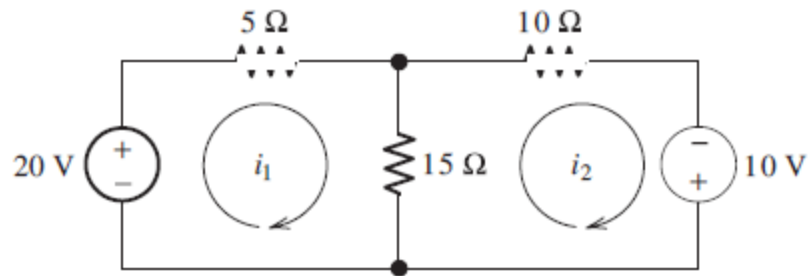\*P2.65. Solve for the power delivered to the  $15\text{-}\Omega$  resistor and for the mesh currents shown in Figure P2.65.



\*P2.66. Determine the value of  $v_2$  and the power delivered by the source in the circuit of Figure P2.24 by using mesh-current analysis.



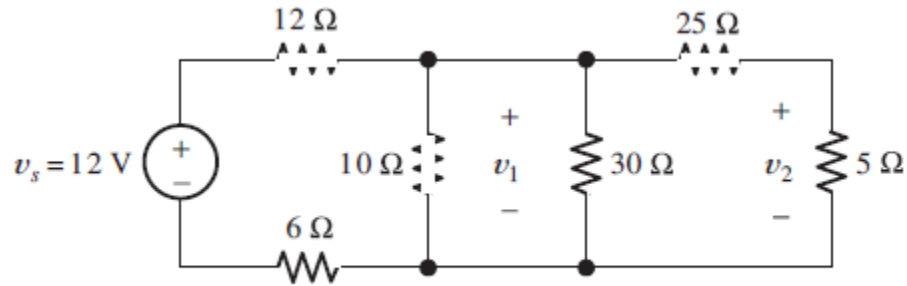


Figure P2.24

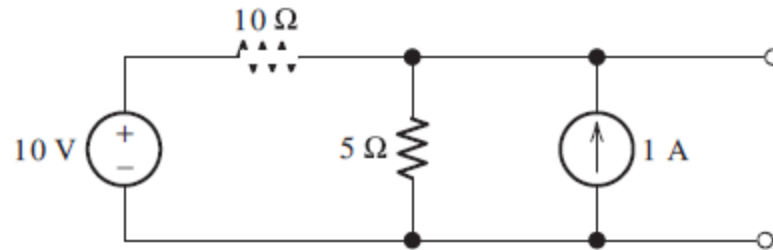
**\*P2.80.** Find the Thévenin and Norton equivalent circuits for the two-terminal circuit shown in Figure P2.80.



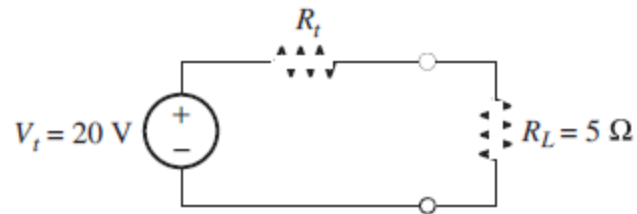
**\*P2.91.** Figure P2.91 shows a resistive load  $R_L$  connected to a Thévenin equivalent circuit. For what value of Thévenin resistance is the power delivered to the load maximized? Find the maximum power delivered to the load. (*Hint:* Be careful; this is a trick question if you don't stop to think about it.)



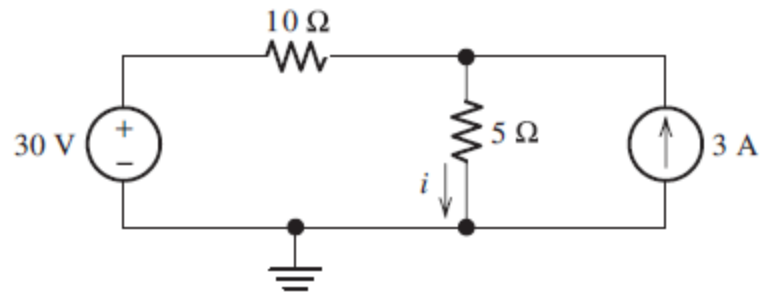**\*P2.94.** Use superposition to find the current  $i$  in Figure P2.94. First, zero the current source and find the value  $i_v$  caused by the voltage source alone. Then, zero the voltage source and find the value  $i_c$  caused by the current source alone. Finally, add the results algebraically.




**\*P2.103.** The Wheatstone bridge shown in Figure 2.64 has  $v_s = 10\text{ V}$ ,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 10\text{ k}\Omega$ , and  $R_x = 5932\ \Omega$ . The detector can be modeled as a  $5\text{-k}\Omega$  resistance. **a.** What value of  $R_3$  is required to balance the bridge? **b.** Suppose that  $R_3$  is  $1\ \Omega$  higher than the value found in part (a). Find the current through the detector. (*Hint:* Find the Thévenin equivalent for the circuit with the detector removed. Then, place the detector across the Thévenin equivalent and solve for the current.) Comment.

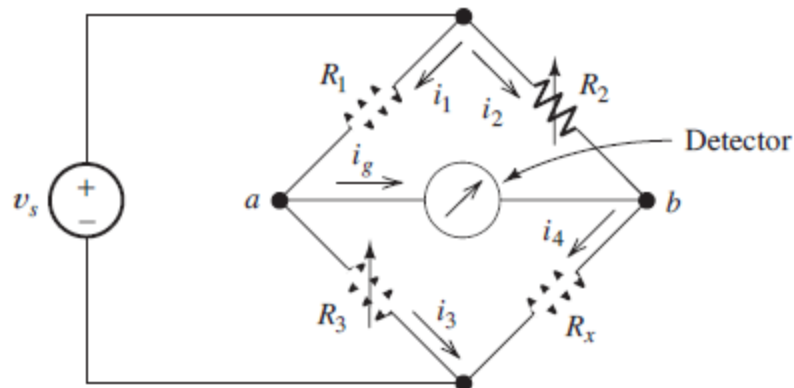


**Figure 2.64** The Wheatstone bridge. When the Wheatstone bridge is balanced,  $i_g = 0$  and  $v_{ab} = 0$ .

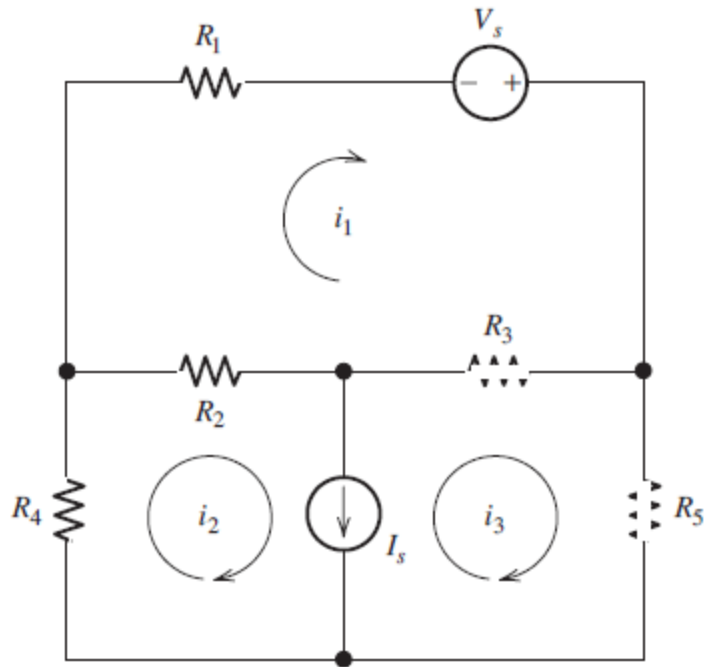**T2.4.** Write a set of equations that can be used to solve for the mesh currents of Figure T2.4. Be sure to indicate which of the equations you write form the set.





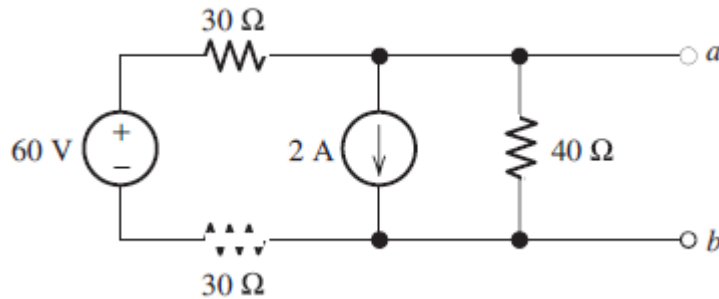**T2.5.** Determine the Thévenin and Norton equivalent circuits for the circuit of Figure T2.5. Draw the equivalent circuits labeling the terminals to correspond with the original circuit.



**T2.6.** According to the superposition principle, what percentage of the total current flowing through the  $5\text{-}\Omega$  resistance in the circuit of Figure T2.6 results from the  $5\text{-V}$  source? What percentage of the power supplied to the  $5\text{-}\Omega$  resistance is supplied by the  $5\text{-V}$  source? Assume that both sources are active when answering both questions.

