



دانشگاه سمنان

Semnan University  
Faculty of Mechanical Engineering

دانشکده مهندسی مکانیک



دانشکده مهندسی مکانیک

تمرین درس مبانی برق ۱

نام و شماره دانشجویی:


## INTRODUCTION TO ELECTRICAL ENGINEERING EXERCISES

Chapter 3 – Inductance and Capacitance



**\*P3.5.** A  $2000\text{-}\mu\text{F}$  capacitor, initially charged to  $100\text{ V}$ , is discharged by a steady current of  $100\ \mu\text{A}$ . How long does it take to discharge the capacitor to  $0\text{ V}$ ?



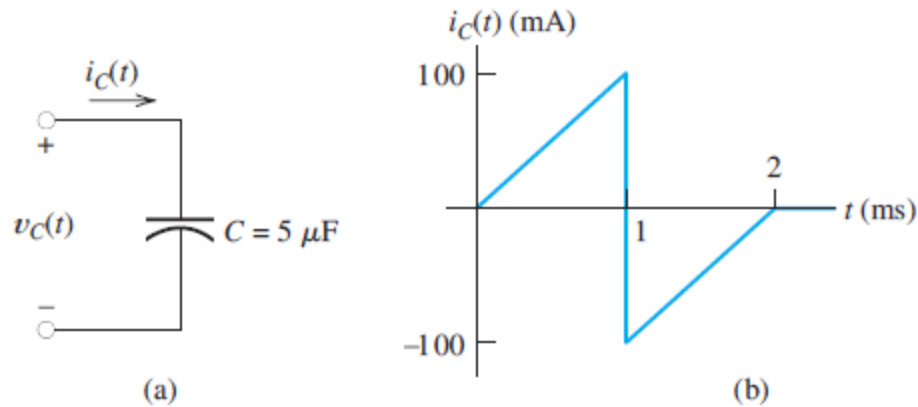**P3.16.** The current through a  $5\text{-}\mu\text{F}$  capacitor is shown in Figure P3.16. At  $t = 0$ , the voltage is  $v_C(0) = 0\text{ V}$ . Sketch the voltage, power, and stored energy to scale versus time.



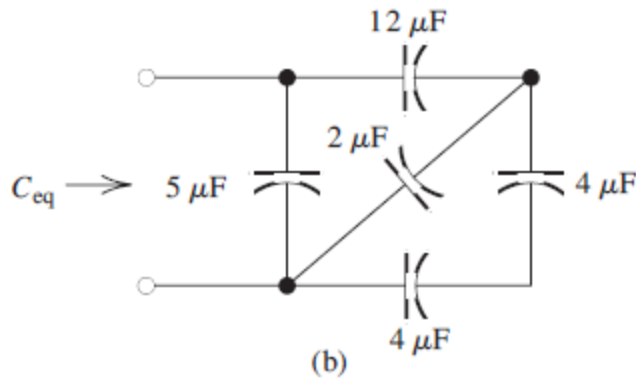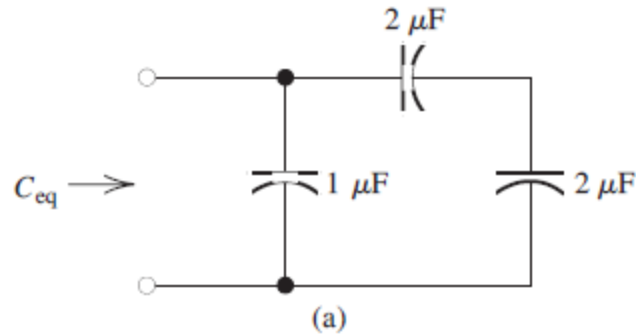
\*P3.24. Find the equivalent capacitance for each of the circuits shown in Figure P3.24.




**\*P3.32.** Suppose that we have a 1000-pF parallel-plate capacitor with air dielectric charged to 1000 V. The capacitor terminals are open circuited. Find the stored energy. If the plates are moved farther apart so that  $d$  is doubled, determine the new voltage on the capacitor and the new stored energy. Where did the extra energy come from?



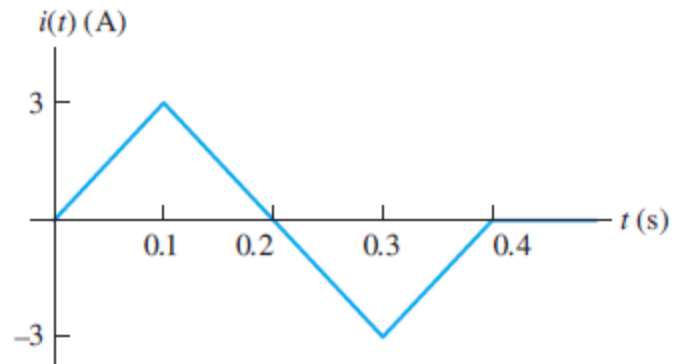**\*P3.43.** The current flowing through a 2-H inductance is shown in Figure P3.43. Sketch the voltage, power, and stored energy versus time.



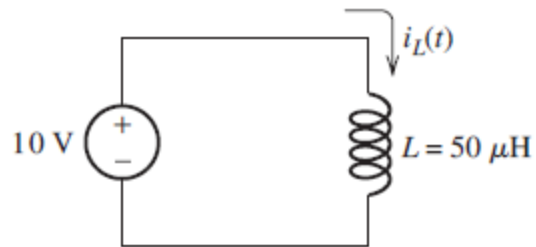**\*P3.44.** A constant voltage of 10 V is applied to a 50- $\mu\text{H}$  inductance, as shown in Figure P3.44. The current in the inductance at  $t = 0$  is  $-100$  mA. At what time  $t_x$  does the current reach  $+100$  mA?





**\*P3.45.** At  $t = 0$ , the current flowing in a 0.5-H inductance is 4 A. What constant voltage must be applied to reduce the current to 0 at  $t = 0.2$  s?






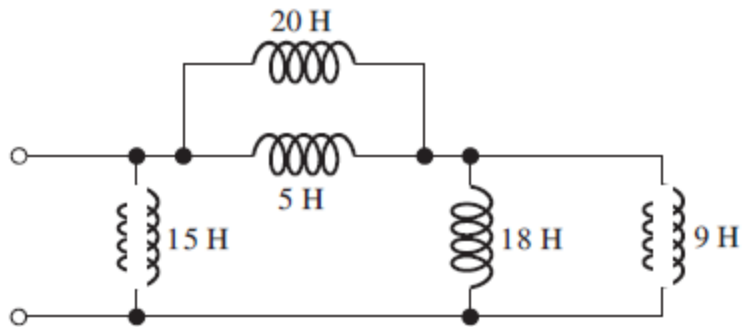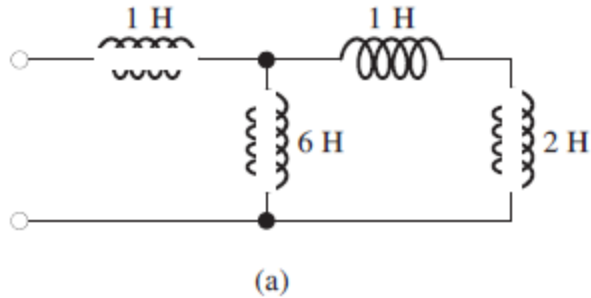
\*P3.60. Determine the equivalent inductance for each of the series and parallel combinations shown in Figure P3.60.



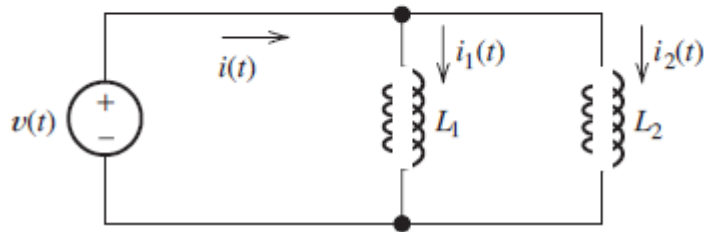\*P3.61. Two inductances  $L_1 = 1\text{ H}$  and  $L_2 = 2\text{ H}$  are connected in parallel as shown in Figure P3.61. The initial currents are  $i_1(0) = 0$  and  $i_2(0) = 0$ . Find an expression for  $i_1(t)$  in terms of  $i(t)$ ,  $L_1$ , and  $L_2$ . Repeat for  $i_2(t)$ . Comment.



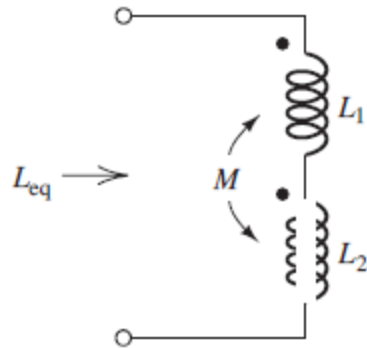
- \*P3.72. **a.** Derive an expression for the equivalent inductance for the circuit shown in Figure P3.72. **b.** Repeat if the dot for  $L_2$  is moved to the bottom end.



**T3.1.** The current flowing through a  $10\text{-}\mu\text{F}$  capacitor having terminals labeled  $a$  and  $b$  is  $i_{ab} = 0.3 \exp(-2000t)$  A for  $t \geq 0$ . Given that  $v_{ab}(0) = 0$ , find an expression for  $v_{ab}(t)$  for  $t \geq 0$ . Then, find the energy stored in the capacitor for  $t = \infty$ .



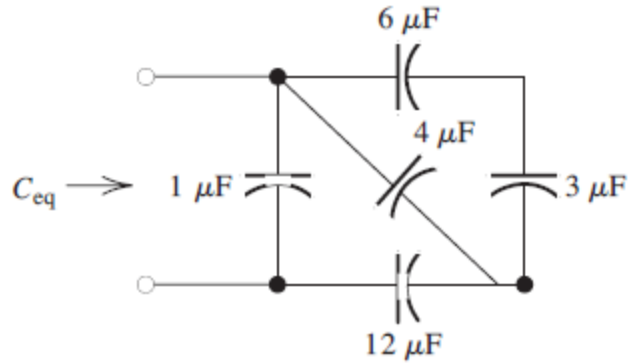**T3.2.** Determine the equivalent capacitance  $C_{eq}$  for Figure T3.2.




**T3.3.** A certain parallel-plate capacitor has plate length of 2 cm and width of 3 cm. The dielectric has a thickness of 0.1 mm and a relative dielectric constant of 80. Determine the capacitance.



**T3.4.** A 2-mH inductance has  $i_{ab} = 0.3 \sin(2000t)$  A. Find an expression for  $v_{ab}(t)$ . Then, find the peak energy stored in the inductance.



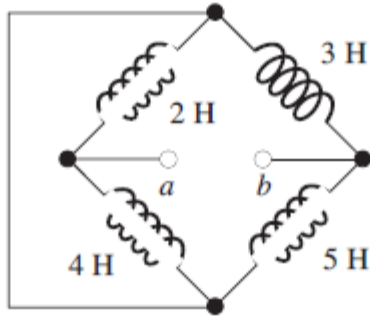**T3.5.** Determine the equivalent inductance  $L_{eq}$  between terminals  $a$  and  $b$  in Figure T3.5.





**T3.6.** Figure T3.6 has  $L_1 = 40$  mH,  $M = 20$  mH, and  $L_2 = 30$  mH. Find expressions for  $v_1(t)$  and  $v_2(t)$ .

