



دانشگاه سمنان

Semnan University  
Faculty of Mechanical Engineering

دانشکده مهندسی مکانیک



دانشکده مهندسی مکانیک

تمرین درس مبانی برق ۱

نام و شماره دانشجویی:


## INTRODUCTION TO ELECTRICAL ENGINEERING EXERCISES

Chapter 4 – Transients


**\*P4.4.** A  $100\text{-}\mu\text{F}$  capacitance is initially charged to  $1000\text{V}$ . At  $t = 0$ , it is connected to a  $1\text{-k}\Omega$  resistance. At what time  $t_2$  has 50 percent of the initial energy stored in the capacitance been dissipated in the resistance?



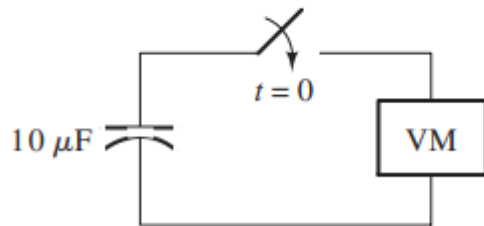
**\*P4.5.** At  $t = 0$ , a charged  $10\text{-}\mu\text{F}$  capacitance is connected to a voltmeter, as shown in Figure P4.5. The meter can be modeled as a resistance. At  $t = 0$ , the meter reads  $50\text{ V}$ . At  $t = 30\text{ s}$ , the reading is  $25\text{ V}$ . Find the resistance of the voltmeter.



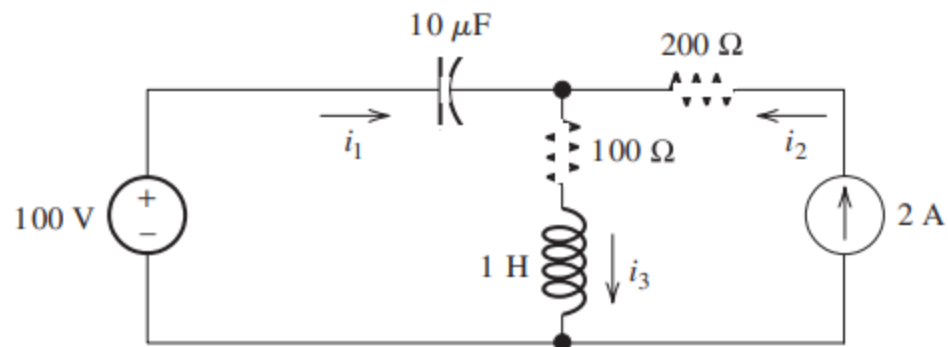
**\*P4.21.** Solve for the steady-state values of  $i_1$ ,  $i_2$ , and  $i_3$  for the circuit shown in Figure P4.21.



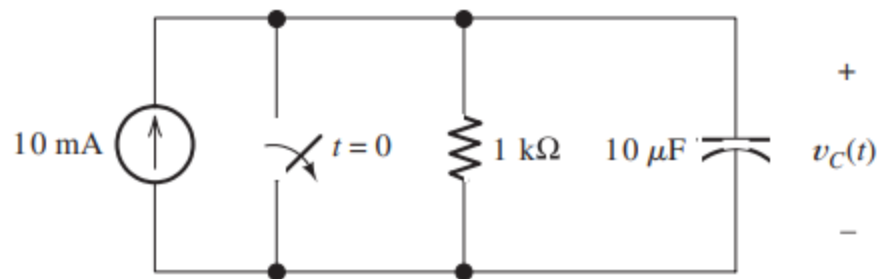
**\*P4.22.** Consider the circuit shown in Figure P4.22. What is the steady-state value of  $v_C$  after the switch opens? Determine how long it takes after the switch opens before  $v_C$  is within 1 percent of its steady-state value.



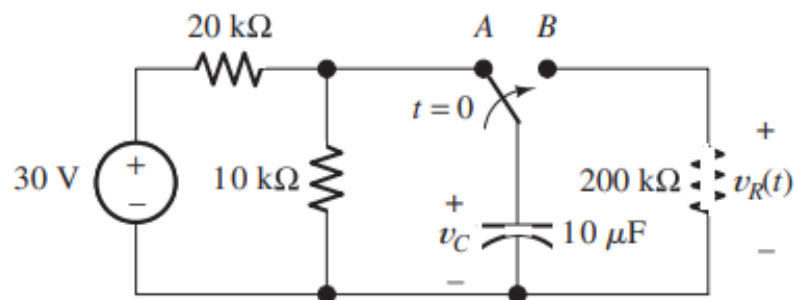
**\*P4.23.** In the circuit of Figure P4.23, the switch is in position *A* for a long time prior to  $t = 0$ . Find expressions for  $v_R(t)$  and sketch it to scale for  $-2 \leq t \leq 10$  s.



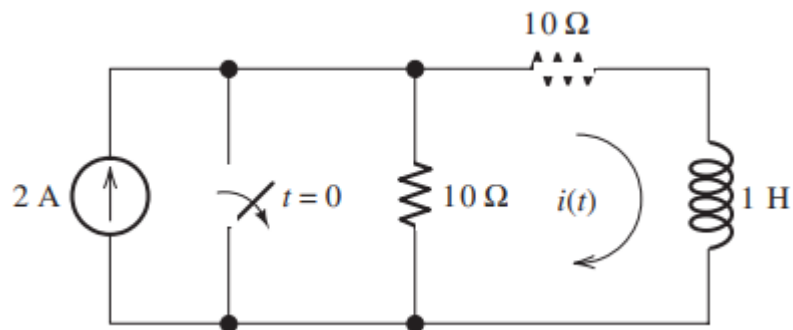**\*P4.33.** The circuit shown in Figure P4.33 is operating in steady state with the switch closed prior to  $t = 0$ . Find  $i(t)$  for  $t < 0$  and for  $t \geq 0$ .




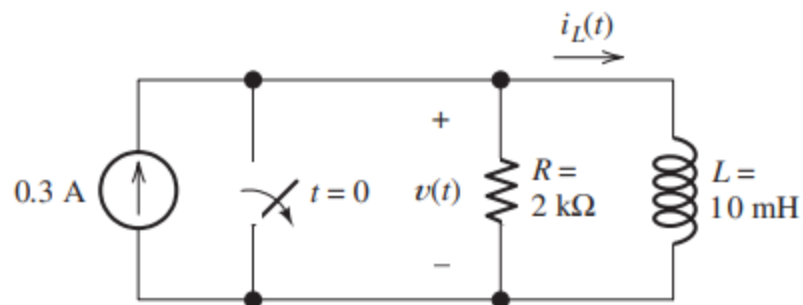**\*P4.34.** Consider the circuit shown in Figure P4.34. The initial current in the inductor is  $i_L(0^-) = -0.2$  A. Find expressions for  $i_L(t)$  and  $v(t)$  for  $t \geq 0$  and sketch to scale versus time.






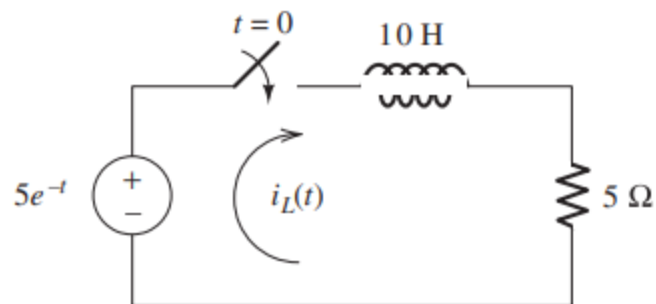
**\*P4.45.** Write the differential equation for  $i_L(t)$  and find the complete solution for the circuit of Figure P4.45. [Hint: Try a particular solution of the form  $i_{Lp}(t) = Ae^{-t}$ .]



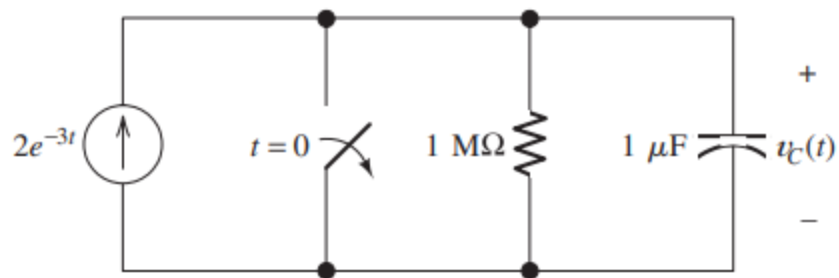**\*P4.46.** Solve for  $v_C(t)$  for  $t > 0$  in the circuit of Figure P4.46. [*Hint:* Try a particular solution of the form  $v_{Cp}(t) = Ae^{-3t}$ .]



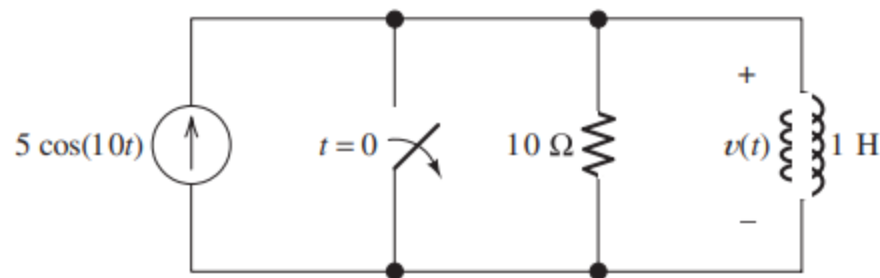**\*P4.47.** Solve for  $v(t)$  for  $t > 0$  in the circuit of Figure P4.47, given that the inductor current is zero prior to  $t = 0$ . [Hint: Try a particular solution of the form  $v_p = A \cos(10t) + B \sin(10t)$ .]



**\*P4.61.** A dc source is connected to a series  $RLC$  circuit by a switch that closes at  $t = 0$ , as shown in Figure P4.61. The initial conditions are  $i(0+) = 0$  and  $v_C(0+) = 0$ . Write the differential equation for  $v_C(t)$ . Solve for  $v_C(t)$ , if  $R = 80 \Omega$ .

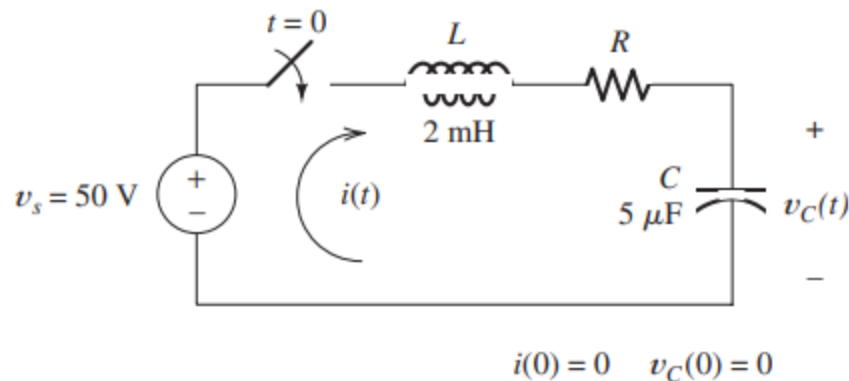



Figure P4.61

**\*P4.62.** Repeat Problem P4.61 for  $R = 40 \Omega$ .


**\*P4.63.** Repeat Problem P4.61 for  $R = 20 \Omega$ .



**T4.1.** Consider the circuit shown in Figure T4.1. The circuit has been operating for a long time with the switch closed prior to  $t = 0$ . **a.** Determine the values of  $i_L$ ,  $i_1$ ,  $i_2$ ,  $i_3$ , and  $v_C$  just before the switch opens. **b.** Determine the values of  $i_L$ ,  $i_1$ ,  $i_2$ ,  $i_3$ , and  $v_C$  immediately after the switch opens. **c.** Find  $i_L(t)$  for  $t > 0$ . **d.** Find  $v_C(t)$  for  $t > 0$ .

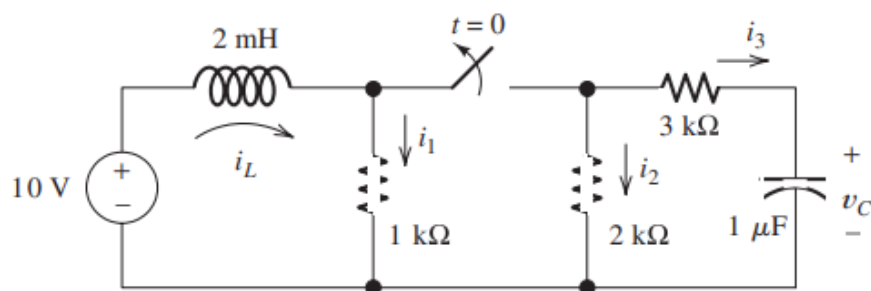

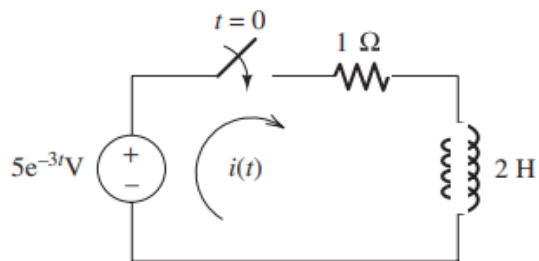- T4.2.** Consider the circuit shown in Figure T4.2.
- Write the differential equation for  $i(t)$ .
  - Find the time constant and the form of the complementary solution.
  - Find the particular solution.
  - Find the complete solution for  $i(t)$ .



**T4.3.** Consider the circuit shown in Figure T4.3 in which the initial inductor current and capacitor voltage are both zero.

- Write the differential equation for  $v_C(t)$ .
- Find the particular solution.
- Is this circuit overdamped, critically damped, or underdamped? Find the form of the complementary solution.
- Find the complete solution for  $v_C(t)$ .

