



دانشگاه سمنان

Semnan University  
Faculty of Mechanical Engineering

دانشکده مهندسی مکانیک



دانشکده مهندسی مکانیک

درس مبانی برق ۱


نیمسال اول ۹۸-۹۹

# ELECTRICAL ENGINEERING

PRINCIPLES AND APPLICATIONS

Allan R. Hambley

5<sup>th</sup> Edition

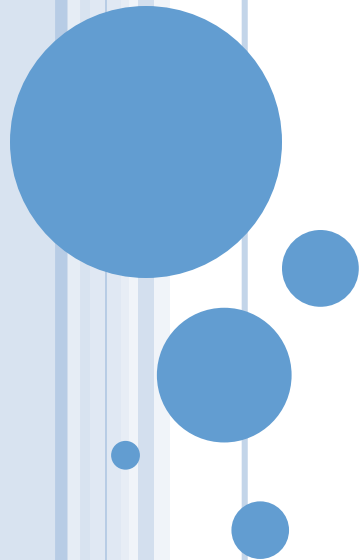

### ❑ CONTENTS:

- ❖ Chapter 1: Introduction
- ❖ Chapter 2: Resistive Circuits
- ❖ Chapter 3: Inductance and Capacitance
- ❖ Chapter 4: Transients
- ❖ Chapter 5: **Steady-State Sinusoidal Analysis**



## INTRODUCTION

- ❑ Identify sinusoidal signal properties
- ❑ Analyze steady-state ac circuits (using phasors and complex impedances)
- ❑ Power of steady-state ac circuits
- ❑ Thévenin and Norton equivalent circuits
- ❑ Determine load impedances for maximum power transfer
- ❑ Introduction to three-phase power distribution
- ❑ Analyze balanced three-phase circuits



## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ Sinusoidal voltage

$$v(t) = V_m \cos(\omega t + \theta)$$

$V_m$  is the **peak value**

$\omega$  is the **angular frequency**


$\theta$  is the **phase angle**.

**period  $T$**        $\omega T = 2\pi$

**frequency**       $f = \frac{1}{T}$  hertz (Hz).

**angular frequency**       $\omega = \frac{2\pi}{T}$        $\rightarrow$        $\omega = 2\pi f$

radians per second (rad/s)

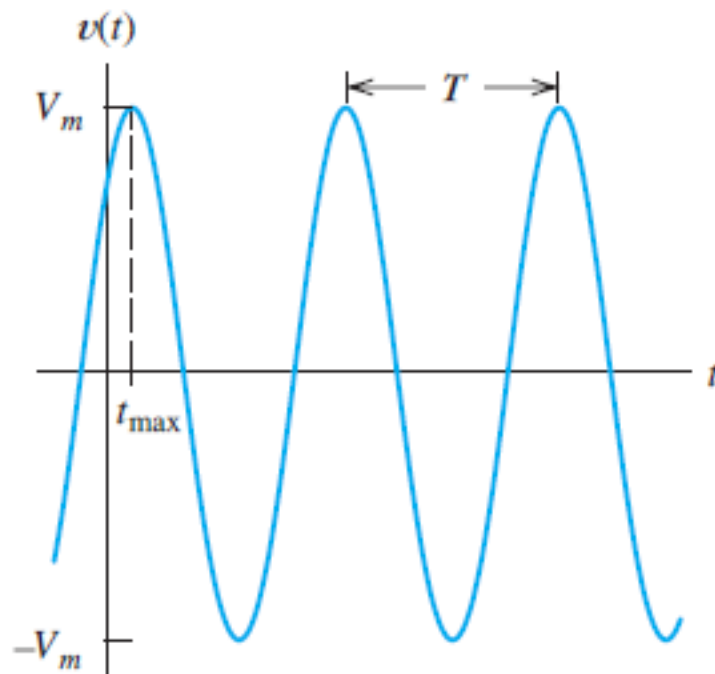

## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

□ For uniformity:

❖ express sinusoidal functions by using the cosine function

$$\sin(z) = \cos(z - 90^\circ)$$

$$v_x(t) = 10 \sin(200t + 30^\circ) \quad \longrightarrow \quad v_x(t) = 10 \cos(200t + 30^\circ - 90^\circ) \\ = 10 \cos(200t - 60^\circ)$$



## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ Root-Mean-Square Values (RMS)

❖ Applying a periodic voltage  $v(t)$  with period  $T$  to a resistance  $R$

✓ Power 
$$p(t) = \frac{v^2(t)}{R}$$

✓ Energy (in one T) 
$$E_T = \int_0^T p(t) dt$$

✓ Average power 
$$P_{\text{avg}} = \frac{E_T}{T} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt$$

$$\Rightarrow P_{\text{avg}} = \frac{\left[ \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \right]^2}{R}$$



## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ Root-Mean-Square Values (RMS)

❖ **root-mean-square** (rms) value of the periodic voltage  $v(t)$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$\Rightarrow P_{\text{avg}} = \frac{V_{\text{rms}}^2}{R}$$

❖ rms value is also called the **effective value**



## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ Root-Mean-Square Values (RMS)

❖ Similarly for current:

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$P_{\text{avg}} = I_{\text{rms}}^2 R$$



## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ RMS Value of a Sinusoid

$$v(t) = V_m \cos(\omega t + \theta)$$

$$\Rightarrow V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t + \theta) dt}$$

$$\cos^2(z) = \frac{1}{2} + \frac{1}{2} \cos(2z)$$

$$\Rightarrow V_{\text{rms}} = \sqrt{\frac{V_m^2}{2T} \int_0^T [1 + \cos(2\omega t + 2\theta)] dt}$$

$$\Rightarrow V_{\text{rms}} = \sqrt{\frac{V_m^2}{2T} \left[ t + \frac{1}{2\omega} \sin(2\omega t + 2\theta) \right]_0^T}$$



## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ RMS Value of a Sinusoid

$$\rightarrow V_{\text{rms}} = \sqrt{\frac{V_m^2}{2T} \left[ T + \frac{1}{2\omega} \sin(2\omega T + 2\theta) - \frac{1}{2\omega} \sin(2\theta) \right]}$$

$$\begin{aligned} \frac{1}{2\omega} \sin(2\omega T + 2\theta) - \frac{1}{2\omega} \sin(2\theta) &= \frac{1}{2\omega} \sin(4\pi + 2\theta) - \frac{1}{2\omega} \sin(2\theta) \\ &= \frac{1}{2\omega} \sin(2\theta) - \frac{1}{2\omega} \sin(2\theta) \\ &= 0 \end{aligned}$$

$$\rightarrow V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$



## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

## Example 5.1 Power Delivered to a Resistance by a Sinusoidal Source


$$v(t) = 100 \cos(100\pi t) \text{ V}$$

50- $\Omega$  resistance

$$\omega = 100\pi$$

$$f = \omega/2\pi = 50 \text{ Hz}$$

$$T = 1/f = 20 \text{ ms}$$

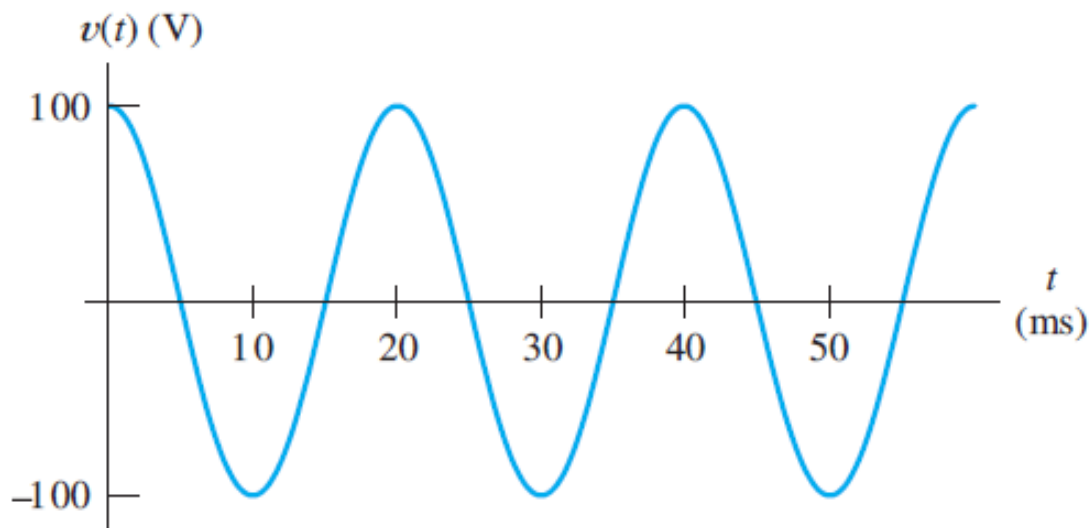

$$V_m = 100 \text{ V.} \quad \Rightarrow \quad V_{\text{rms}} = V_m/\sqrt{2} = 70.71 \text{ V.}$$




## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES
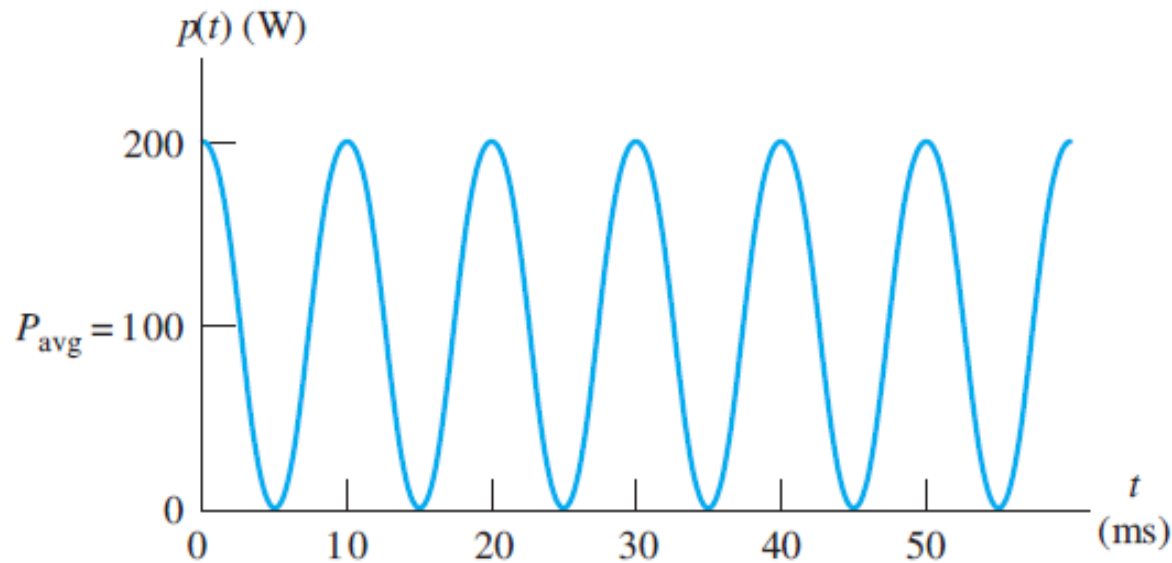
## Example 5.1 Power Delivered to a Resistance by a Sinusoidal Source

$$\Rightarrow P_{\text{avg}} = \frac{V_{\text{rms}}^2}{R} = \frac{(70.71)^2}{50} = 100 \text{ W}$$

$$p(t) = \frac{v^2(t)}{R} = \frac{100^2 \cos^2(100\pi t)}{50} = 200 \cos^2(100\pi t) \text{ W}$$




## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ RMS Values of Nonsinusoidal Voltages or Currents

#### Example 5.2 RMS Value of a Triangular Voltage

$t = 0$  and  $t = T = 2$  s

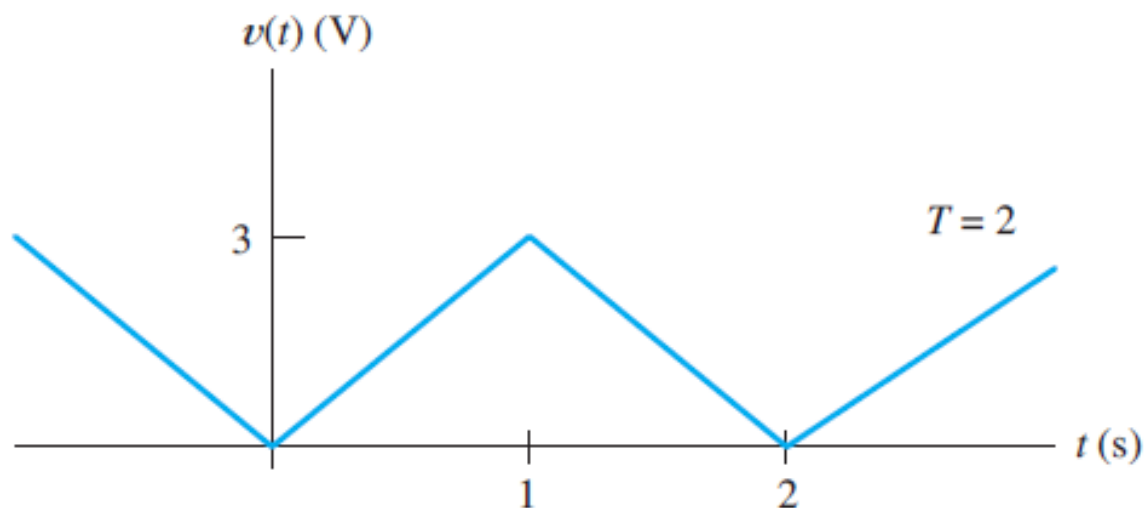


## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ RMS Values of Nonsinusoidal Voltages or Currents
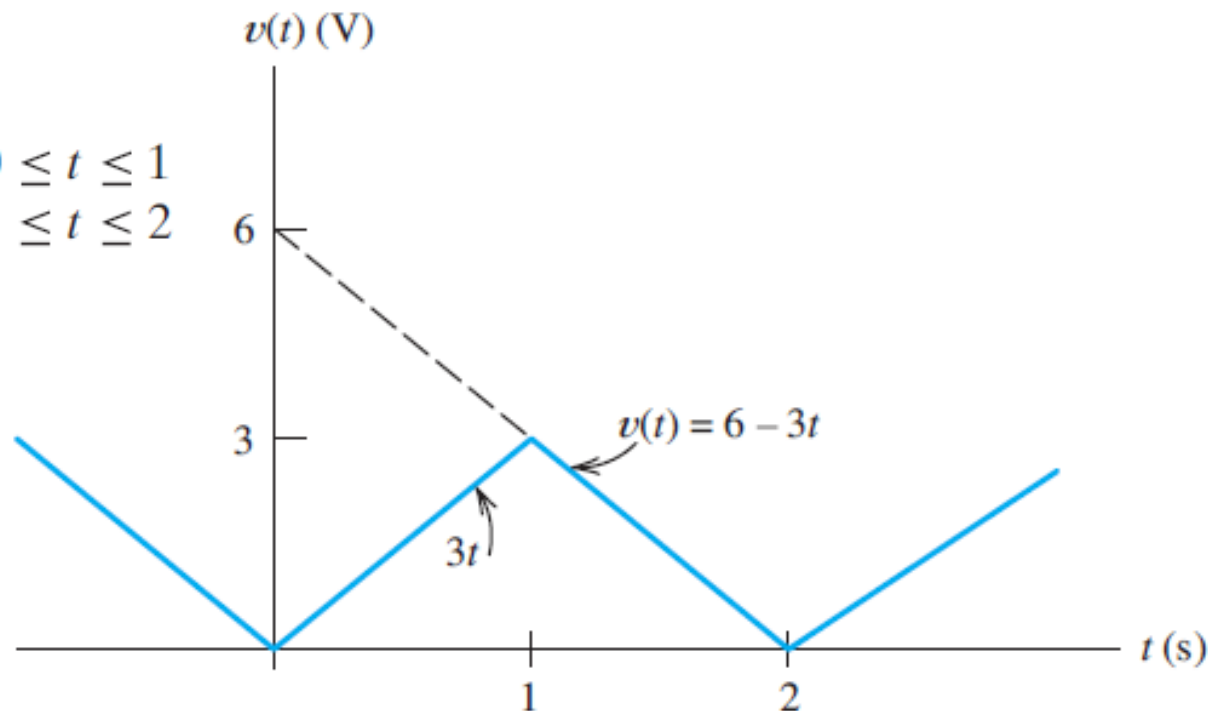
#### Example 5.2 RMS Value of a Triangular Voltage

$$v(t) = \begin{cases} 3t & \text{for } 0 \leq t \leq 1 \\ 6 - 3t & \text{for } 1 \leq t \leq 2 \end{cases}$$



## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ RMS Values of Nonsinusoidal Voltages or Currents

#### Example 5.2 RMS Value of a Triangular Voltage

$$\begin{aligned}
 V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \\
 &= \sqrt{\frac{1}{2} \left[ \int_0^1 9t^2 dt + \int_1^2 (6 - 3t)^2 dt \right]} \\
 &= \sqrt{\frac{1}{2} \left[ 3t^3 \Big|_{t=0}^{t=1} + (36t - 18t^2 + 3t^3) \Big|_{t=1}^{t=2} \right]} \\
 &= \sqrt{\frac{1}{2} [3 + (72 - 36 - 72 + 18 + 24 - 3)]} = \sqrt{3} \text{ V}
 \end{aligned}$$




## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

### □ Exercise

$$v(t) = 150 \cos(200\pi t - 30^\circ) \text{ V}$$

$$\omega = 200\pi, f = 100 \text{ Hz}, T = 10 \text{ ms},$$
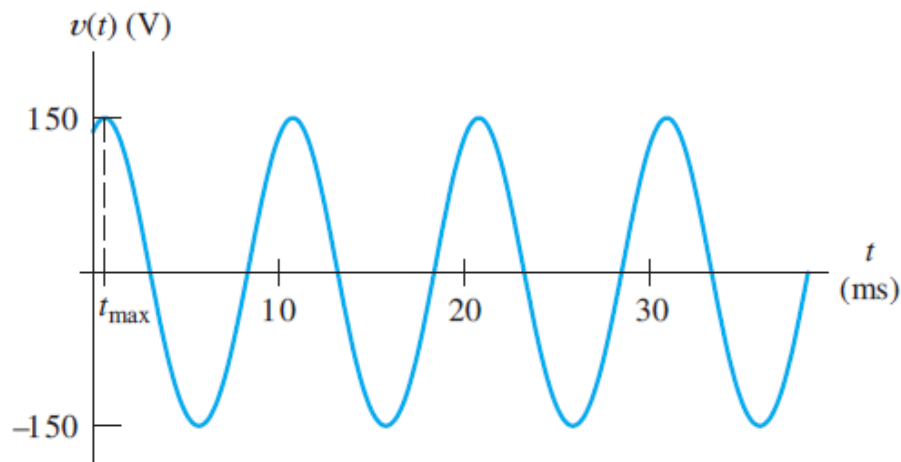
$$V_m = 150 \text{ V}, V_{\text{rms}} = 106.1 \text{ V},$$



❖ First  $t_{\max}$  after  $t = 0 \text{ s}$ :

$$t_{\max} = \frac{30^\circ}{360^\circ} \times T = 0.833 \text{ ms}$$





## 5.1 SINUSOIDAL CURRENTS AND VOLTAGES

□ Exercise Express  $v(t) = 100 \sin(300\pi t + 60^\circ)$  V as a cosine function

$$\Rightarrow v(t) = 100 \cos(300\pi t - 30^\circ) \text{ V.}$$

□ Exercise

❖ rms value: 110V

❖ Frequency: 60Hz

❖ Peak voltage at  $t = 5\text{ms}$

$$\Rightarrow v(t) = 155.6 \cos(377t - 108^\circ) \text{ V.}$$



## 5.2 PHASORS

□ Vector representation of sinusoidal signals in complex-number plane

□ Convenient method for ac circuits:

❖ For example: KVL leads to

$$v(t) = 10 \cos(\omega t) + 5 \sin(\omega t + 60^\circ) + 5 \cos(\omega t + 90^\circ)$$

❖ Put into form:

$$v(t) = V_m \cos(\omega t + \theta)$$

❖ Using standard trigonometric identities...



## 5.2 PHASORS

### □ Phasor Definition

❖ For sinusoidal voltages:

$$v_1(t) = V_1 \cos(\omega t + \theta_1) \quad \Rightarrow \quad \mathbf{V}_1 = V_1 \underline{\angle \theta_1}$$

$$v_2(t) = V_2 \sin(\omega t + \theta_2)$$

$$\sin(z) = \cos(z - 90^\circ) \quad \Rightarrow \quad v_2(t) = V_2 \cos(\omega t + \theta_2 - 90^\circ)$$

$$\Rightarrow \quad \mathbf{V}_2 = V_2 \underline{\angle \theta_2 - 90^\circ}$$



## 5.2 PHASORS

### □ Phasor Definition

❖ For sinusoidal currents:

$$i_1(t) = I_1 \cos(\omega t + \theta_1) \quad \Rightarrow \quad \mathbf{I}_1 = I_1 \underline{\angle \theta_1}$$

$$i_2(t) = I_2 \sin(\omega t + \theta_2) \quad \Rightarrow \quad \mathbf{I}_2 = I_2 \underline{\angle \theta_2 - 90^\circ}$$



## 5.2 PHASORS

### □ Adding Sinusoids Using Phasors

$$v(t) = 10 \cos(\omega t) + 5 \sin(\omega t + 60^\circ) + 5 \cos(\omega t + 90^\circ)$$

$$\Rightarrow v(t) = 10 \cos(\omega t) + 5 \cos(\omega t + 60^\circ - 90^\circ) + 5 \cos(\omega t + 90^\circ)$$

$$\Rightarrow v(t) = 10 \cos(\omega t) + 5 \cos(\omega t - 30^\circ) + 5 \cos(\omega t + 90^\circ)$$

Euler's formula  $\cos(\theta) = \operatorname{Re}\left(e^{j\theta}\right) = \operatorname{Re}[\cos(\theta) + j\sin(\theta)]$

$$\Rightarrow v(t) = 10 \operatorname{Re}\left[e^{j\omega t}\right] + 5 \operatorname{Re}\left[e^{j(\omega t - 30^\circ)}\right] + 5 \operatorname{Re}\left[e^{j(\omega t + 90^\circ)}\right]$$

$$\Rightarrow v(t) = \operatorname{Re}\left[10e^{j\omega t}\right] + \operatorname{Re}\left[5e^{j(\omega t - 30^\circ)}\right] + \operatorname{Re}\left[5e^{j(\omega t + 90^\circ)}\right]$$



## 5.2 PHASORS

### □ Adding Sinusoids Using Phasors

$$\Rightarrow v(t) = \text{Re} \left[ 10e^{j\omega t} + 5e^{j(\omega t - 30^\circ)} + 5e^{j(\omega t + 90^\circ)} \right]$$

$$\Rightarrow v(t) = \text{Re} \left[ \left( 10 + 5e^{-j30^\circ} + 5e^{j90^\circ} \right) e^{j\omega t} \right]$$

$$\Rightarrow v(t) = \text{Re} \left[ \left( 10 \angle 0^\circ + 5 \angle -30^\circ + 5 \angle 90^\circ \right) e^{j\omega t} \right]$$

$$\begin{aligned} \Rightarrow 10 \angle 0^\circ + 5 \angle -30^\circ + 5 \angle 90^\circ &= 10 + 4.33 - j2.50 + j5 \\ &= 14.33 + j2.5 \\ &= 14.54 \angle 9.90^\circ \\ &= 14.54e^{j9.90^\circ} \end{aligned}$$



## 5.2 PHASORS

### □ Adding Sinusoids Using Phasors

$$\Rightarrow v(t) = \operatorname{Re} \left[ \left( 14.54 e^{j9.90^\circ} \right) e^{j\omega t} \right]$$

$$\Rightarrow v(t) = \operatorname{Re} \left[ 14.54 e^{j(\omega t + 9.90^\circ)} \right]$$

$$\Rightarrow v(t) = 14.54 \cos(\omega t + 9.90^\circ)$$

### □ Streamlined Procedure for Adding Sinusoids

- ❖ Write the phasor for each term
- ❖ Add the phasors by using complex-number arithmetic



## 5.2 PHASORS

### Example 5.3 Using Phasors to Add Sinusoids

$$v_1(t) = 20 \cos(\omega t - 45^\circ)$$

$$v_2(t) = 10 \sin(\omega t + 60^\circ)$$

$$\Rightarrow \begin{aligned} \mathbf{V}_1 &= 20 \angle -45^\circ \\ \mathbf{V}_2 &= 10 \angle -30^\circ \end{aligned}$$

$$\Rightarrow v_s(t) = v_1(t) + v_2(t)$$

$$\begin{aligned} \Rightarrow \mathbf{V}_s &= \mathbf{V}_1 + \mathbf{V}_2 \\ &= 20 \angle -45^\circ + 10 \angle -30^\circ \\ &= 14.14 - j14.14 + 8.660 - j5 \\ &= 22.80 - j19.14 \\ &= 29.77 \angle -40.01^\circ \end{aligned}$$

$$\Rightarrow v_s(t) = 29.77 \cos(\omega t - 40.01^\circ)$$





## 5.2 PHASORS

### □ Exercise

$$v_1(t) = 10 \cos(\omega t) + 10 \sin(\omega t)$$

$$i_1(t) = 10 \cos(\omega t + 30^\circ) + 5 \sin(\omega t + 30^\circ)$$

$$i_2(t) = 20 \sin(\omega t + 90^\circ) + 15 \cos(\omega t - 60^\circ)$$

$$v_1(t) = 14.14 \cos(\omega t - 45^\circ)$$

$$\Rightarrow i_1(t) = 11.18 \cos(\omega t + 3.44^\circ)$$

$$i_2(t) = 30.4 \cos(\omega t - 25.3^\circ)$$




## 5.2 PHASORS

### □ Phasors as Rotating Vectors

$$v(t) = V_m \cos(\omega t + \theta)$$

$$\Rightarrow v(t) = \operatorname{Re} \left[ V_m e^{j(\omega t + \theta)} \right]$$
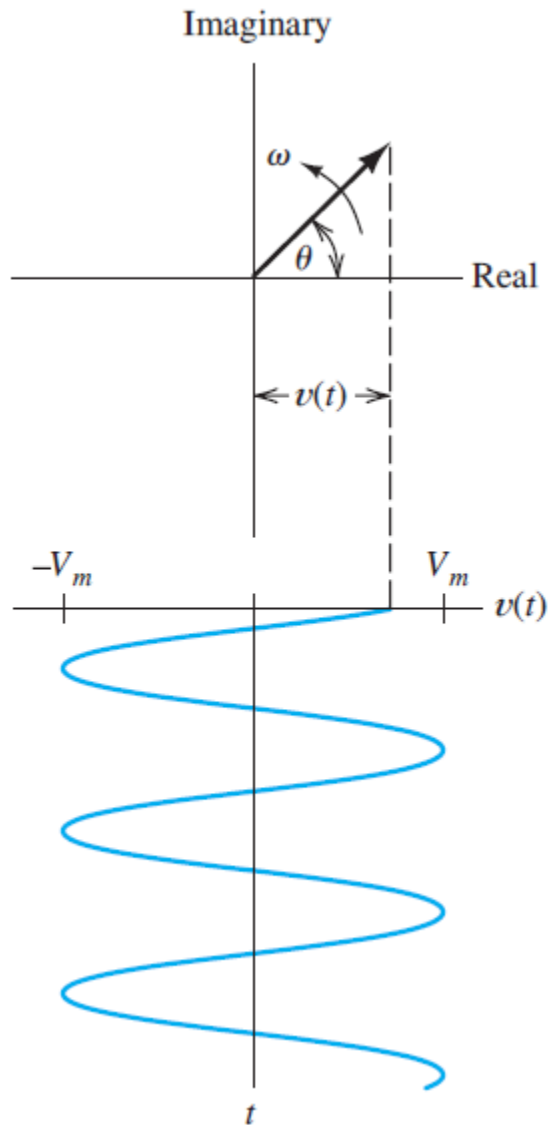
$$\Rightarrow V_m e^{j(\omega t + \theta)} = V_m \angle \omega t + \theta$$



## 5.2 PHASORS

### □ Phase Relationships


$$v_1(t) = 3 \cos(\omega t + 40^\circ)$$

$$v_2(t) = 4 \cos(\omega t - 20^\circ)$$

$$\Rightarrow \mathbf{V}_1 = 3 \angle 40^\circ$$

$$\mathbf{V}_2 = 4 \angle -20^\circ$$

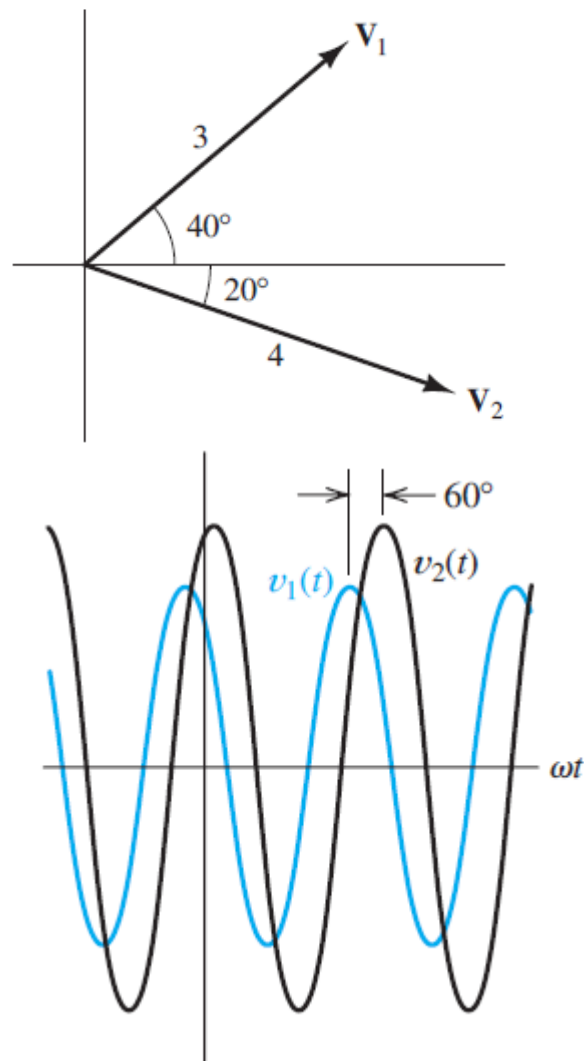$\Rightarrow \mathbf{V}_1$  leads  $\mathbf{V}_2$  by  $60^\circ$   
 $\mathbf{V}_2$  lags  $\mathbf{V}_1$  by  $60^\circ$



## 5.2 PHASORS

### □ Exercise

$$v_1(t) = 10 \cos(\omega t - 30^\circ)$$

$$v_2(t) = 10 \cos(\omega t + 30^\circ)$$

$$v_3(t) = 10 \sin(\omega t + 45^\circ)$$

$v_1$  lags  $v_2$  by  $60^\circ$  (or  $v_2$  leads  $v_1$  by  $60^\circ$ )

→  $v_1$  leads  $v_3$  by  $15^\circ$  (or  $v_3$  lags  $v_1$  by  $15^\circ$ )

$v_2$  leads  $v_3$  by  $75^\circ$  (or  $v_3$  lags  $v_2$  by  $75^\circ$ )



## 5.3 COMPLEX IMPEDANCES

- ❖ Solve sinusoidal steady-state circuit problems using Phasors
- ❖ Use complex arithmetic

### □ Inductance

$$i_L(t) = I_m \sin(\omega t + \theta)$$

$$\Rightarrow v_L(t) = L \frac{di_L(t)}{dt}$$

$$\Rightarrow v_L(t) = \omega L I_m \cos(\omega t + \theta)$$


$$\mathbf{I}_L = I_m \angle \theta - 90^\circ \Rightarrow \mathbf{V}_L = \omega L I_m \angle \theta = V_m \angle \theta$$



## 5.3 COMPLEX IMPEDANCES

### □ Inductance

#### ❖ Phasor diagram

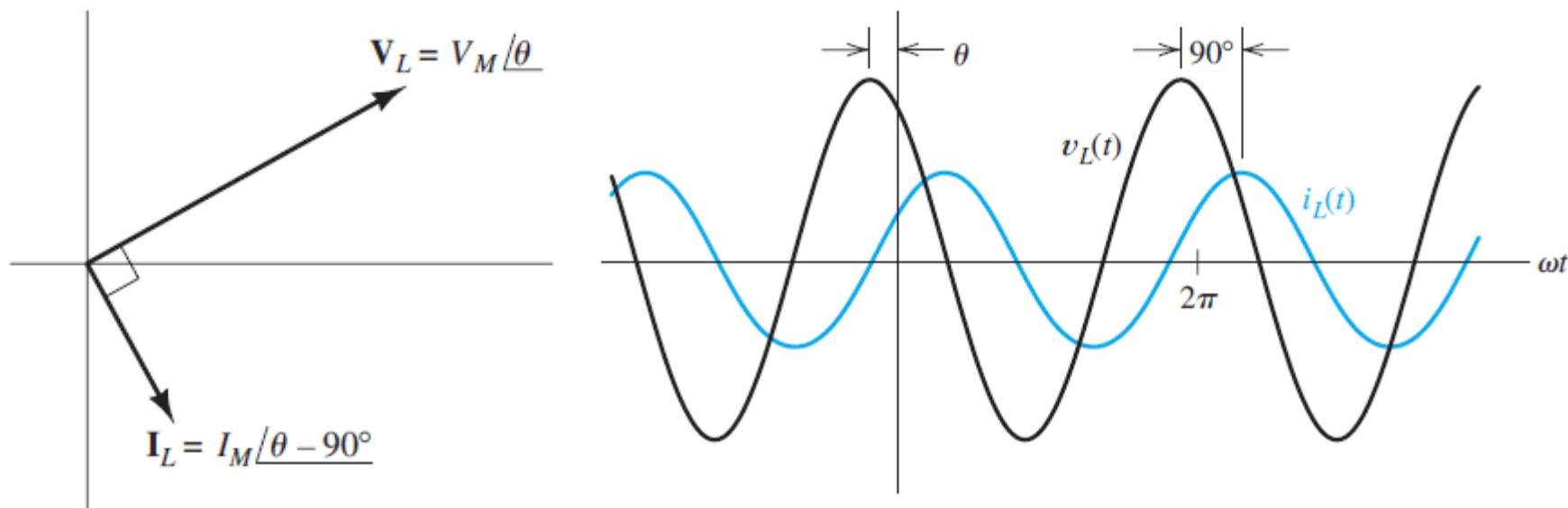

✓ Current lags voltage by 90 degrees for a pure inductance

## 5.3 COMPLEX IMPEDANCES

### □ Inductance

$$\mathbf{V}_L = \omega L I_m \angle \theta = V_m \angle \theta$$

$$\Rightarrow \mathbf{V}_L = (\omega L \angle 90^\circ) \times I_m \angle \theta - 90^\circ$$

$$\Rightarrow \mathbf{V}_L = (\omega L \angle 90^\circ) \times \mathbf{I}_L$$

$$\Rightarrow \mathbf{V}_L = j\omega L \times \mathbf{I}_L$$

**impedance** of the inductance

$$Z_L = j\omega L = \omega L \angle 90^\circ$$

$$\mathbf{V}_L = Z_L \mathbf{I}_L$$



## 5.3 COMPLEX IMPEDANCES

### □ Inductance

❖ Ohm's law in Phasor form

$$\mathbf{V}_L = Z_L \mathbf{I}_L$$

- ✓ For an inductance, the impedance is an imaginary number
- ✓ For a resistance, the impedance is a real number
- ✓ Impedances that are pure imaginary are also called **reactances**






## 5.3 COMPLEX IMPEDANCES
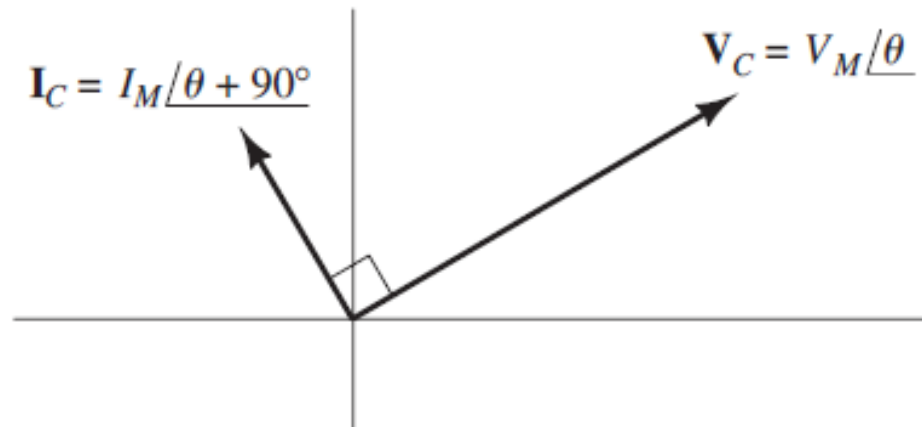
### □ Capacitance

$$\mathbf{V}_C = Z_C \mathbf{I}_C$$

$$Z_C = -j \frac{1}{\omega C} = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$$




## 5.3 COMPLEX IMPEDANCES
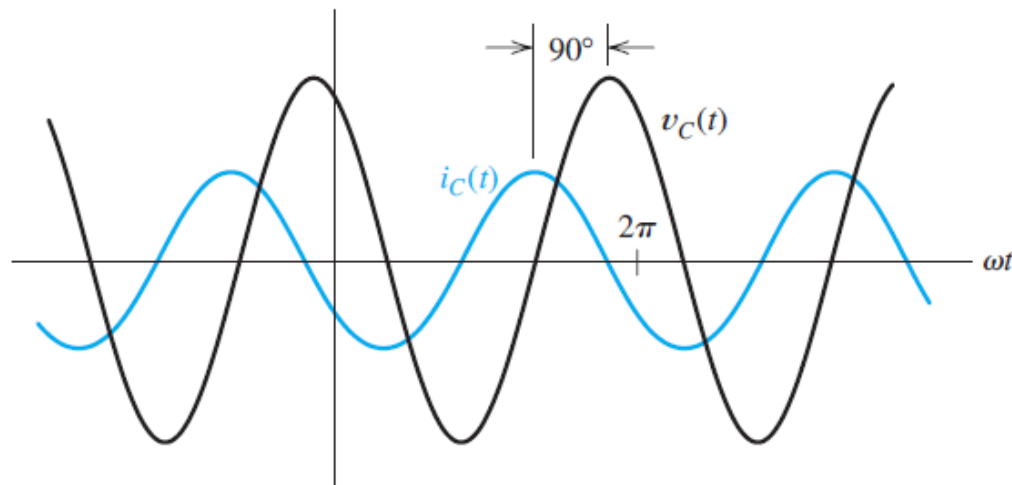
### □ Capacitance

$$\mathbf{V}_C = V_m \angle \theta \quad \Rightarrow \quad \mathbf{I}_C = \frac{\mathbf{V}_C}{Z_C} = \frac{V_m \angle \theta}{(1/\omega C) \angle -90^\circ} = \omega C V_m \angle \theta + 90^\circ$$

$$\Rightarrow \quad \mathbf{I}_C = I_m \angle \theta + 90^\circ$$




✓ Current leads voltage by 90 degrees for a pure capacitance

## 5.3 COMPLEX IMPEDANCES

### □ Resistance

$$\mathbf{V}_R = R\mathbf{I}_R$$

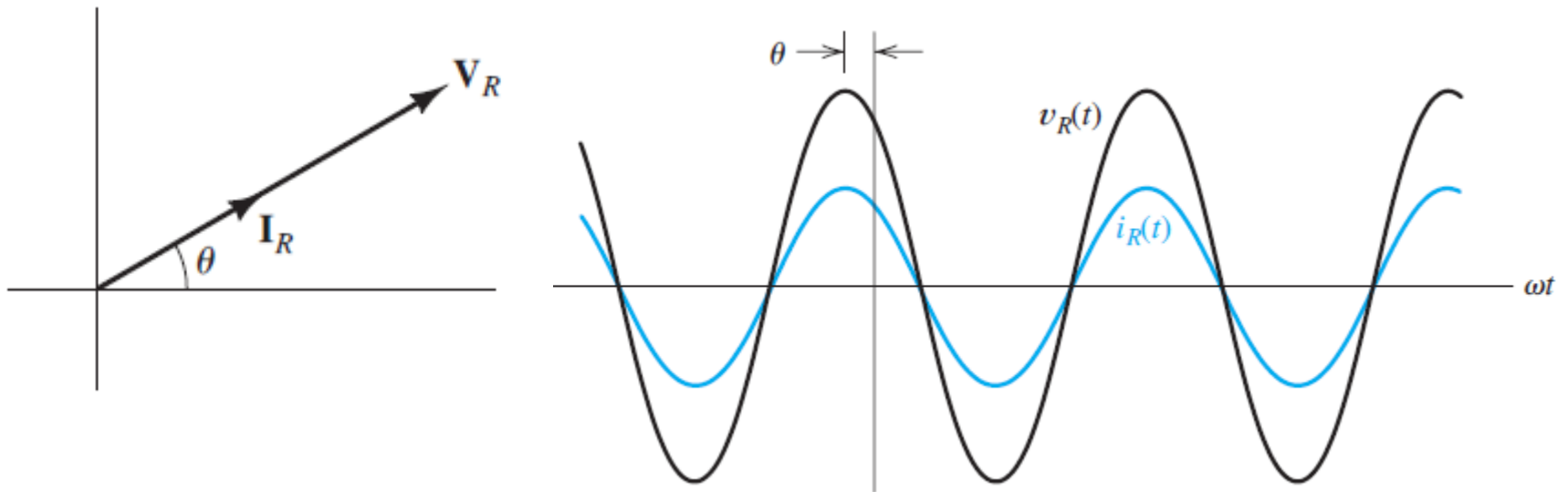

✓ Current and voltage are in phase for a pure resistance

## 5.3 COMPLEX IMPEDANCES

### □ Exercise


0.25-H inductance

$$v_L(t) = 100 \cos(200t)$$

$$\Rightarrow Z_L = j50 = 50 \angle 90^\circ$$

$$\Rightarrow \mathbf{V}_L = 100 \angle 0^\circ$$
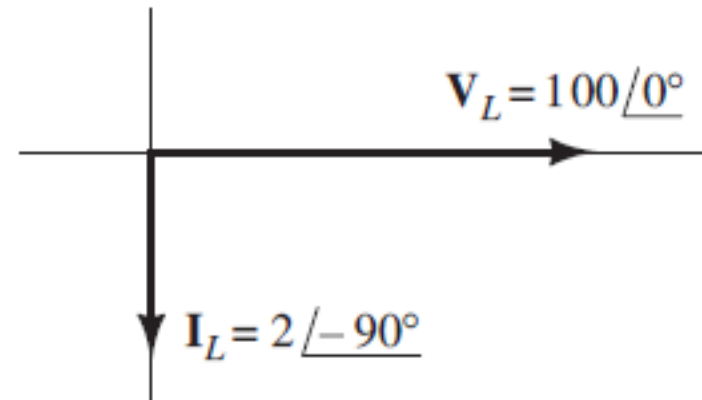
$$\Rightarrow \mathbf{I}_L = 2 \angle -90^\circ$$



## 5.3 COMPLEX IMPEDANCES

### □ Exercise


100- $\mu$ F capacitance

$$v_L(t) = 100 \cos(200t)$$

$$\Rightarrow Z_C = -j50 = 50 \angle -90^\circ$$

$$\Rightarrow V_L = 100 \angle 0^\circ$$

$$\Rightarrow I_C = 2 \angle 90^\circ$$

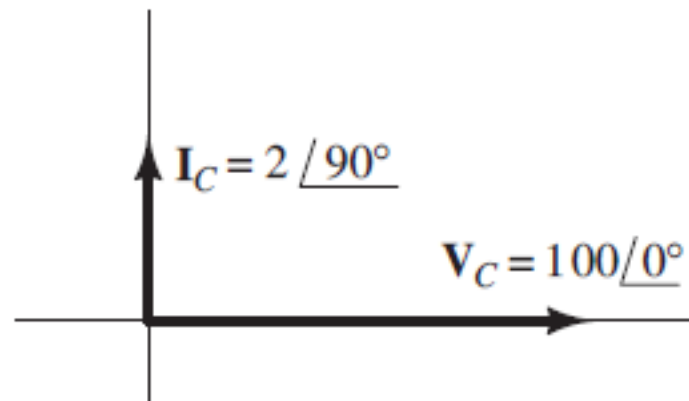

## 5.3 COMPLEX IMPEDANCES


### □ Exercise

50- $\Omega$  resistance

$$v_L(t) = 100 \cos(200t)$$

$$\Rightarrow \mathbf{V}_L = 100 \angle 0^\circ$$
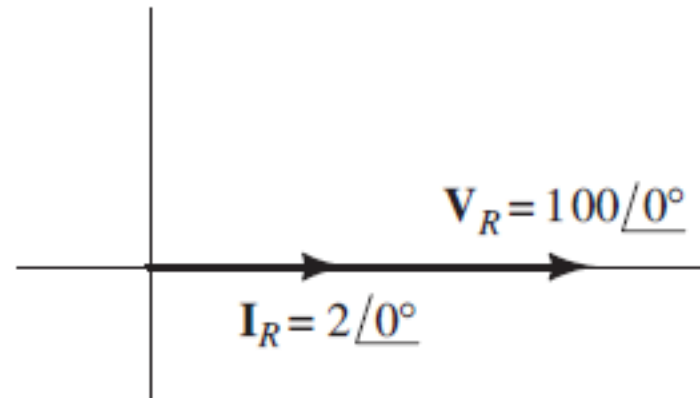
$$\Rightarrow \mathbf{I}_R = 2 \angle 0^\circ$$



## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### □ Kirchhoff's Laws in Phasor Form

❖ KVL equation:

$$v_1(t) + v_2(t) - v_3(t) = 0 \quad \Rightarrow \quad \mathbf{V}_1 + \mathbf{V}_2 - \mathbf{V}_3 = 0$$

❖ Similarly for KCL

### □ Procedure for steady-state analysis of circuits with sinusoidal sources:

- ❖ Replace time descriptions with corresponding phasors
- ❖ Replace inductances and capacitances by their complex impedances
- ❖ Analyze the circuit by using any of previous techniques with complex arithmetic



## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES


### Example 5.4 Steady-State AC Analysis of a Series Circuit

$$\omega = 500$$

$$\mathbf{V}_s = 100 \angle 30^\circ$$

$$Z_L = j\omega L = j500 \times 0.3 = j150 \Omega$$

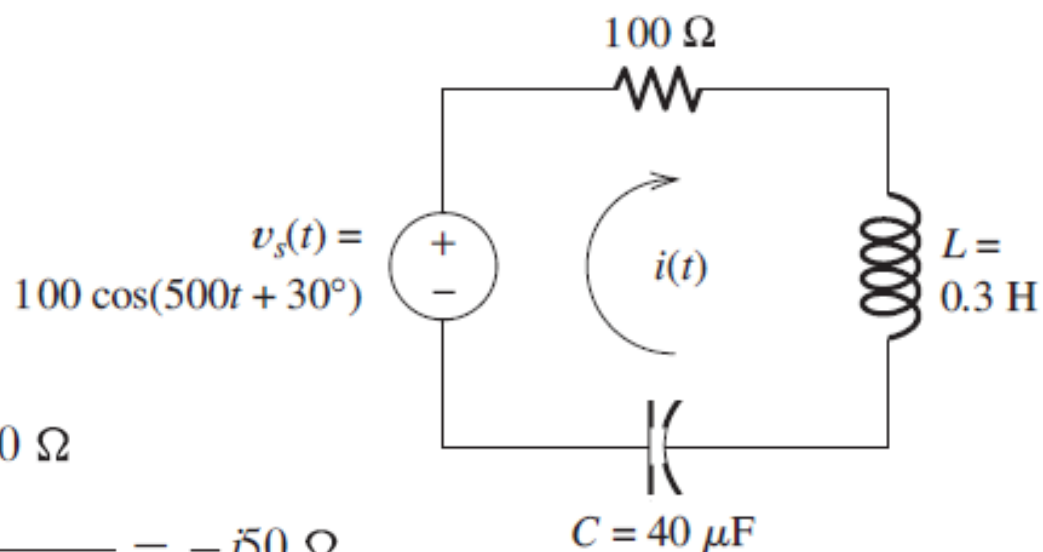
$$Z_C = -j\frac{1}{\omega C} = -j\frac{1}{500 \times 40 \times 10^{-6}} = -j50 \Omega$$





## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES
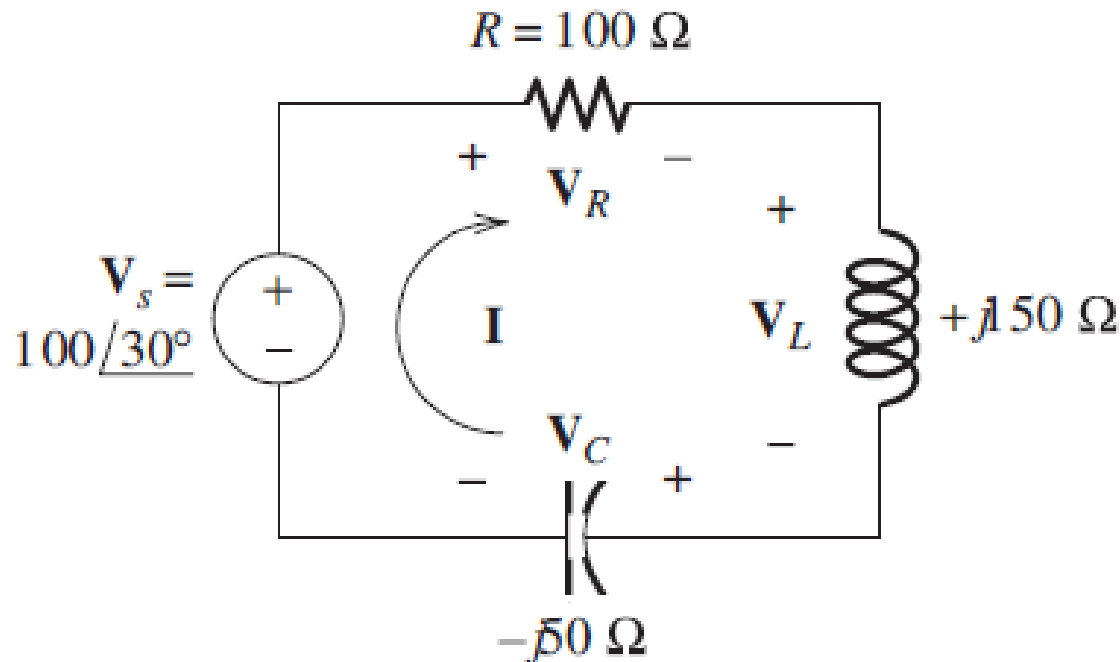
### Example 5.4 Steady-State AC Analysis of a Series Circuit



## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### Example 5.4 Steady-State AC Analysis of a Series Circuit

$$Z_{\text{eq}} = R + Z_L + Z_C \quad \Rightarrow \quad Z_{\text{eq}} = 100 + j150 - j50 = 100 + j100$$

$$\Rightarrow \quad Z_{\text{eq}} = 141.4 \angle 45^\circ$$

$$\Rightarrow \quad \mathbf{I} = \frac{\mathbf{V}_s}{Z} = \frac{100 \angle 30^\circ}{141.4 \angle 45^\circ} = 0.707 \angle -15^\circ$$

$$\Rightarrow \quad i(t) = 0.707 \cos(500t - 15^\circ)$$



## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### Example 5.4 Steady-State AC Analysis of a Series Circuit

$$\mathbf{V}_R = R \times \mathbf{I} = 100 \times 0.707 \angle -15^\circ = 70.7 \angle -15^\circ$$


$$\begin{aligned} \mathbf{V}_L &= j\omega L \times \mathbf{I} = \omega L \angle 90^\circ \times \mathbf{I} = 150 \angle 90^\circ \times 0.707 \angle -15^\circ \\ &= 106.1 \angle 75^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{V}_C &= -j\frac{1}{\omega C} \times \mathbf{I} = \frac{1}{\omega C} \angle -90^\circ \times \mathbf{I} = 50 \angle -90^\circ \times 0.707 \angle -15^\circ \\ &= 35.4 \angle -105^\circ \end{aligned}$$



## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES
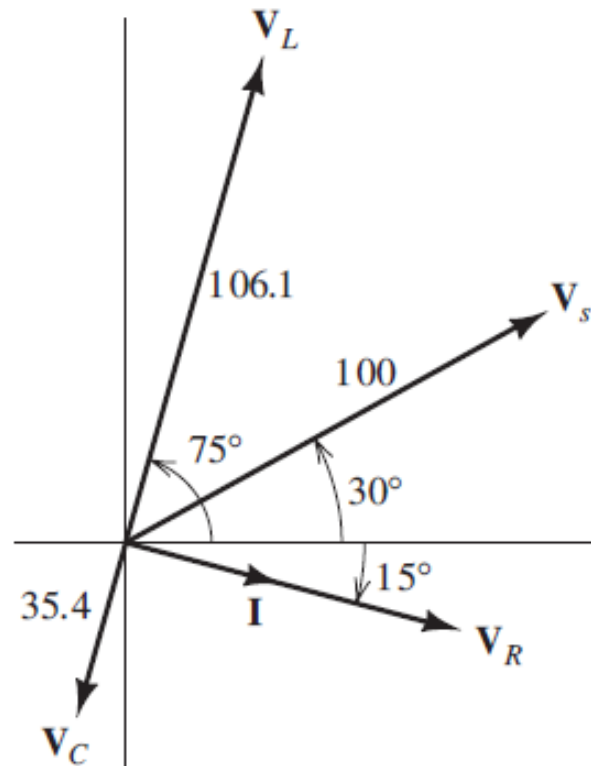
### Example 5.4 Steady-State AC Analysis of a Series Circuit




## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### Example 5.5 Series and Parallel Combinations of Complex Impedances

$$\omega = 1000$$

$$\mathbf{V}_s = 10 \angle -90^\circ$$

$$v_s(t) = 10 \sin(1000t)$$

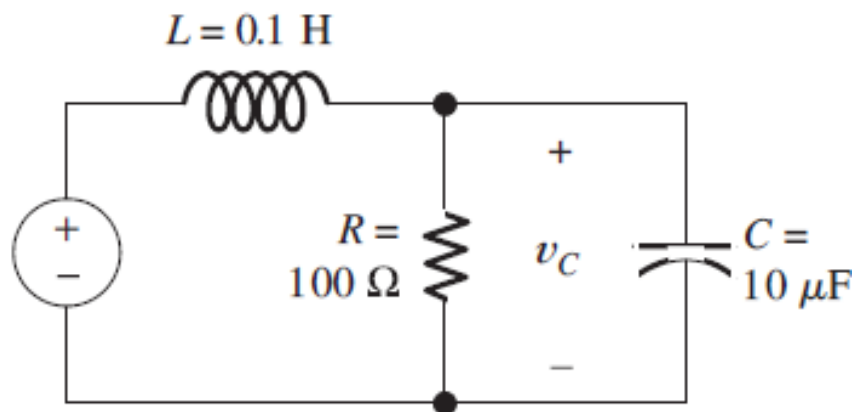


$$Z_L = j\omega L = j1000 \times 0.1 = j100 \Omega$$

$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{1000 \times 10 \times 10^{-6}} = -j100 \Omega$$

## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES
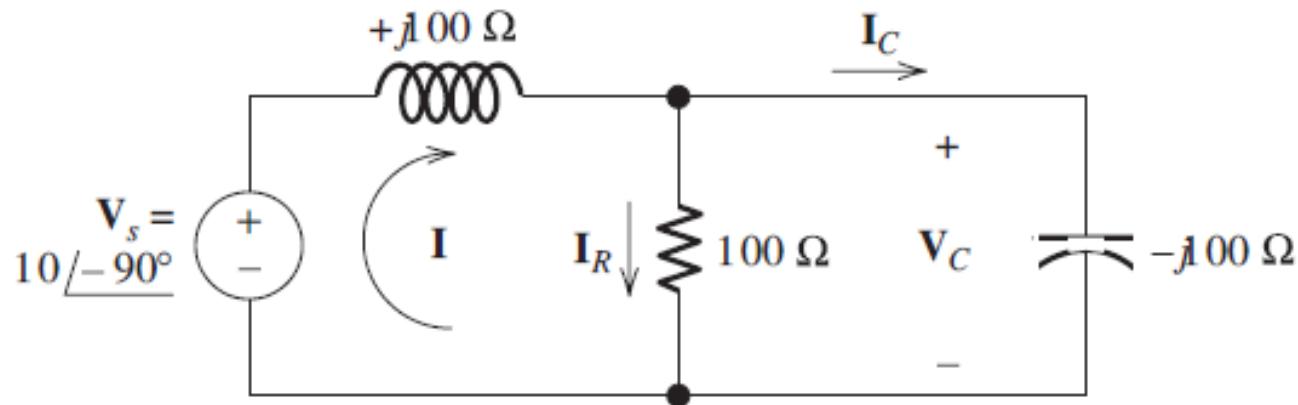
### Example 5.5 Series and Parallel Combinations of Complex Impedances




$$\begin{aligned}
 Z_{RC} &= \frac{1}{1/R + 1/Z_C} = \frac{1}{1/100 + 1/(-j100)} \\
 &= \frac{1}{0.01 + j0.01} = \frac{1 \angle 0^\circ}{0.01414 \angle 45^\circ} = 70.71 \angle -45^\circ
 \end{aligned}$$

## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### Example 5.5 Series and Parallel Combinations of Complex Impedances

$$\Rightarrow Z_{RC} = 50 - j50$$

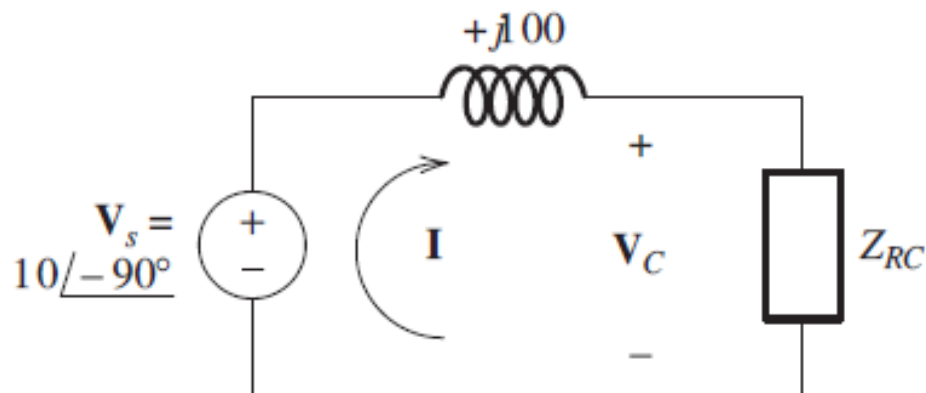

## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### Example 5.5 Series and Parallel Combinations of Complex Impedances

$$\begin{aligned}
 \mathbf{V}_C &= \mathbf{V}_s \frac{Z_{RC}}{Z_L + Z_{RC}} = 10 \angle -90^\circ \frac{70.71 \angle -45^\circ}{j100 + 50 - j50} \\
 &= 10 \angle -90^\circ \frac{70.71 \angle -45^\circ}{50 + j50} = 10 \angle -90^\circ \frac{70.71 \angle -45^\circ}{70.71 \angle 45^\circ} \\
 &= 10 \angle -180^\circ
 \end{aligned}$$

$$\Rightarrow v_C(t) = 10 \cos(1000t - 180^\circ) = -10 \cos(1000t)$$





## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### Example 5.5 Series and Parallel Combinations of Complex Impedances

$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}_s}{Z_L + Z_{RC}} = \frac{10 \angle -90^\circ}{j100 + 50 - j50} = \frac{10 \angle -90^\circ}{50 + j50} \\ &= \frac{10 \angle -90^\circ}{70.71 \angle 45^\circ} = 0.1414 \angle -135^\circ \end{aligned}$$

$$\mathbf{I}_R = \frac{\mathbf{V}_C}{R} = \frac{10 \angle -180^\circ}{100} = 0.1 \angle -180^\circ$$


$$\mathbf{I}_C = \frac{\mathbf{V}_C}{Z_C} = \frac{10 \angle -180^\circ}{-j100} = \frac{10 \angle -180^\circ}{100 \angle -90^\circ} = 0.1 \angle -90^\circ$$



## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### □ Node-Voltage Analysis
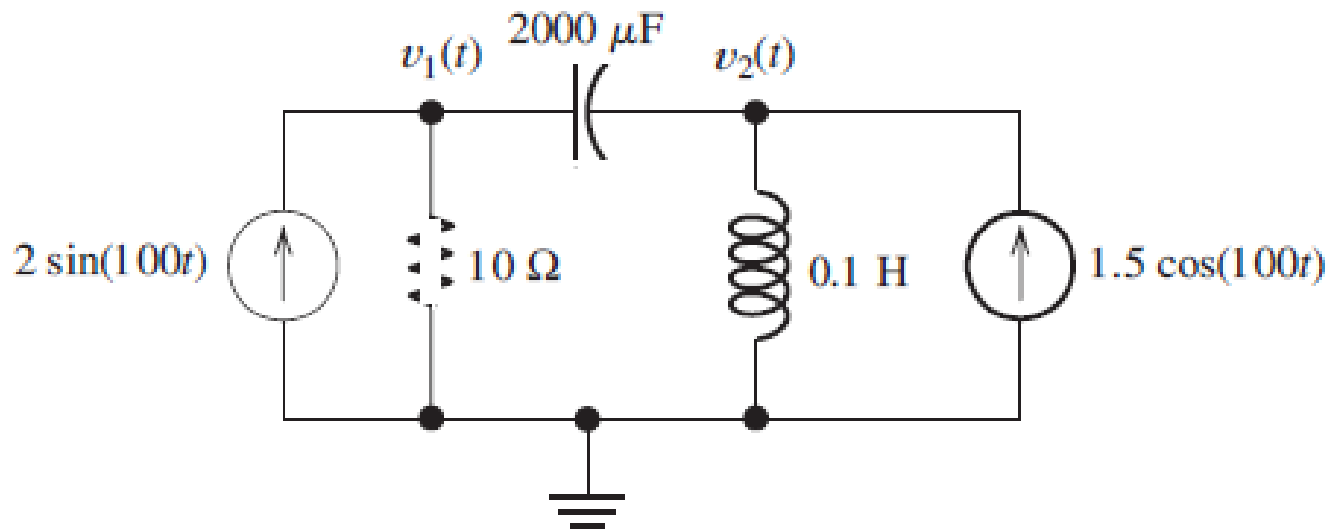
#### Example 5.6 Steady-State AC Node-Voltage Analysis



## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES


### Example 5.6 Steady-State AC Node-Voltage Analysis

$$\frac{\mathbf{V}_1}{10} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j5} = 2 \angle -90^\circ$$

$$\frac{\mathbf{V}_2}{j10} + \frac{\mathbf{V}_2 - \mathbf{V}_1}{-j5} = 1.5 \angle 0^\circ$$

$$(0.1 + j0.2)\mathbf{V}_1 - j0.2\mathbf{V}_2 = -j2$$
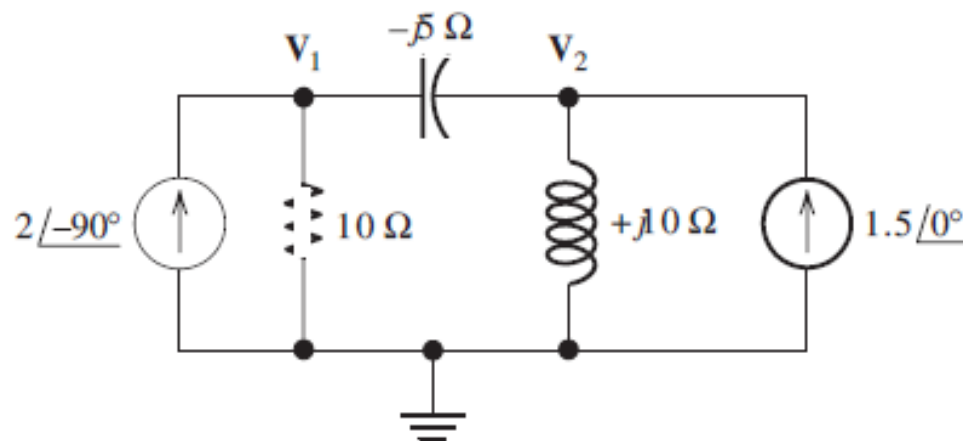
$$-j0.2\mathbf{V}_1 + j0.1\mathbf{V}_2 = 1.5$$




$$\Rightarrow \mathbf{V}_1 = 16.1 \angle 29.7^\circ$$

$$\Rightarrow v_1(t) = 16.1 \cos(100t + 29.7^\circ)$$

## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### □ Exercise

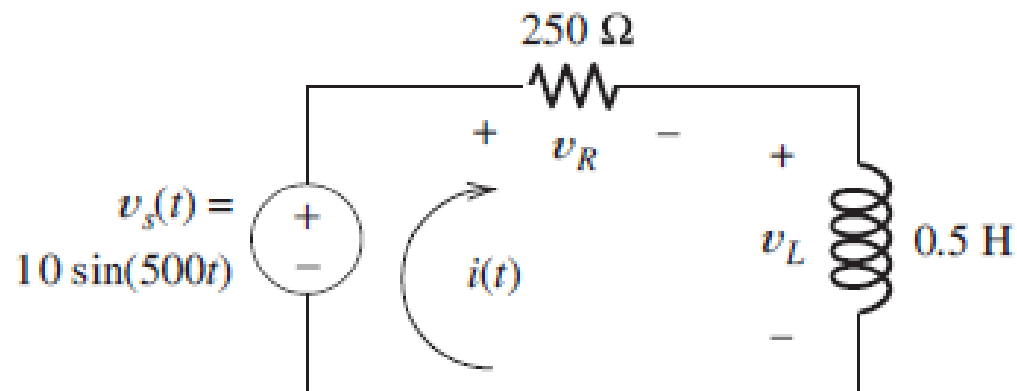


$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{10 \angle -90^\circ}{250 + j250} = 28.28 \angle -135^\circ \text{ mA}$$

$$\Rightarrow i(t) = 28.28 \cos(500t - 135^\circ) \text{ mA}$$


$$\Rightarrow \mathbf{V}_R = R\mathbf{I} = 7.07 \angle -135^\circ$$
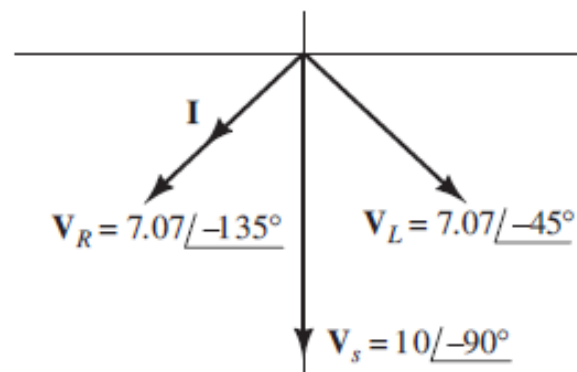
$$\Rightarrow \mathbf{V}_L = j\omega L\mathbf{I} = 7.07 \angle -45^\circ$$



## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### □ Exercise

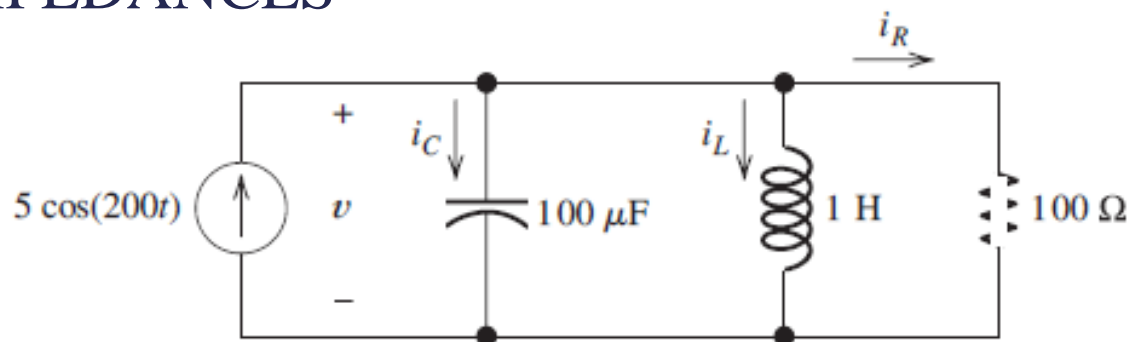

$$Z = \frac{1}{1/100 + 1/(-j50) + 1/(+j200)} = 55.47 \angle -56.31^\circ \Omega$$

$$\Rightarrow \mathbf{V} = \mathbf{Z}\mathbf{I} = 277.4 \angle -56.31^\circ \text{ V}$$


$$\Rightarrow \mathbf{I}_C = \mathbf{V}/(-j50) = 5.547 \angle 33.69^\circ \text{ A}$$

$$\Rightarrow \mathbf{I}_L = \mathbf{V}/(j200) = 1.387 \angle -146.31^\circ \text{ A}$$

$$\Rightarrow \mathbf{I}_R = \mathbf{V}/(100) = 2.774 \angle -56.31^\circ \text{ A}$$

## 5.4 CIRCUIT ANALYSIS WITH PHASORS AND COMPLEX IMPEDANCES

### □ Mesh-Current Analysis

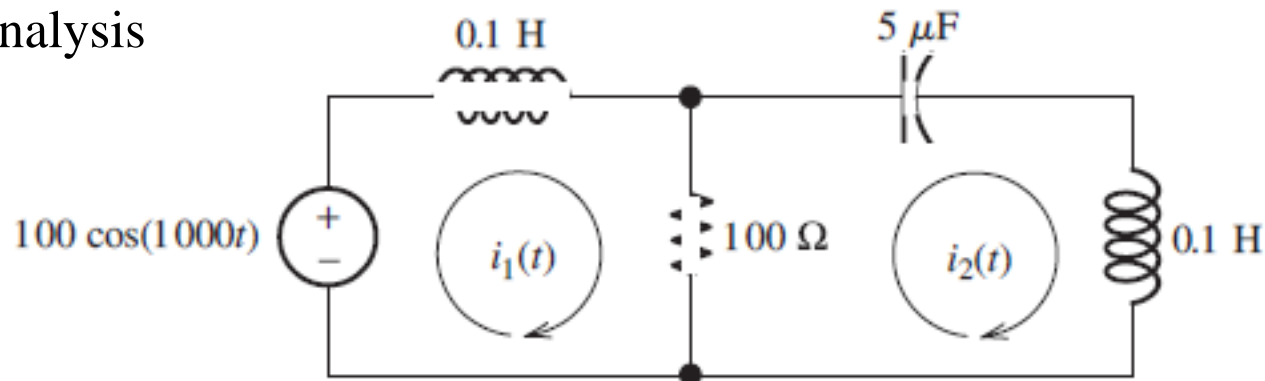

$$j100\mathbf{I}_1 + 100(\mathbf{I}_1 - \mathbf{I}_2) = 100$$

$$-j200\mathbf{I}_2 + j100\mathbf{I}_2 + 100(\mathbf{I}_2 - \mathbf{I}_1) = 0$$

$$\begin{aligned} \Rightarrow (100 + j100)\mathbf{I}_1 - 100\mathbf{I}_2 &= 100 \\ -100\mathbf{I}_1 + (100 - j100)\mathbf{I}_2 &= 0 \end{aligned}$$

$$\begin{aligned} \Rightarrow \mathbf{I}_1 &= 1.414 \angle -45^\circ \text{ A} \\ \mathbf{I}_2 &= 1 \angle 0^\circ \text{ A} \end{aligned}$$


## 5.5 POWER IN AC CIRCUITS

- Power delivered to a general load

$$v(t) = V_m \cos(\omega t)$$

$$\Rightarrow \mathbf{V} = V_m \angle 0^\circ$$

$$Z = |Z| \angle \theta = R + jX$$

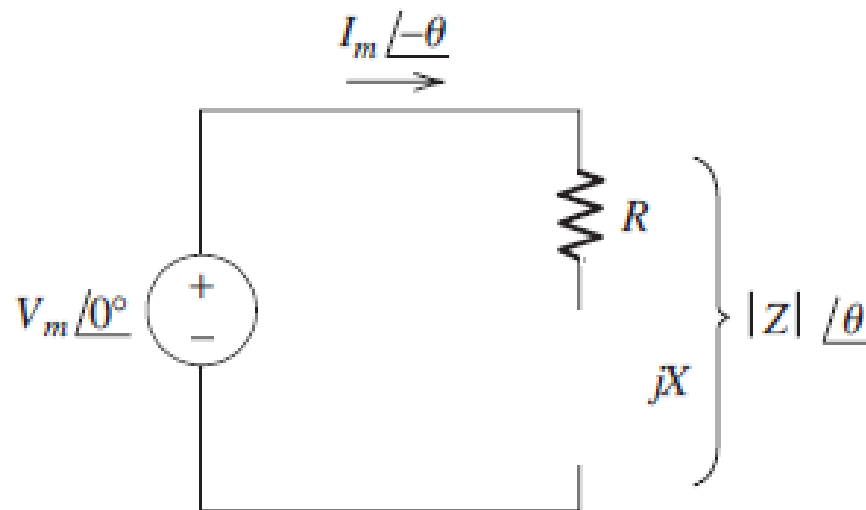

$$\Rightarrow \mathbf{I} = \frac{\mathbf{V}}{Z} = \frac{V_m \angle 0^\circ}{|Z| \angle \theta} = I_m \angle -\theta$$

$$I_m = \frac{V_m}{|Z|}$$


## 5.5 POWER IN AC CIRCUITS

### □ Current, Voltage, and Power for a Resistive Load

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t)$$
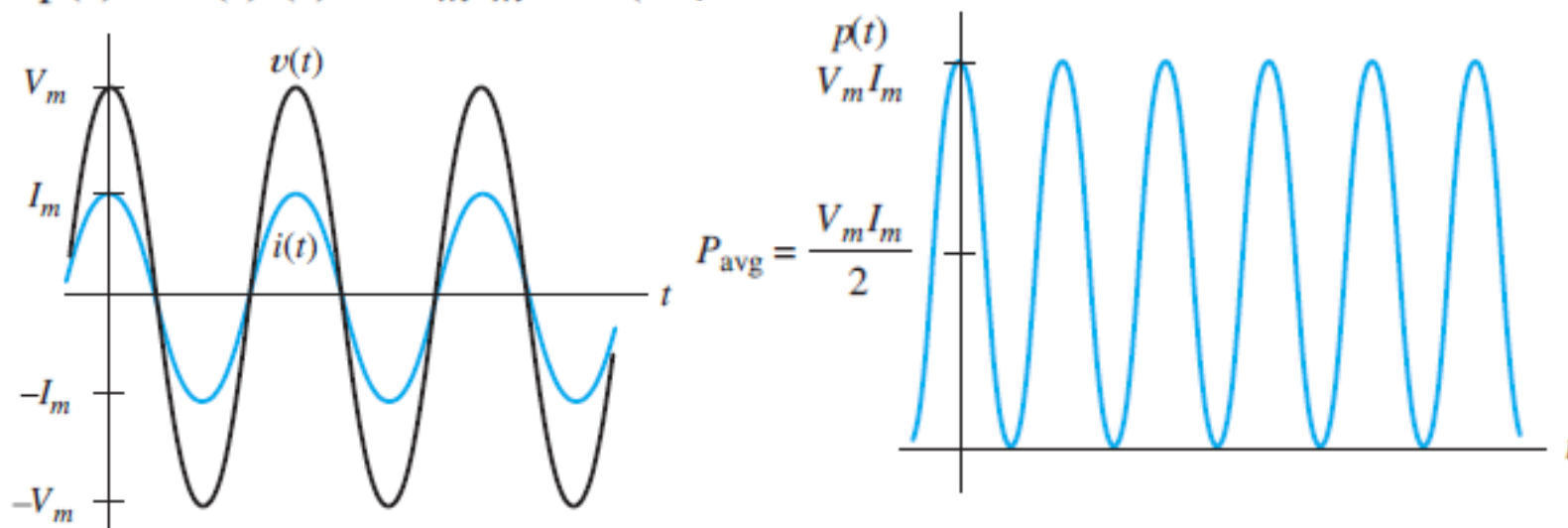
$$p(t) = v(t)i(t) = V_m I_m \cos^2(\omega t)$$







## 5.5 POWER IN AC CIRCUITS

- Current, Voltage, and Power for a Inductive Load  $Z = \omega L \angle 90^\circ$

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - 90^\circ) = I_m \sin(\omega t)$$
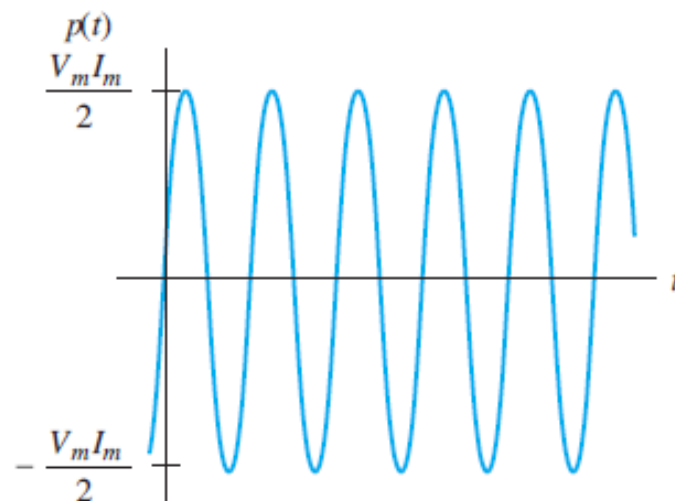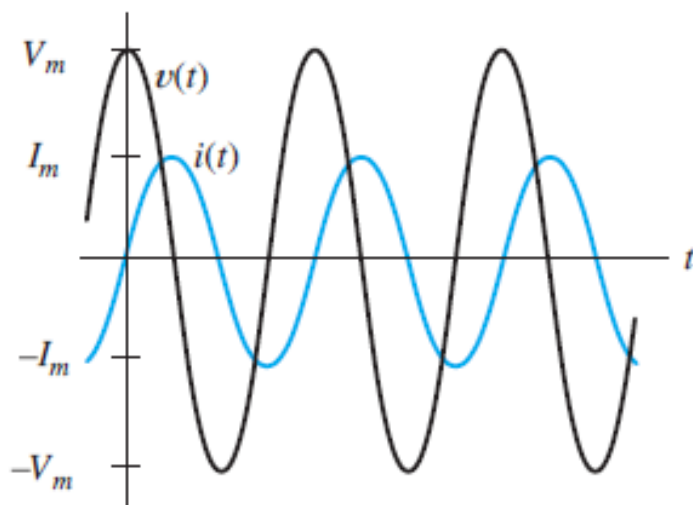
$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t) \sin(\omega t) = \frac{V_m I_m}{2} \sin(2\omega t)$$



Reactive Power



## 5.5 POWER IN AC CIRCUITS

- Current, Voltage, and Power for a Capacitive Load  $Z = (1/\omega C) \angle -90^\circ$

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t + 90^\circ) = -I_m \sin(\omega t)$$
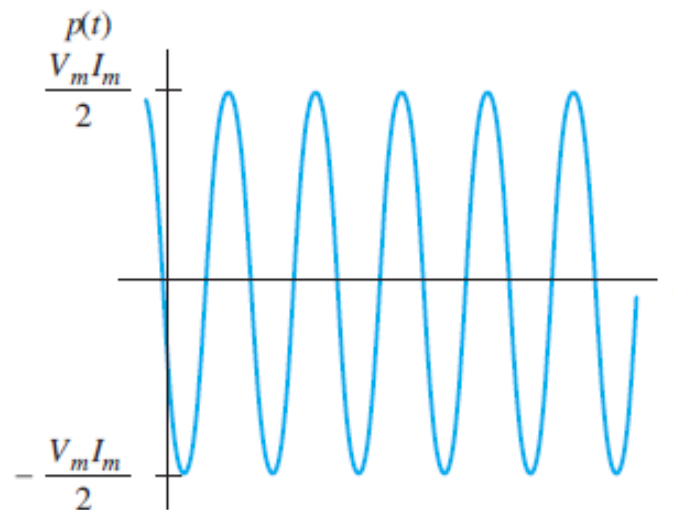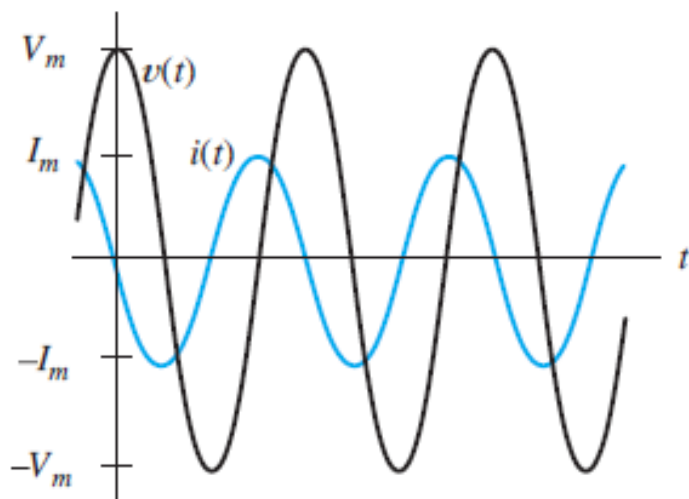
$$p(t) = v(t)i(t) = -V_m I_m \cos(\omega t) \sin(\omega t) = -\frac{V_m I_m}{2} \sin(2\omega t)$$



Reactive Power

## 5.5 POWER IN AC CIRCUITS

### □ Power Calculations for a General RLC Load

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - \theta)$$

$$p(t) = V_m I_m \cos(\omega t) \cos(\omega t - \theta)$$

$$\cos(\omega t - \theta) = \cos(\theta) \cos(\omega t) + \sin(\theta) \sin(\omega t)$$

$$\Rightarrow p(t) = V_m I_m \cos(\theta) \cos^2(\omega t) + V_m I_m \sin(\theta) \cos(\omega t) \sin(\omega t)$$



## 5.5 POWER IN AC CIRCUITS

### □ Power Calculations for a General RLC Load

$$\cos^2(\omega t) = \frac{1}{2} + \frac{1}{2} \cos(2\omega t)$$

$$\cos(\omega t) \sin(\omega t) = \frac{1}{2} \sin(2\omega t)$$

$$\Rightarrow p(t) = \frac{V_m I_m}{2} \cos(\theta) [1 + \cos(2\omega t)] + \frac{V_m I_m}{2} \sin(\theta) \sin(2\omega t)$$

average power  $P \Rightarrow P = \frac{V_m I_m}{2} \cos(\theta)$

$$\Rightarrow P = V_{\text{rms}} I_{\text{rms}} \cos(\theta)$$

**Power Factor**



## 5.5 POWER IN AC CIRCUITS

### □ Power Factor

$$\text{PF} = \cos(\theta)$$

phase of the voltage  $\theta_v$  minus the phase of the current  $\theta_i$ ,

$$\theta = \theta_v - \theta_i$$

$\theta$  is called the **power angle**



## 5.5 POWER IN AC CIRCUITS

### □ Reactive Power

$$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta)$$

✓ units are usually given as Volt Amperes Reactive (VARs)


### □ Apparent Power

$$\text{apparent power} = V_{\text{rms}} I_{\text{rms}}$$

✓ units are volt-amperes (VA)

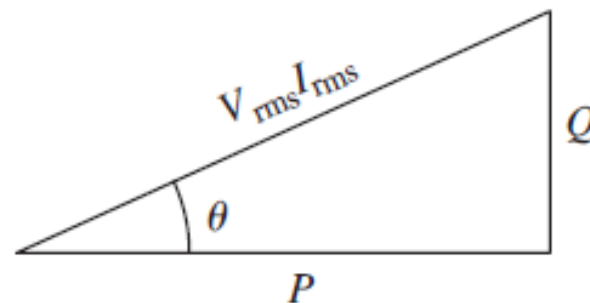
### □ Power Triangle

$$\Rightarrow P^2 + Q^2 = (V_{\text{rms}} I_{\text{rms}})^2$$



## 5.5 POWER IN AC CIRCUITS

## Example 5.7 AC Power Calculations

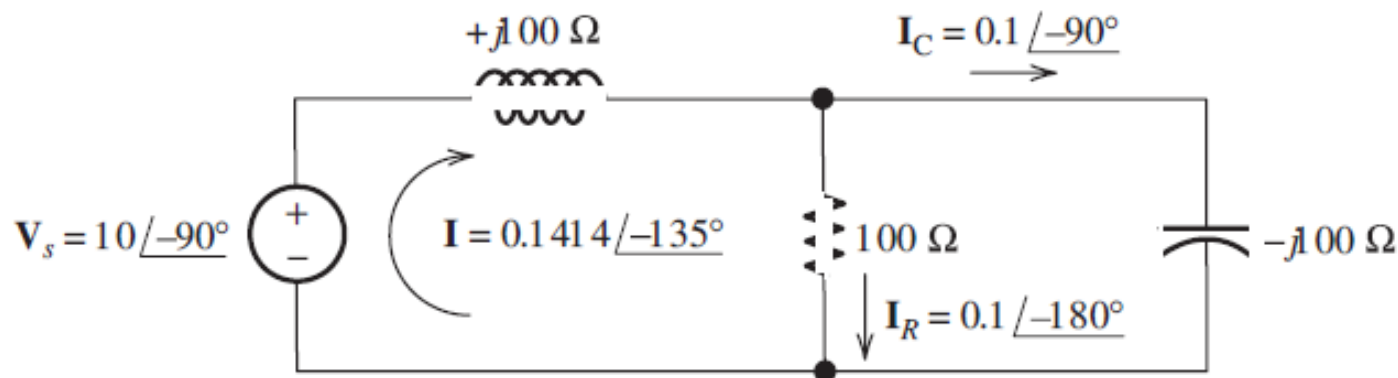

$$\theta = -90^\circ - (-135^\circ) = 45^\circ$$

$$\Rightarrow P = V_{\text{srms}} I_{\text{rms}} \cos(\theta)$$

$$V_{\text{srms}} = \frac{|\mathbf{V}_s|}{\sqrt{2}} = \frac{10}{\sqrt{2}} = 7.071 \text{ V}$$

$$= 7.071 \times 0.1 \cos(45^\circ) = 0.5 \text{ W}$$

$$I_{\text{rms}} = \frac{|\mathbf{I}|}{\sqrt{2}} = \frac{0.1414}{\sqrt{2}} = 0.1 \text{ A}$$

$$\Rightarrow Q = V_{\text{srms}} I_{\text{rms}} \sin(\theta)$$

$$= 7.071 \times 0.1 \sin(45^\circ) = 0.5 \text{ VAR}$$





## 5.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

- Valid for only steady-state operation
- Same as before (with Complex Impedance)

$$\mathbf{V}_t = \mathbf{V}_{oc}$$

$$\mathbf{I}_n = \mathbf{I}_{sc}$$

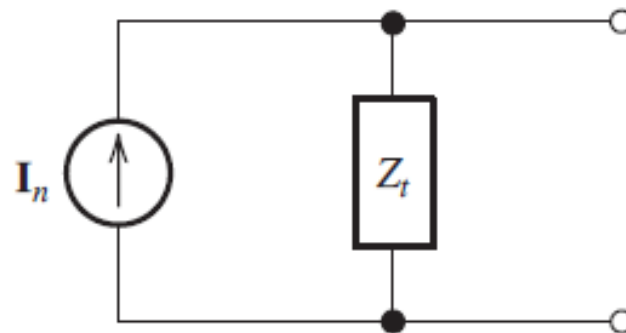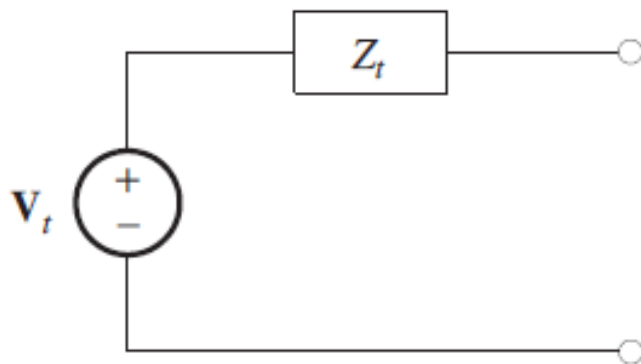
$$\mathbf{Z}_t = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}} = \frac{\mathbf{V}_t}{\mathbf{I}_n}$$






## 5.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
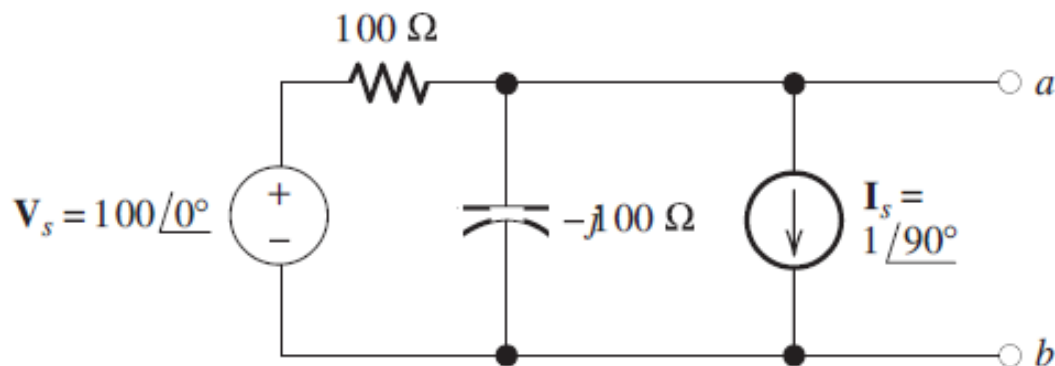
## Example 5.10 Thévenin and Norton Equivalents




$$Z_t = \frac{1}{1/100 + 1/(-j100)} = \frac{1}{0.01 + j0.01}$$
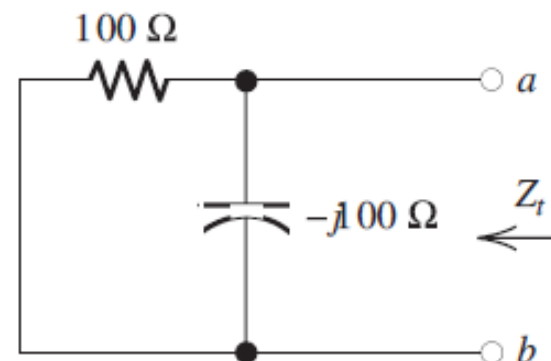
$$= \frac{1}{0.01414 \angle 45^\circ} = 70.71 \angle -45^\circ = 50 - j50 \Omega$$



## 5.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
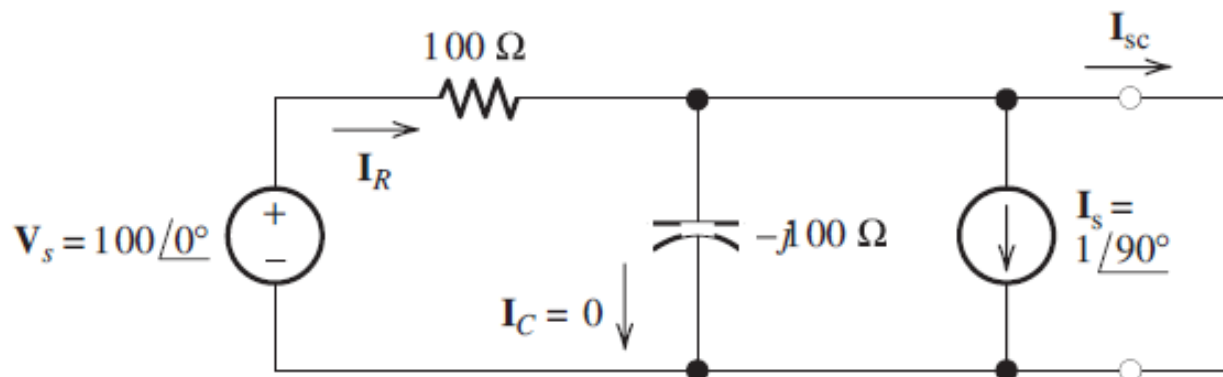
### Example 5.10 Thévenin and Norton Equivalents



$$\mathbf{I}_R = \frac{\mathbf{V}_s}{100} = \frac{100}{100} = 1 \angle 0^\circ \text{ A}$$


$$\Rightarrow \mathbf{I}_{sc} = \mathbf{I}_R - \mathbf{I}_s = 1 - 1 \angle 90^\circ = 1 - j = 1.414 \angle -45^\circ \text{ A}$$

$$\Rightarrow \mathbf{V}_t = \mathbf{I}_{sc} Z_t = 1.414 \angle -45^\circ \times 70.71 \angle -45^\circ = 100 \angle -90^\circ \text{ V}$$





## 5.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
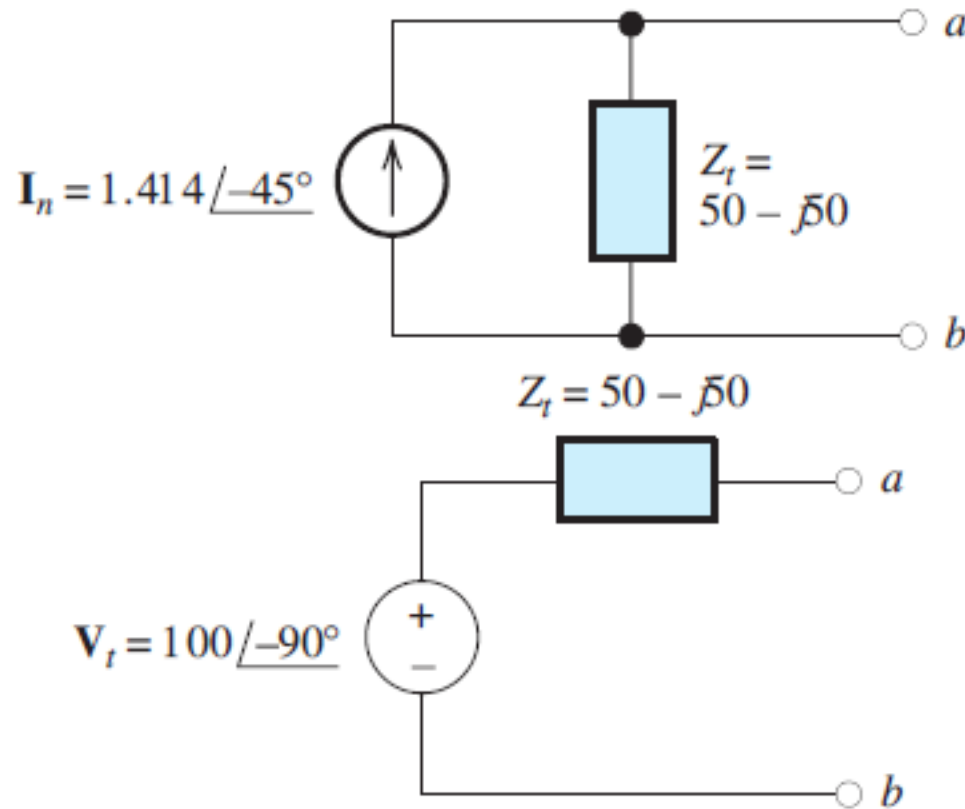
## Example 5.10 Thévenin and Norton Equivalents


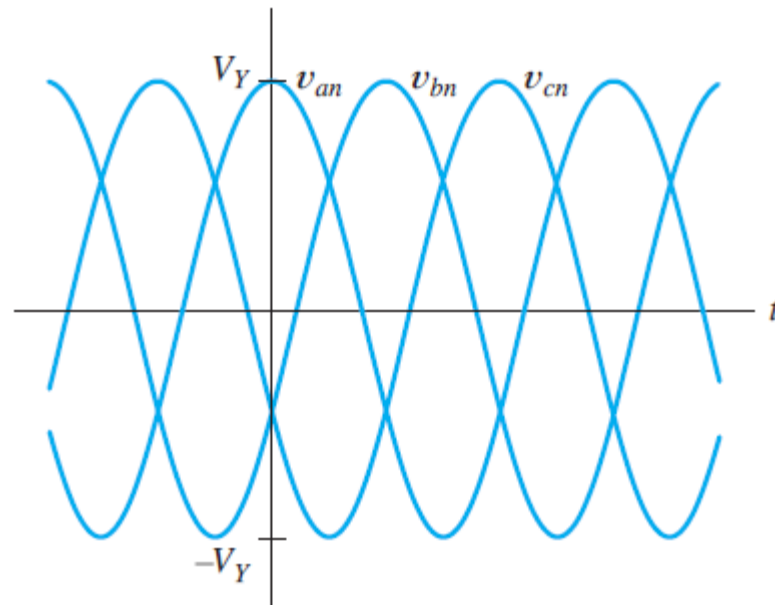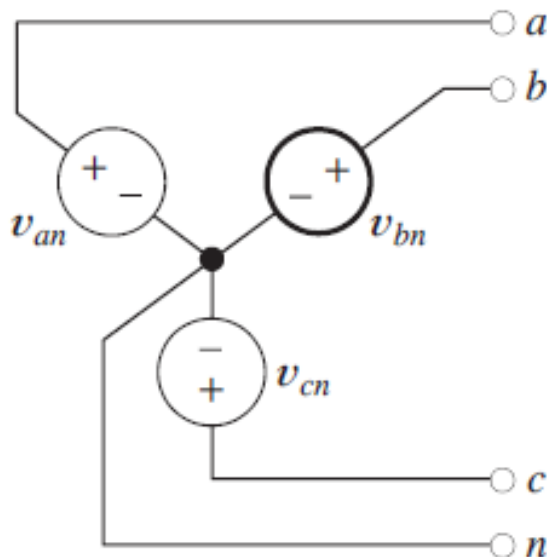
## 5.7 BALANCED THREE-PHASE CIRCUITS

- Balanced three-phase source
  - ❖ three equal-amplitude ac voltages having phases that are 120 degrees apart
  - ❖ wye connected (Y connected)



$$v_{an}(t) = V_Y \cos(\omega t)$$

$$v_{bn}(t) = V_Y \cos(\omega t - 120^\circ)$$

$$v_{cn}(t) = V_Y \cos(\omega t + 120^\circ)$$


## 5.7 BALANCED THREE-PHASE CIRCUITS

## □ Phasor Notation

$$\mathbf{V}_{an} = V_Y \angle 0^\circ$$


$$\mathbf{V}_{bn} = V_Y \angle -120^\circ$$
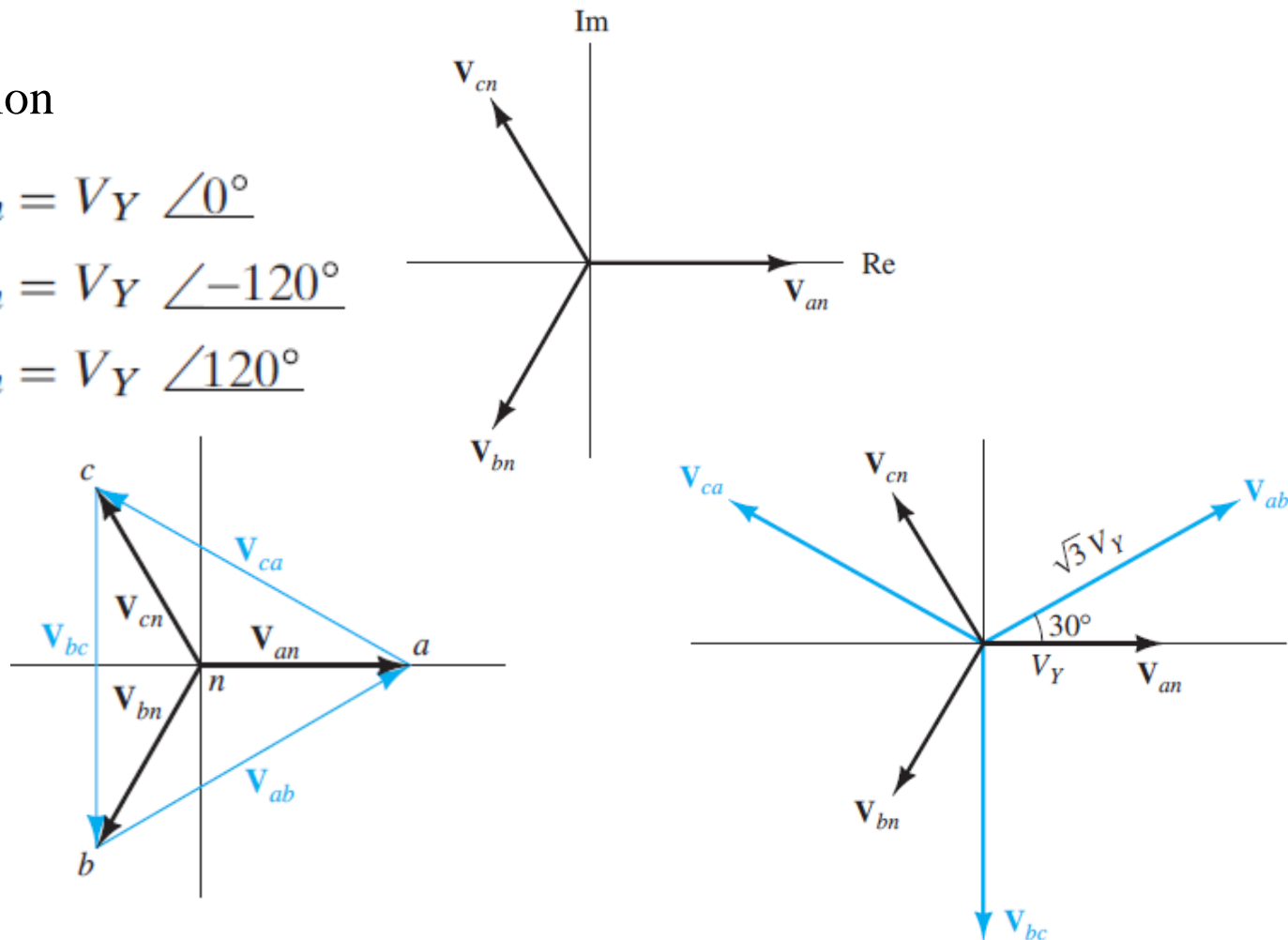
$$\mathbf{V}_{cn} = V_Y \angle 120^\circ$$



## 5.7 BALANCED THREE-PHASE CIRCUITS


### □ Wye-Wye Connection

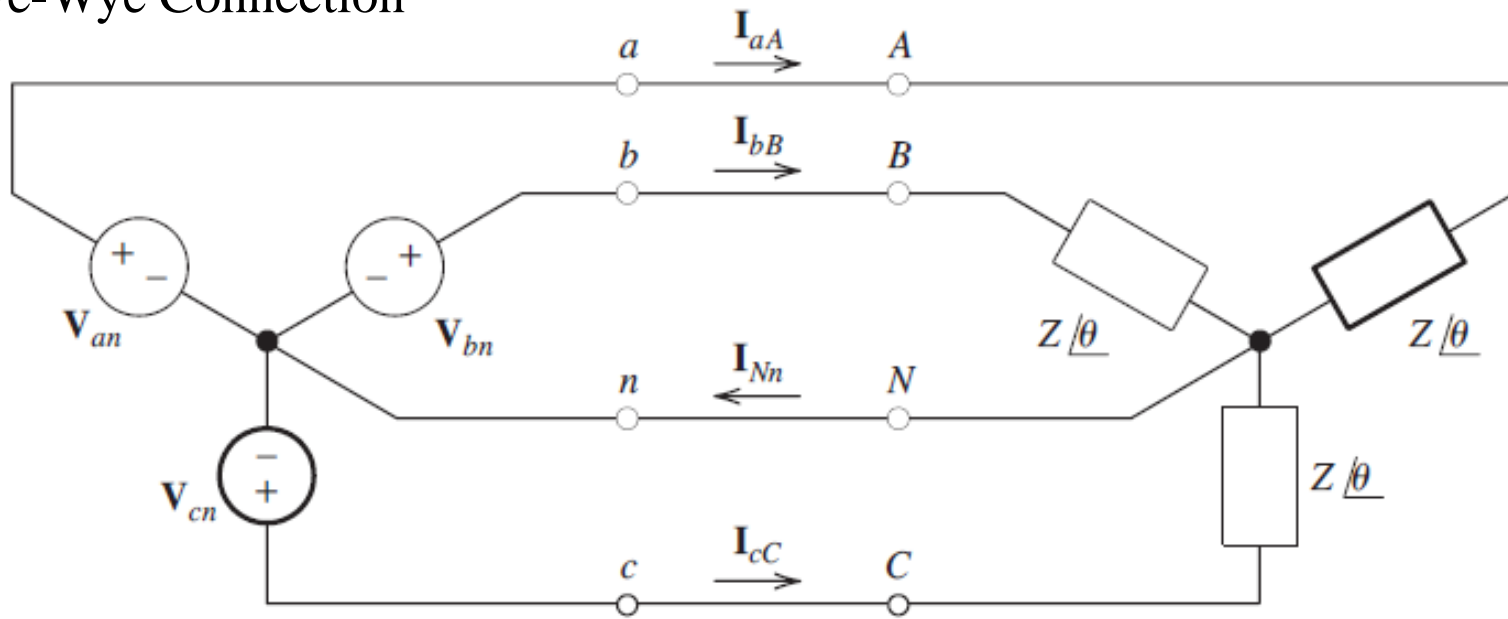

$$\mathbf{I}_{aA} = \frac{\mathbf{V}_{an}}{Z \angle \theta} = \frac{V_Y \angle 0^\circ}{Z \angle \theta} = I_L \angle -\theta$$

## 5.7 BALANCED THREE-PHASE CIRCUITS

### □ Delta-Delta Connection

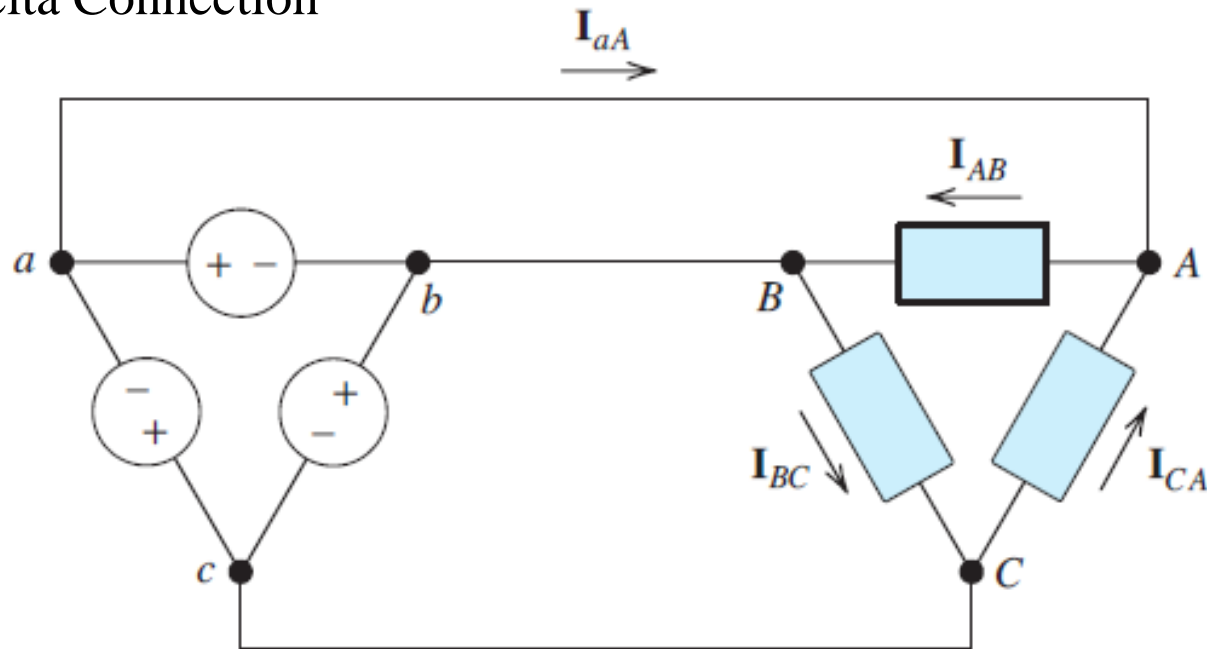

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{Z_{\Delta} \angle \theta} = \frac{\mathbf{V}_{ab}}{Z_{\Delta} \angle \theta} = \frac{V_L \angle 30^\circ}{Z_{\Delta} \angle \theta} = \frac{V_L}{Z_{\Delta}} \angle 30^\circ - \theta$$

## EXERCISES

- P5.6
- P5.12
- P5.13
- P5.23
- P5.24
- P5.25
- P5.35
- P5.37
- P5.44
- P5.46
- P5.49
- P5.52
- P5.67
- P5.78
- P5.87
- P5.91
- P5.95
- P5.96
- P5.99
- T5.1
- T5.2
- T5.3
- T5.4
- T5.5
- T5.6

