



دانشگاه سمنان

Semnan University
Faculty of Mechanical Engineering

دانشکده مهندسی مکانیک



دانشکده مهندسی مکانیک

درس مبانی برق ۱


نیمسال اول ۹۸-۹۹

ELECTRICAL ENGINEERING

PRINCIPLES AND APPLICATIONS

Allan R. Hambley

5th Edition

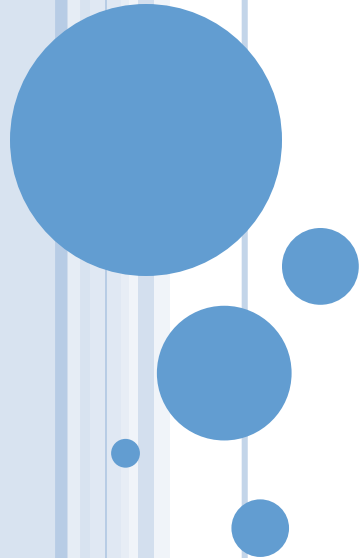

□ CONTENTS:

- ❖ Chapter 1: Introduction
- ❖ Chapter 2: Resistive Circuits
- ❖ Chapter 3: Inductance and Capacitance
- ❖ Chapter 4: **Transients**
- ❖ Chapter 5: Steady-State Sinusoidal Analysis



INTRODUCTION

- ❑ Transient and steady-state response concepts
- ❑ Solve first-order RC or RL circuits
- ❑ First-order circuits time constant.
- ❑ Solve RLC circuits in dc steady-state conditions
- ❑ Solve second-order circuits
- ❑ Second-order system natural frequency and damping ratio



4.1 FIRST-ORDER RC CIRCUITS

□ Discharge of a Capacitance through a Resistance


❖ Current equation at the top node:

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t)}{R} = 0$$

$$\Rightarrow RC \frac{dv_C(t)}{dt} + v_C(t) = 0$$

$$v_C(t) = Ke^{st}$$

$$\Rightarrow RCKse^{st} + Ke^{st} = 0$$

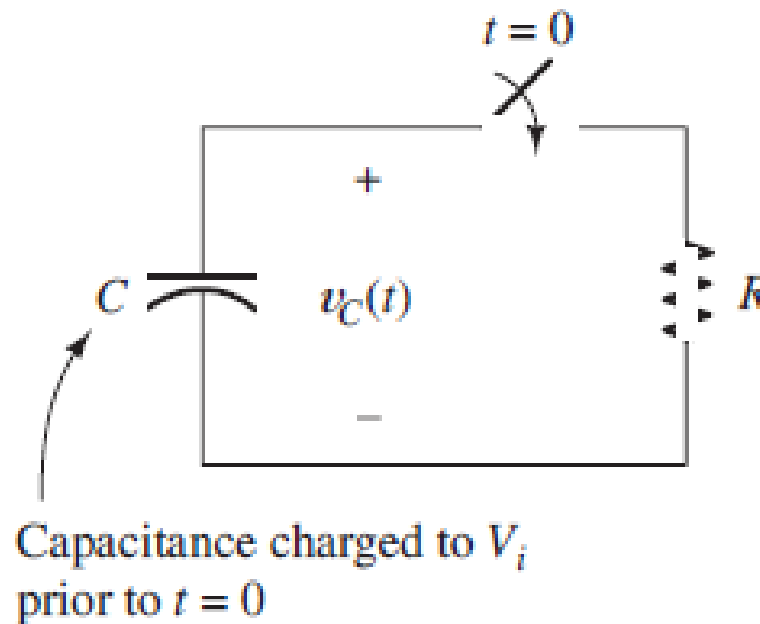

4.1 FIRST-ORDER RC CIRCUITS

□ Discharge of a Capacitance through a Resistance

$$RCsKe^{st} + Ke^{st} = 0 \quad \Rightarrow \quad K(RCs+1).e^{st} = 0$$

❖ Solve for “s”:


$$s = \frac{-1}{RC} \quad \Rightarrow \quad v_C(t) = Ke^{-t/RC}$$

❖ Initial condition for “K”:

$$v_C(0+) = V_i$$

$$\Rightarrow v_C(0+) = V_i = Ke^0 = K$$

$$\Rightarrow v_C(t) = V_i e^{-t/RC}$$

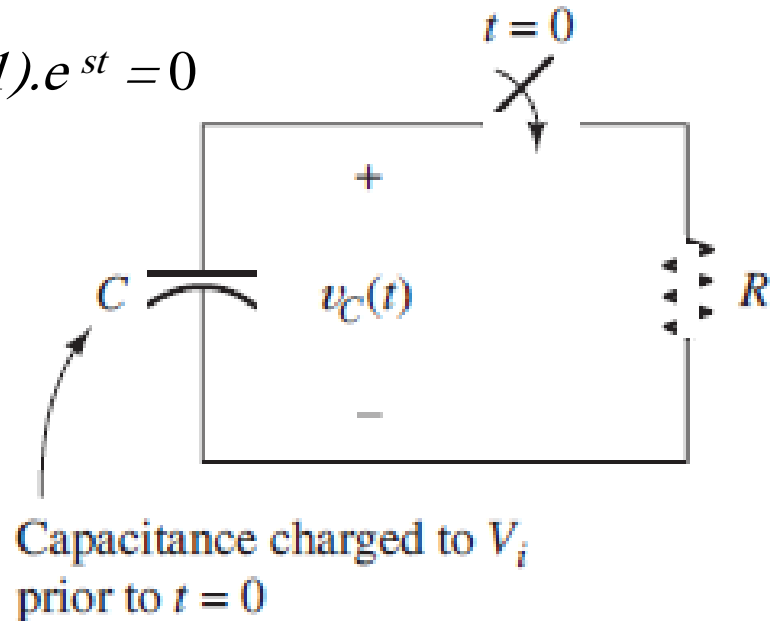


4.1 FIRST-ORDER RC CIRCUITS

□ Time constant

$$v_C(t) = V_i e^{-t/RC}$$

$$\tau = RC$$

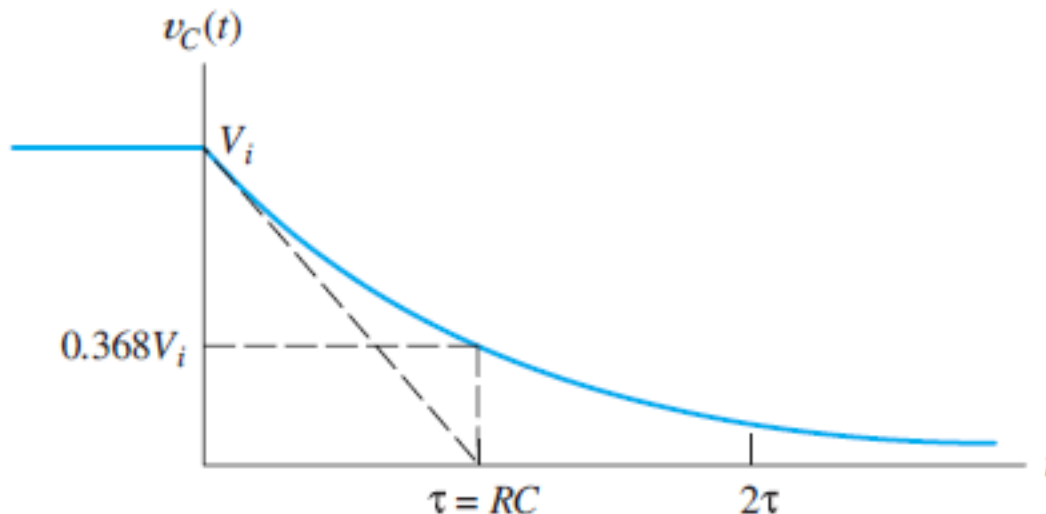

- ❖ Voltage decays to 36.8%
- ❖ Applying RC circuits in timing applications

4.1 FIRST-ORDER RC CIRCUITS

- Charging a Capacitance from a DC Source through a Resistance

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t) - V_s}{R} = 0$$


$$\Rightarrow RC \frac{dv_C(t)}{dt} + v_C(t) = V_s$$

$$v_C(0+) = v_C(0-) = 0$$

$$v_C(t) = K_1 + K_2 e^{st}$$

$$(1 + RCs)K_2 e^{st} + K_1 = V_s$$
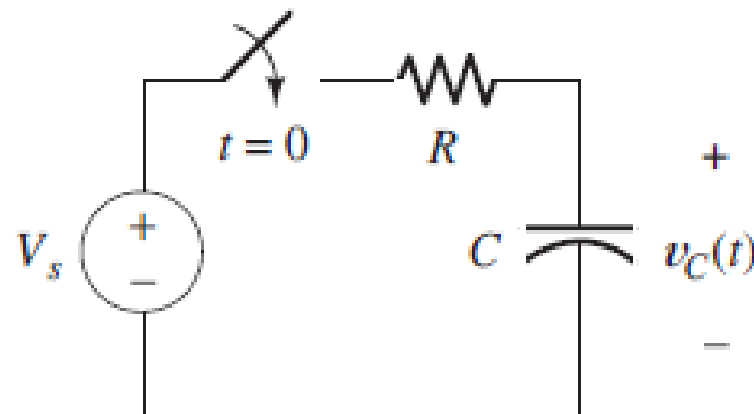
$$\Rightarrow K_1 = V_s \quad s = \frac{-1}{RC} \quad \Rightarrow v_C(t) = V_s + K_2 e^{-t/RC}$$



4.1 FIRST-ORDER RC CIRCUITS


- Charging a Capacitance from a DC Source through a Resistance

$$v_C(0+) = 0 = V_s + K_2 e^0 = V_s + K_2$$

$$\Rightarrow K_2 = -V_s$$

$$\Rightarrow v_C(t) = V_s - V_s e^{-t/RC}$$
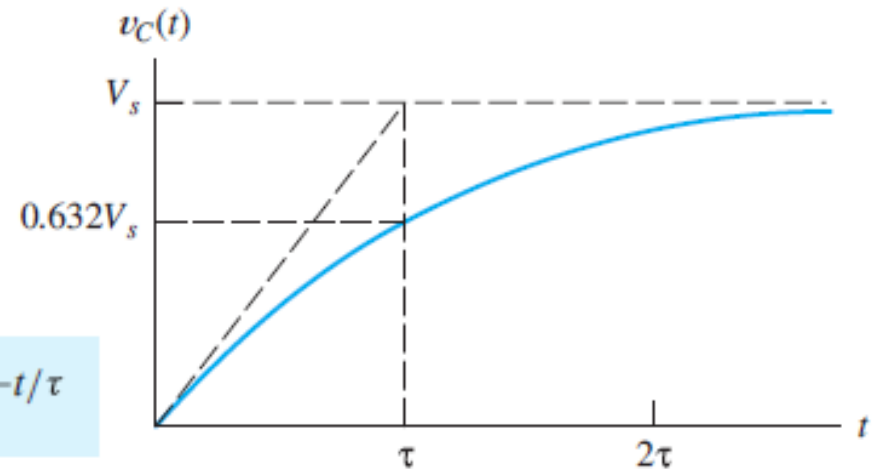
$$\tau = RC \Rightarrow v_C(t) = V_s - V_s e^{-t/\tau}$$



- Steady-state (forced) and Transient response

4.2 DC STEADY STATE

□ Constant dc sources:

❖ Capacitance:

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

- ✓ For steady-state conditions with dc sources, **capacitances** behave as **open circuits**

❖ Inductance:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

- ✓ For steady-state conditions with dc sources, **inductances** behave as **short circuits**


□ Determining the forced (steady-state) response for *RLC* circuits with dc sources:

- ❖ 1. Replace capacitances with open circuits.
- ❖ 2. Replace inductances with short circuits.
- ❖ 3. Solve the remaining circuit.



4.2 DC STEADY STATE

Example 4.1 Steady-State DC Analysis

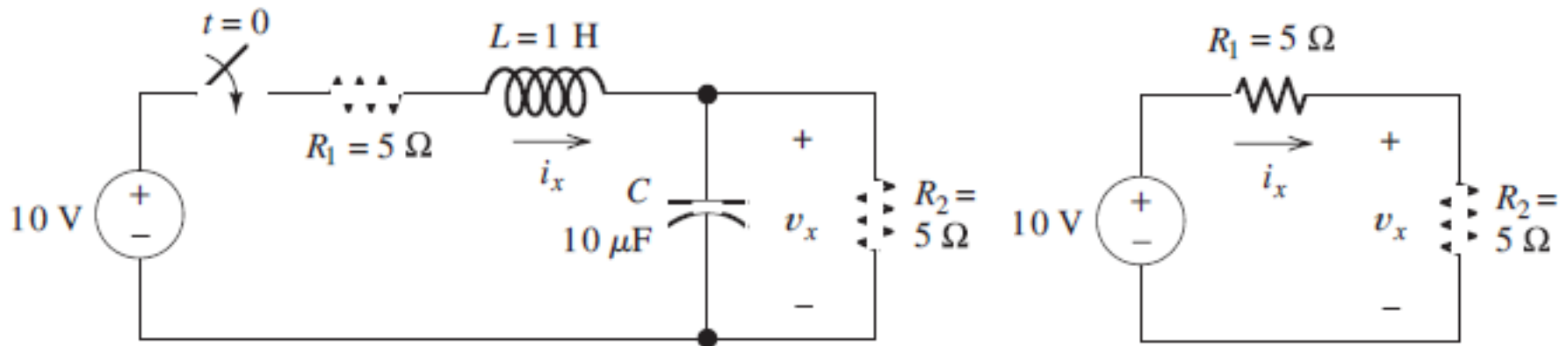


$$i_x = \frac{10}{R_1 + R_2} = 1 \text{ A}$$


$$v_x = R_2 i_x = 5 \text{ V}$$

4.2 DC STEADY STATE

□ Exercise

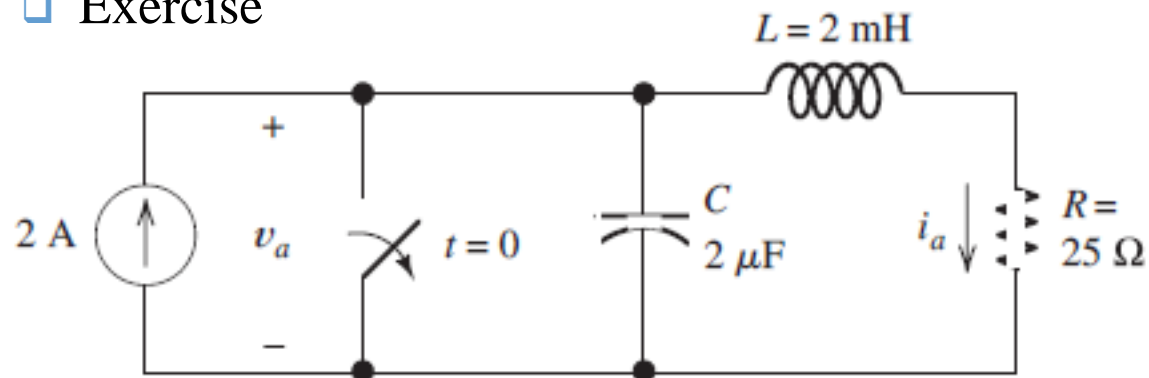
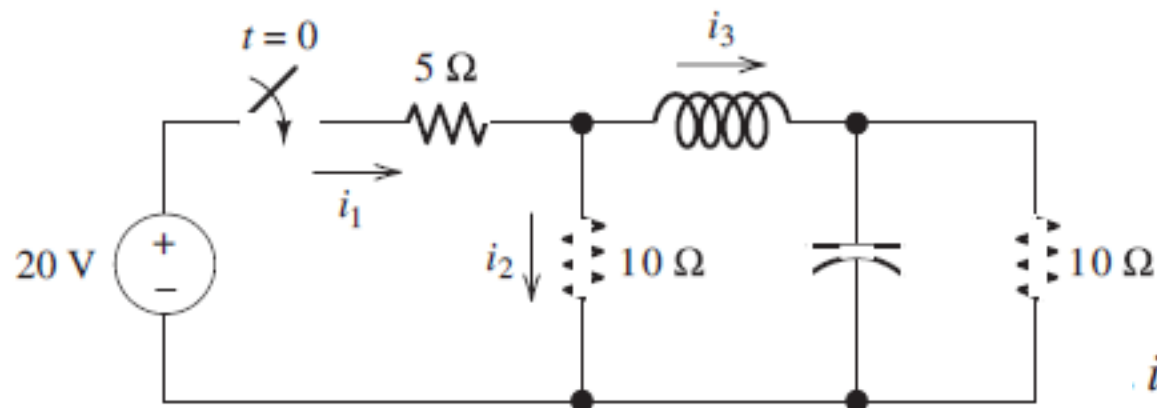
$$v_a = 50 \text{ V}, i_a = 2 \text{ A};$$



$$i_1 = 2 \text{ A}, i_2 = 1 \text{ A}, i_3 = 1 \text{ A}.$$

4.3 RL CIRCUITS


Example 4.2 RL Transient Analysis

□ For current: $i(t) = 0$ for $t < 0$

❖ KVL equation:

$$Ri(t) + L \frac{di}{dt} = V_s$$

$$i(t) = K_1 + K_2 e^{st}$$

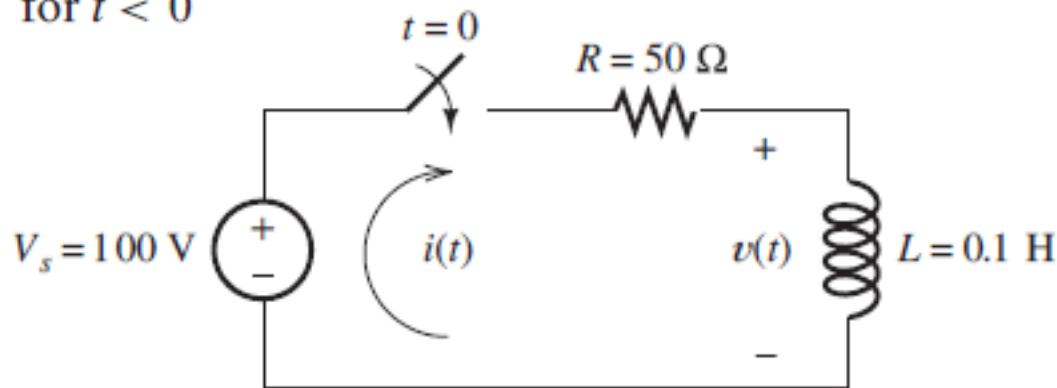

$$\Rightarrow RK_1 + (RK_2 + sLK_2)e^{st} = V_s$$

$$\Rightarrow K_1 = \frac{V_s}{R} = 2$$

$$\Rightarrow s = \frac{-R}{L}$$

$$\Rightarrow i(t) = 2 + K_2 e^{-tR/L}$$

4.3 RL CIRCUITS


Example 4.2 RL Transient Analysis

$$i(t) = 2 + K_2 e^{-tR/L}$$

$$i(0+) = 0 = 2 + K_2 e^0 = 2 + K_2 \quad \Rightarrow \quad K_2 = -2.$$

$$\Rightarrow i(t) = 2 - 2e^{-t/\tau} \quad \text{for } t > 0$$

$$\tau = \frac{L}{R}$$

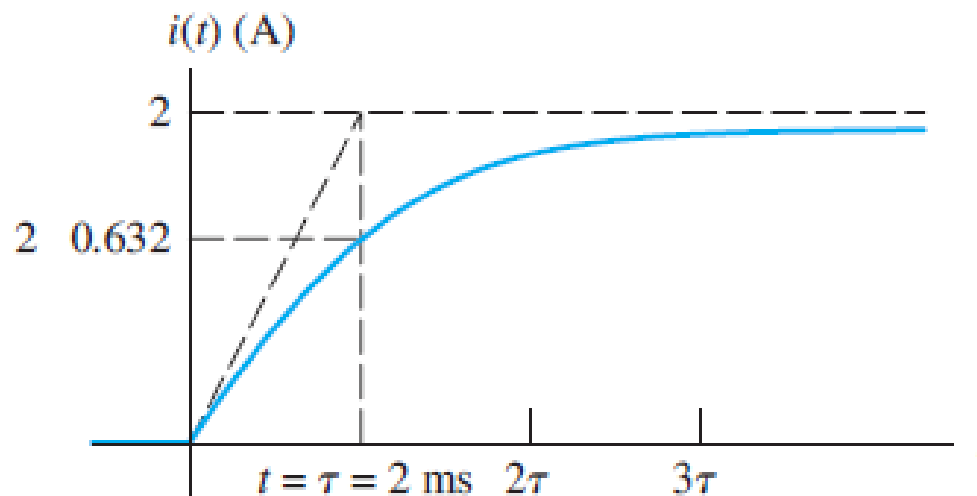

4.3 RL CIRCUITS

Example 4.2 *RL Transient Analysis*



□ For voltage:

$$v(t) = 0 \quad \text{for } t < 0$$

$$V_s = 100 \text{ V}$$

$$v(t) = 100 - 50i(t) \quad \text{for } t > 0$$

$$\Rightarrow v(t) = 100e^{-t/\tau}$$

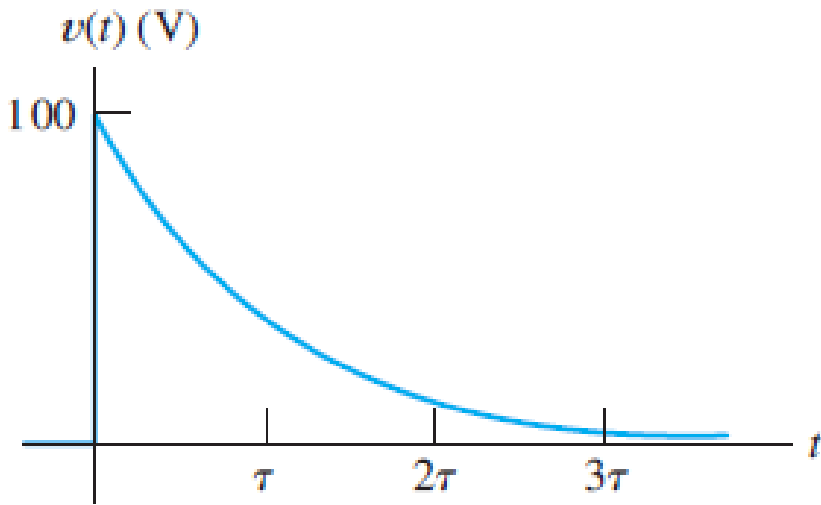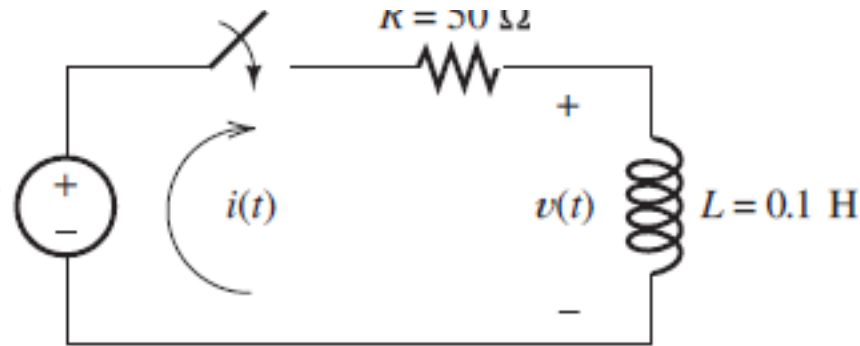

4.3 RL CIRCUITS

Example 4.3 *RL Transient Analysis*


- Prior to $t = 0$:
 - ❖ the inductor behaves as a short circuit

$$v(t) = 0 \quad \text{for } t < 0$$

$$i(t) = \frac{V_s}{R_1} \quad \text{for } t < 0$$

$$i(t) = Ke^{-t/\tau} \quad \text{for } t > 0 \quad \tau = \frac{L}{R_2}$$
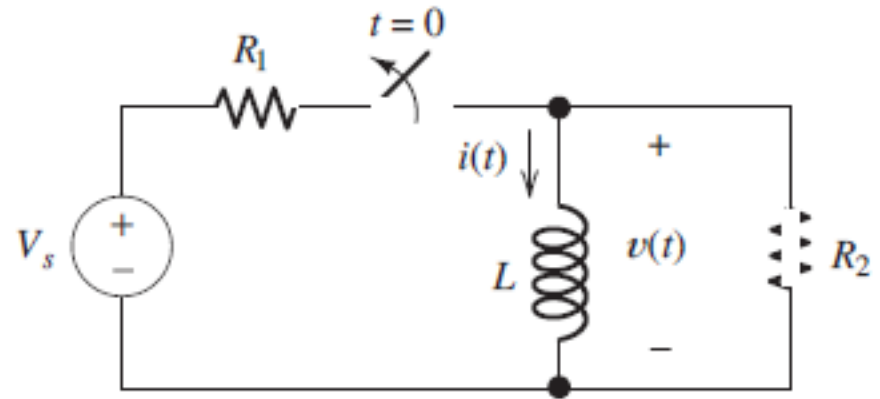
$$i(0+) = \frac{V_s}{R_1} = Ke^{-0} = K$$




4.3 RL CIRCUITS

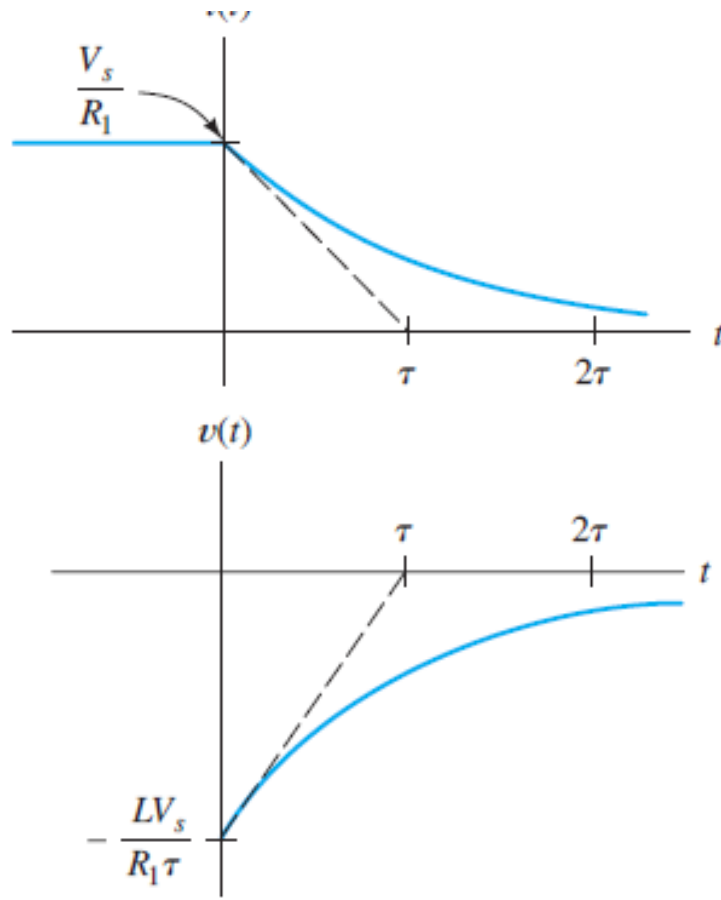Example 4.3 RL Transient Analysis

$$i(t) = \frac{V_s}{R_1} e^{-t/\tau} \quad \text{for } t > 0$$

$$\begin{aligned} v(t) &= L \frac{di(t)}{dt} \\ &= 0 \quad \text{for } t < 0 \\ &= -\frac{LV_s}{R_1 \tau} e^{-t/\tau} \quad \text{for } t > 0 \end{aligned}$$



4.3 RL CIRCUITS

□ Exercise

$$\frac{v(t)}{R} + \frac{1}{L} \int_0^t v(x) dx + 0 = 2$$


$$\Rightarrow \frac{dv(t)}{dt} + \frac{R}{L} v(t) = 0$$

$$\Rightarrow v(t) = K \exp(-t / \tau)$$

$$\tau = L / R = 0.2 \text{ s}$$

$$v(0+) = 20 = K \Rightarrow v(t) = 20 \exp(-t / \tau) \quad i_R = v / R = 2 \exp(-t / \tau)$$
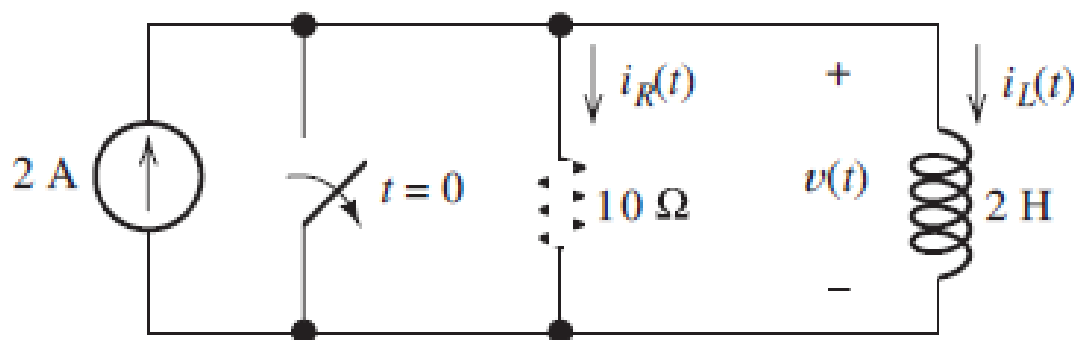
$$\Rightarrow i_L(t) = \frac{1}{L} \int_0^t v(x) dx = \frac{1}{2} [-20\tau \exp(-x / \tau)]_0^t = 2 - 2 \exp(-t / \tau)$$



4.3 RL CIRCUITS

□ Exercise

$$i(0^-) = 1 \text{ A} \Rightarrow i(0^+) = 1 \text{ A}$$

$$\frac{di(t)}{dt} + 200i(t) = 100 \quad 100 \text{ V}$$


$$\Rightarrow i(t) = K_1 + K_2 \exp(-t/\tau)$$

$$\tau = 1/200 = 5 \text{ ms}$$

$$i(\infty) = K_1 = 100/200 = 0.5 \text{ A.}$$


$$i(0^+) = 1 = K_1 + K_2 \Rightarrow K_2 = 0.5 \Rightarrow i(t) = 1.0 \text{ A for } t < 0$$
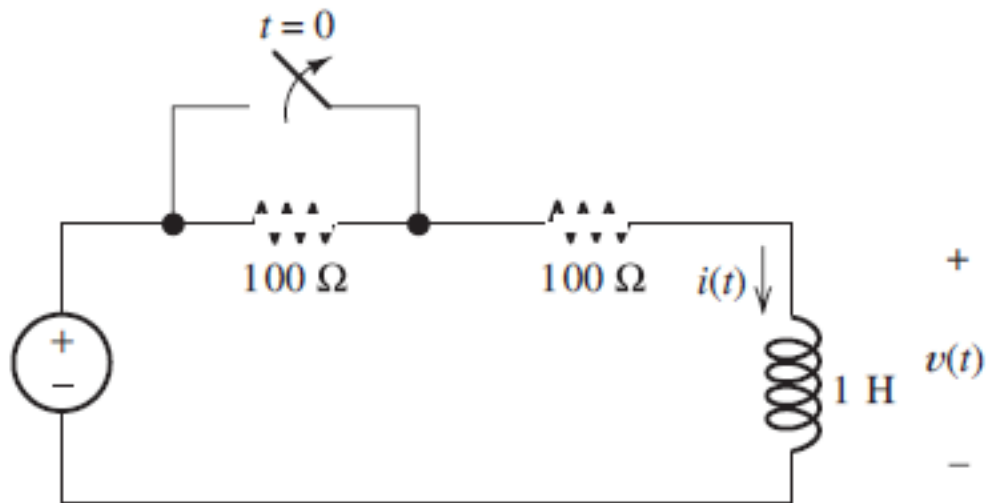
$$= 0.5 + 0.5 \exp(-t/\tau) \text{ for } t > 0$$



4.3 RL CIRCUITS

□ Exercise

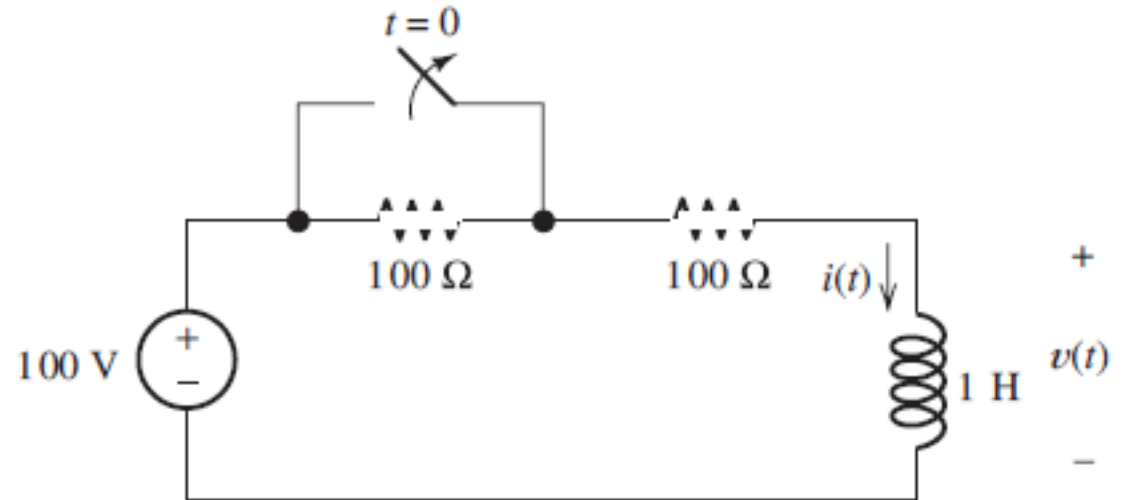

$$i(t) = 1.0 \text{ A for } t < 0$$

$$= 0.5 + 0.5 \exp(-t / \tau) \text{ for } t > 0$$

$$\Rightarrow v(t) = L \frac{di(t)}{dt}$$

$$= 0 \text{ V for } t < 0$$

$$= -100 \exp(-t / \tau) \text{ for } t > 0.$$

4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

□ Circuits that contain one energy-storage element

✓ (either an inductance or a capacitance)



❖ KVL:

$$L \frac{di(t)}{dt} + Ri(t) = v_t(t)$$

$$\Rightarrow \frac{L}{R} \frac{di(t)}{dt} + i(t) = \frac{v_t(t)}{R}$$

$$\Rightarrow \tau \frac{dx(t)}{dt} + x(t) = f(t)$$

forcing function.

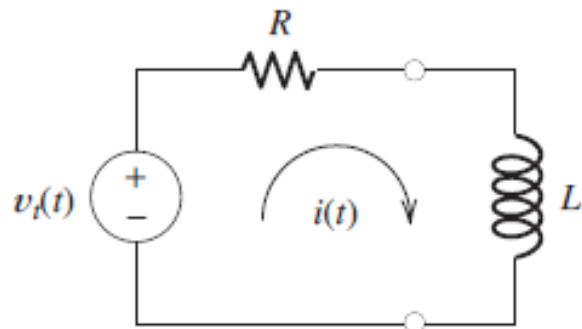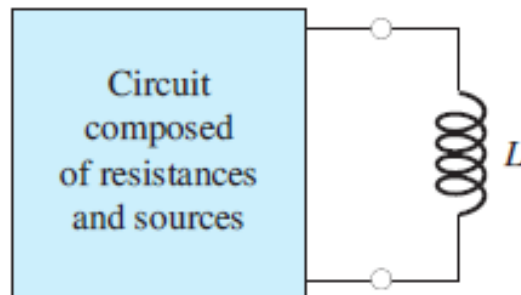

✓ Linear first-order differential equation

4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

□ Solution of the Differential Equation

$$\tau \frac{dx(t)}{dt} + x(t) = f(t)$$

❖ General solution: $X(t) = X_c(t) + X_p(t)$

✓ **Complementary solution** $X_c(t)$ (homogeneous equation, natural response)

$$\tau \frac{dx_c(t)}{dt} + x_c(t) = 0$$

✓ **Particular solution** $X_p(t)$ (forced response)

- Satisfies the differential equation
- May not be consistent with the initial conditions

$$\tau \frac{dx_p(t)}{dt} + x_p(t) = f(t)$$



4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

□ Example

$$\tau \frac{dx(t)}{dt} + x(t) = f(t) \quad f(t) = 10 \cos(200t)$$

❖ Forced response:

$$\tau \frac{dx_p(t)}{dt} + x_p(t) = f(t) \quad \Rightarrow \quad x_p(t) = A \cos(200t) + B \sin(200t)$$

❖ Natural response:

$$\tau \frac{dx_c(t)}{dt} + x_c(t) = 0 \quad \Rightarrow \quad \frac{dx_c(t)/dt}{x_c(t)} = \frac{-1}{\tau}$$

$$\Rightarrow \ln[x_c(t)] = \frac{-t}{\tau} + c \quad \Rightarrow \quad x_c(t) = e^{(-t/\tau+c)} = e^c e^{-t/\tau}$$

$$\Rightarrow x_c(t) = Ke^{-t/\tau}$$



4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES


□ Step-by-Step Solution:

- 1) Write the circuit differential equation
- 2) Find a particular solution (forced response)
- 3) Find the complementary solution (natural response)
- 4) Add particular and complementary solutions
- 5) Use initial conditions to find parameters



4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

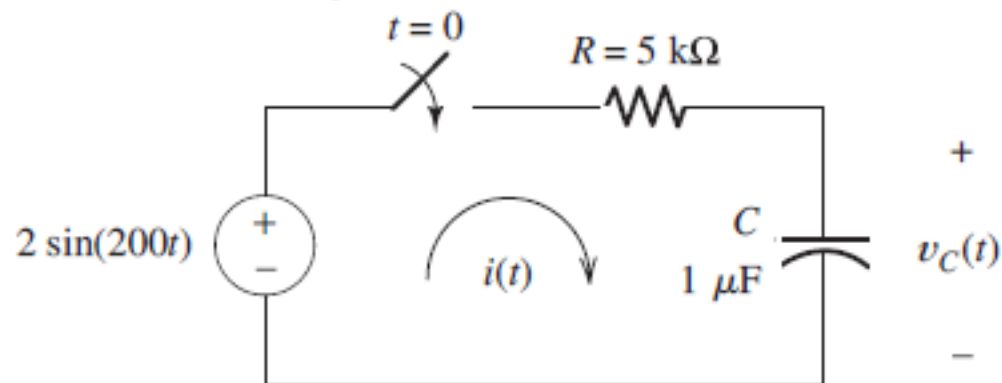Example 4.4 Transient Analysis of an RC Circuit with a Sinusoidal Source



KVL:

$$v_C(0) = 1 \text{ V}$$

$$Ri(t) + \frac{1}{C} \int_0^t i(t) dt + v_C(0) - 2 \sin(200t) = 0 \quad \Rightarrow \quad R \frac{di(t)}{dt} + \frac{1}{C} i(t) = 400 \cos(200t)$$

$$\Rightarrow RC \frac{di(t)}{dt} + i(t) = 400 C \cos(200t)$$

$$\Rightarrow 5 \times 10^{-3} \frac{di(t)}{dt} + i(t) = 400 \times 10^{-6} \cos(200t)$$



4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

Example 4.4 Transient Analysis of an RC Circuit with a Sinusoidal Source

Find a particular solution:

Guessing at the form of $i_p(t)$, possibly including some unknown constants

$$RC \frac{di(t)}{dt} + i(t) = 400 C \cos(200t) \quad \Rightarrow \quad i_p(t) = A \cos(200t) + B \sin(200t)$$

$$\Rightarrow -A \sin(200t) + B \cos(200t) + A \cos(200t) + B \sin(200t) = 400 \times 10^{-6} \cos(200t)$$

Equating the coefficients:

$$\begin{aligned} -A + B &= 0 \\ B + A &= 400 \times 10^{-6} \end{aligned} \quad \Rightarrow \quad \begin{aligned} A &= 200 \times 10^{-6} = 200 \mu\text{A} \\ B &= 200 \times 10^{-6} = 200 \mu\text{A} \end{aligned}$$

$$\Rightarrow i_p(t) = 200 \cos(200t) + 200 \sin(200t) \mu\text{A}$$

$$\Rightarrow i_p(t) = 200\sqrt{2} \cos(200t - 45^\circ)$$



4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

Example 4.4 Transient Analysis of an RC Circuit with a Sinusoidal Source

Obtain homogenous solution:

$$RC \frac{di(t)}{dt} + i(t) = 0 \quad \Rightarrow \quad i_c(t) = Ke^{-t/RC} = Ke^{-t/\tau}$$

General solution: $i(t) = 200 \cos(200t) + 200 \sin(200t) + Ke^{-t/RC} \mu\text{A}$

Determine value K by using initial condition

$$v_C(0+) = 1 \quad v_R(0+) = -1 \text{ V.} \quad \Rightarrow \quad i(0+) = \frac{v_R(0+)}{R} = \frac{-1}{5000} = -200 \mu\text{A}$$



$$\Rightarrow i(0+) = -200 = 200 + K \mu\text{A} \quad \Rightarrow \quad K = -400 \mu\text{A}$$

$$\Rightarrow i(t) = 200 \cos(200t) + 200 \sin(200t) - 400e^{-t/RC} \mu\text{A}$$




4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

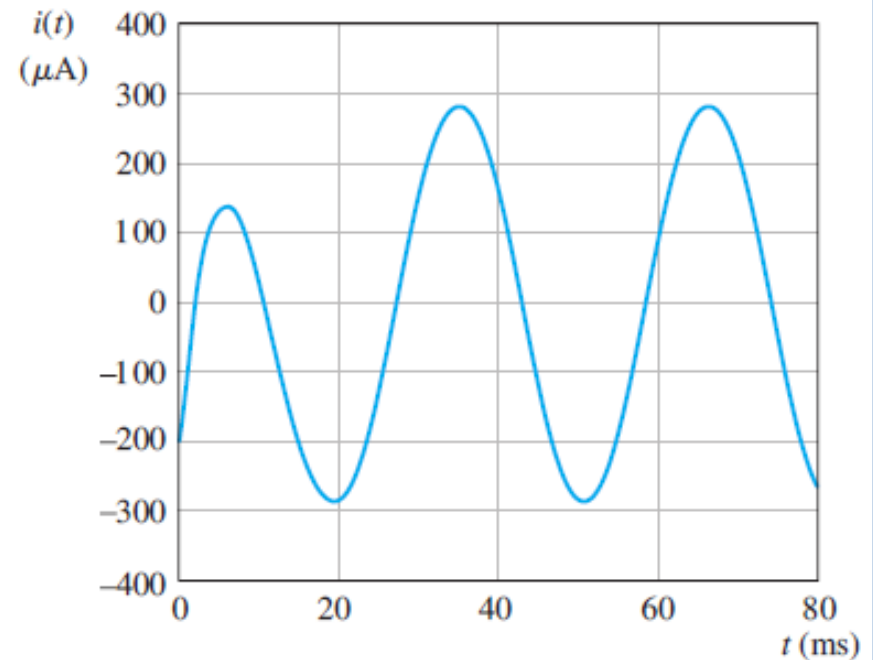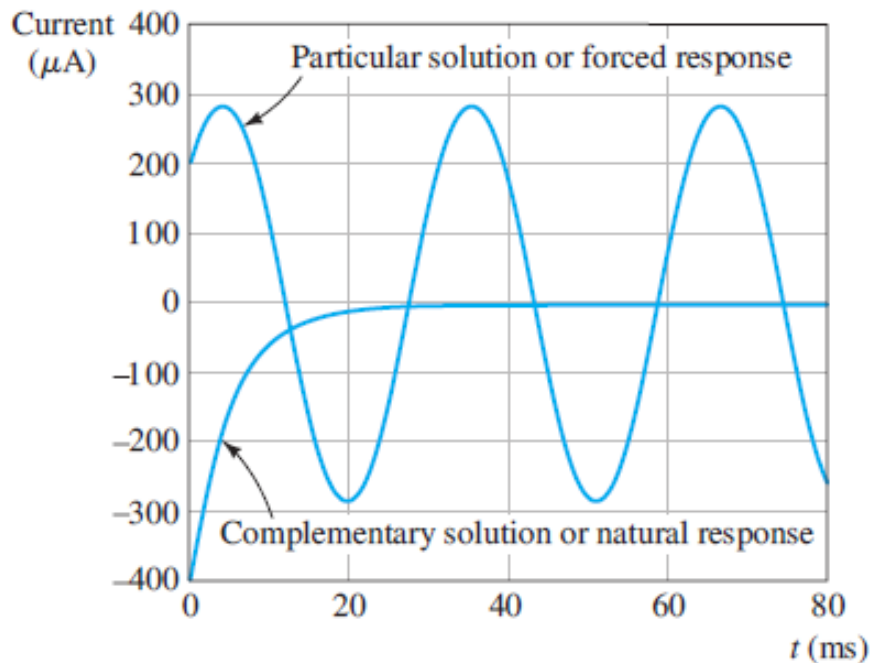Example 4.4 Transient Analysis of an RC Circuit with a Sinusoidal Source



4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

□ Exercises

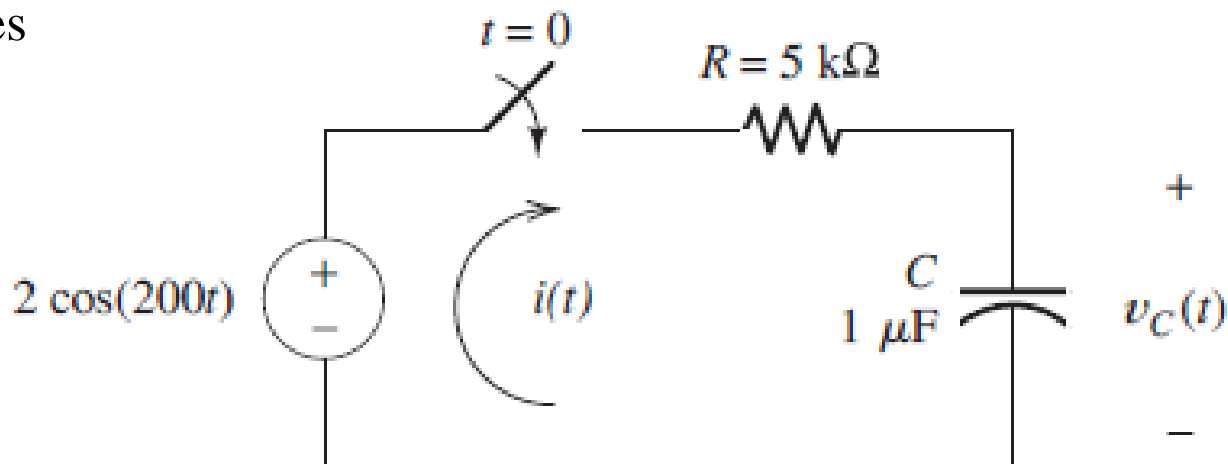


$$v_C(0) = 0$$

$$i(t) = -200 \sin(200t) + 200 \cos(200t) + 200e^{-t/RC} \mu\text{A}$$

$$\tau = RC = 5 \text{ ms}$$

4.4 RC AND RL CIRCUITS WITH GENERAL SOURCES

□ Exercises

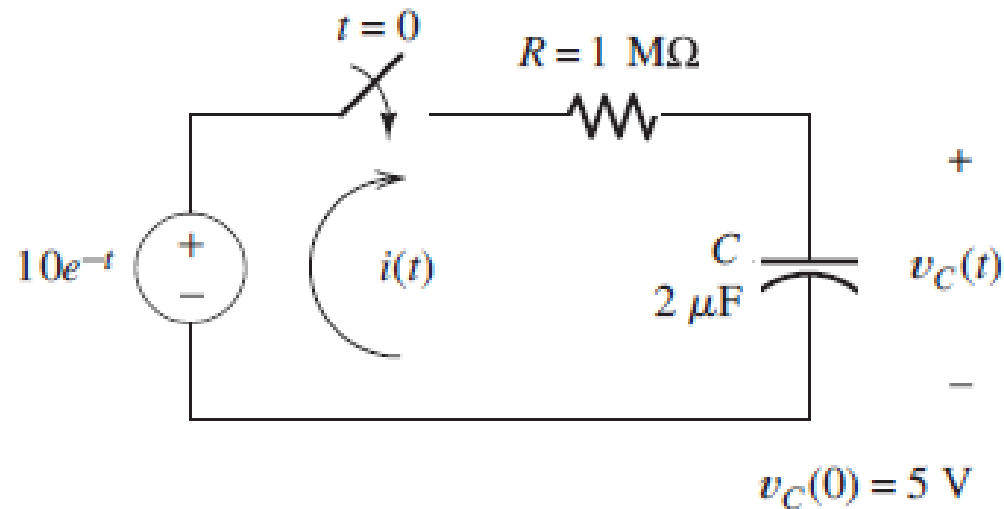


$$i(t) = 20e^{-t} - 15e^{-t/2} \mu\text{A}.$$

4.5 SECOND-ORDER CIRCUITS

- Contain two energy-storage elements
 - ✓ One inductance and one capacitance
 - ✓ Either in series or in parallel

- Differential Equation

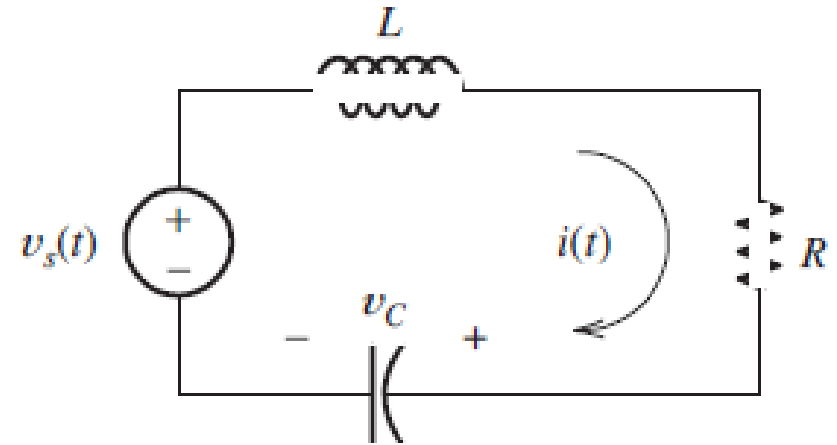

$$L \frac{di(t)}{dt} + Ri(t) + \frac{1}{C} \int_0^t i(t) dt + v_C(0) = v_s(t)$$

$$\Rightarrow L \frac{d^2i(t)}{dt^2} + R \frac{di(t)}{dt} + \frac{1}{C} i(t) = \frac{dv_s(t)}{dt}$$

$$\Rightarrow \frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$$

4.5 SECOND-ORDER CIRCUITS

$$\frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC}i(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$$


❖ Damping coefficient:

$$\alpha = \frac{R}{2L}$$

❖ Undamped resonant frequency:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

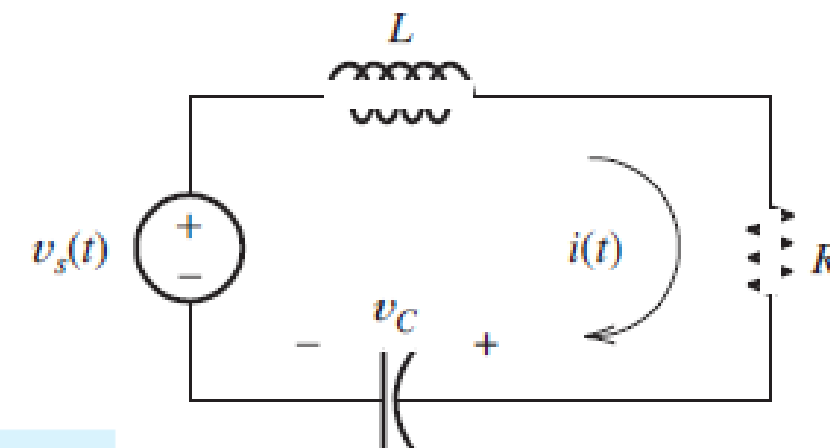❖ Forcing function: $f(t) = \frac{1}{L} \frac{dv_s(t)}{dt}$



$$\Rightarrow \frac{d^2i(t)}{dt^2} + 2\alpha \frac{di(t)}{dt} + \omega_0^2 i(t) = f(t)$$

4.5 SECOND-ORDER CIRCUITS

□ Solution of the Second-Order Equation

$$\frac{d^2x(t)}{dt^2} + 2\alpha\frac{dx(t)}{dt} + \omega_0^2x(t) = f(t)$$

❖ General solution:

✓ Particular solution ($X_p(t)$) plus complementary solution ($X_c(t)$)

$$x(t) = x_p(t) + x_c(t)$$

❖ Particular solution

$$\frac{d^2x_p(t)}{dt^2} + 2\alpha\frac{dx_p(t)}{dt} + \omega_0^2x_p(t) = f(t)$$

❖ Complementary solution

$$\frac{d^2x_c(t)}{dt^2} + 2\alpha\frac{dx_c(t)}{dt} + \omega_0^2x_c(t) = 0$$



4.5 SECOND-ORDER CIRCUITS

□ Complementary solution:

$$\frac{d^2 x_c(t)}{dt^2} + 2\alpha \frac{dx_c(t)}{dt} + \omega_0^2 x_c(t) = 0$$

$$x_c(t) = Ke^{st}$$

$$\Rightarrow s^2 Ke^{st} + 2\alpha s Ke^{st} + \omega_0^2 Ke^{st} = 0$$

$$\Rightarrow (s^2 + 2\alpha s + \omega_0^2) Ke^{st} = 0$$

$$\Rightarrow s^2 + 2\alpha s + \omega_0^2 = 0$$

❖ Characteristic equation:

✓ Damping ratio

$$\zeta = \frac{\alpha}{\omega_0}$$

❖ Roots of the characteristic equation:

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$



4.5 SECOND-ORDER CIRCUITS

❖ 3 Cases:

1) Overdamped case ($\zeta > 1$)

✓ Roots are real and distinct

$$x_c(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

2) Critically damped case

✓ Roots are real and equal

$$x_c(t) = K_1 e^{s_1 t} + K_2 t e^{s_1 t}$$

3) Underdamped case

✓ Roots are complex

$$\begin{aligned} s_1 &= -\alpha + j\omega_n \\ s_2 &= -\alpha - j\omega_n \end{aligned} \quad j = \sqrt{-1}$$

$$\omega_n = \sqrt{\omega_0^2 - \alpha^2} \quad \text{natural frequency}$$

$$\Rightarrow x_c(t) = K_1 e^{-\alpha t} \cos(\omega_n t) + K_2 e^{-\alpha t} \sin(\omega_n t)$$



4.5 SECOND-ORDER CIRCUITS

Example 4.5 Analysis of a Second-Order Circuit with a DC Source


Solve for $v_C(t)$ if $R = 300, 200,$ and 100Ω .

$$i(t) = C \frac{dv_C(t)}{dt}$$

$$L \frac{di(t)}{dt} + Ri(t) + v_C(t) = V_s$$

$$\Rightarrow LC \frac{d^2v_C(t)}{dt^2} + RC \frac{dv_C(t)}{dt} + v_C(t) = V_s$$
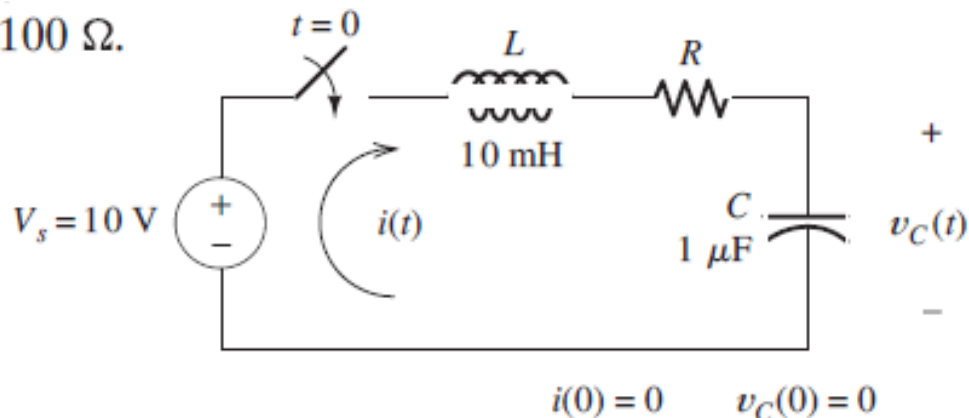
$$\Rightarrow \frac{d^2v_C(t)}{dt^2} + \frac{R}{L} \frac{dv_C(t)}{dt} + \frac{1}{LC} v_C(t) = \frac{V_s}{LC}$$



4.5 SECOND-ORDER CIRCUITS

Example 4.5 Analysis of a Second-Order Circuit with a DC Source



❖ Only dc source:

Replacing:

- Inductance by a short circuit
- Capacitance by an open circuit

Leads to particular solution:
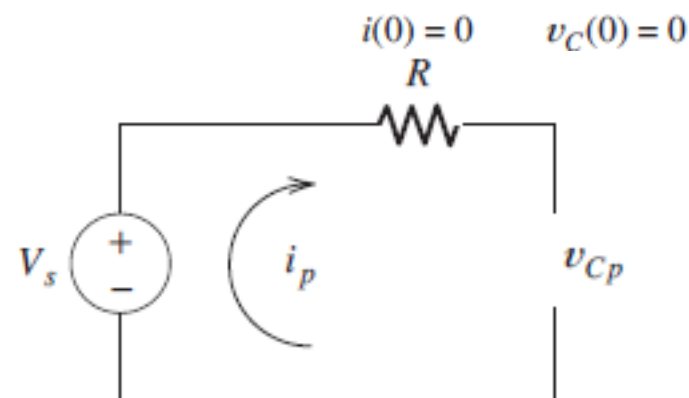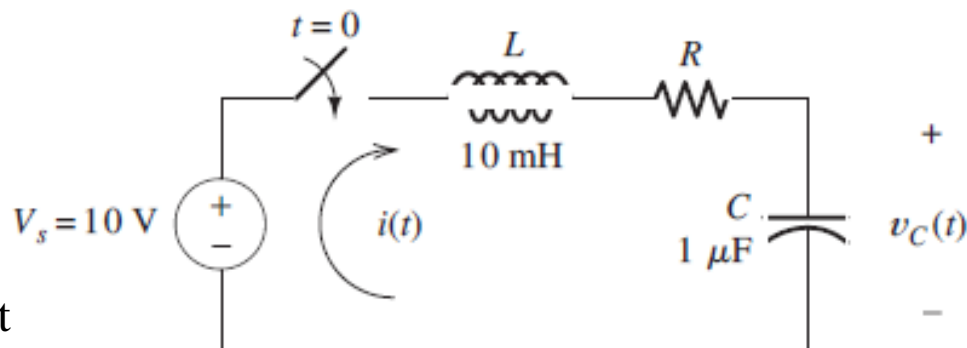
$$\Rightarrow v_{Cp}(t) = V_s = 10 \text{ V}$$



4.5 SECOND-ORDER CIRCUITS

Example 4.5 Analysis of a Second-Order Circuit with a DC Source

Homogenous solution:

Case I ($R = 300 \Omega$)

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^4$$

$$\alpha = \frac{R}{2L} = 1.5 \times 10^4$$

$$\zeta = \alpha/\omega_0 = 1.5 \quad \zeta > 1 \text{ overdamped}$$

$$\begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ &= -1.5 \times 10^4 - \sqrt{(1.5 \times 10^4)^2 - (10^4)^2} \\ &= -2.618 \times 10^4 \end{aligned}$$

$$\begin{aligned} s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \\ &= -0.3820 \times 10^4 \end{aligned}$$

$$\Rightarrow v_C(t) = 10 + K_1 e^{s_1 t} + K_2 e^{s_2 t} \quad \Rightarrow 10 + K_1 + K_2 = 0$$



4.5 SECOND-ORDER CIRCUITS


Example 4.5 Analysis of a Second-Order Circuit with a DC Source

$$i(0) = 0 \quad \Rightarrow \quad i(t) = C \frac{dv_C(t)}{dt} \quad \Rightarrow \quad \frac{dv_C(0)}{dt} = 0$$

$$\Rightarrow s_1 K_1 + s_2 K_2 = 0$$

$$\Rightarrow \begin{aligned} K_1 &= 1.708 \\ K_2 &= -11.708 \end{aligned}$$
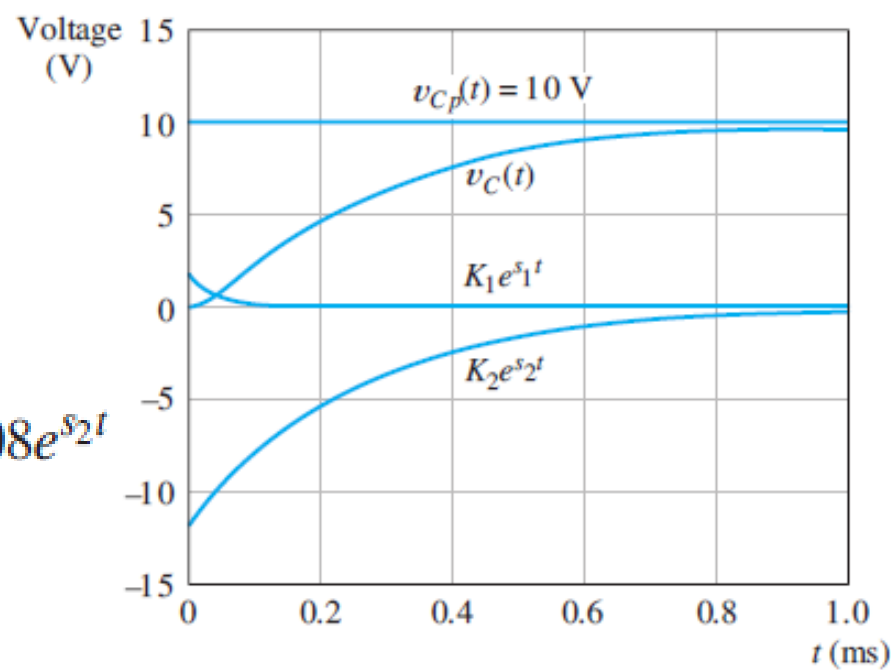
$$\Rightarrow v_C(t) = 10 + 1.708e^{s_1 t} - 11.708e^{s_2 t}$$



4.5 SECOND-ORDER CIRCUITS

Example 4.5 Analysis of a Second-Order Circuit with a DC Source

Case II ($R = 200 \Omega$)

$$\alpha = \frac{R}{2L} = 10^4$$

$$\zeta = \alpha/\omega_0 = 1 \quad \text{critically damped case.}$$


$$\Rightarrow s_1 = s_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -\alpha = -10^4$$

$$\Rightarrow v_C(t) = 10 + K_1 e^{s_1 t} + K_2 t e^{s_1 t}$$

initial conditions $v_C(0) = 0 \quad dv_C(0)/dt = 0.$

$$\begin{aligned} \Rightarrow 10 + K_1 = 0 & \Rightarrow K_1 = -10 \\ s_1 K_1 + K_2 = 0 & \Rightarrow K_2 = -10^5. \end{aligned}$$
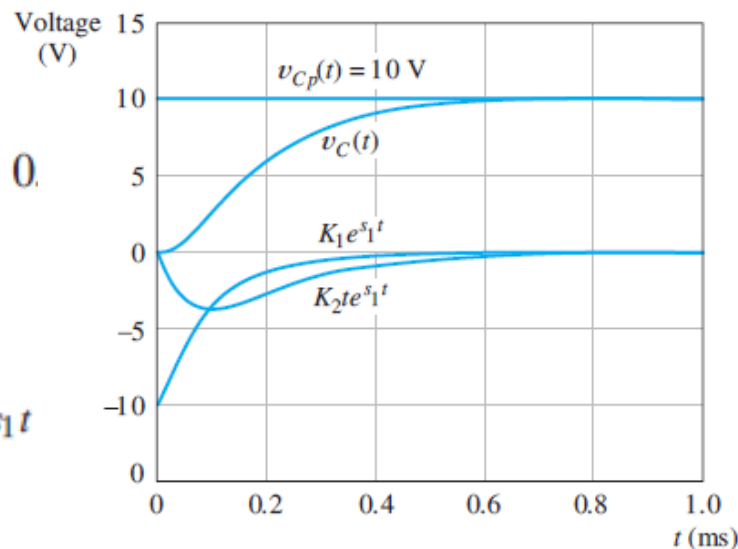
$$\Rightarrow v_C(t) = 10 - 10e^{s_1 t} - 10^5 t e^{s_1 t}$$



4.5 SECOND-ORDER CIRCUITS

Example 4.5 Analysis of a Second-Order Circuit with a DC Source


Case III ($R = 100 \Omega$) $\alpha = \frac{R}{2L} = 5000$ $\zeta = \alpha/\omega_0 = 0.5$ underdamped

$$\Rightarrow \omega_n = \sqrt{\omega_0^2 - \alpha^2} = 8660$$

$$\Rightarrow v_C(t) = 10 + K_1 e^{-\alpha t} \cos(\omega_n t) + K_2 e^{-\alpha t} \sin(\omega_n t)$$

$$\begin{aligned} \Rightarrow 10 + K_1 &= 0 & \Rightarrow K_1 &= -10 \\ -\alpha K_1 + \omega_n K_2 &= 0 & \Rightarrow K_2 &= -5.774. \end{aligned}$$

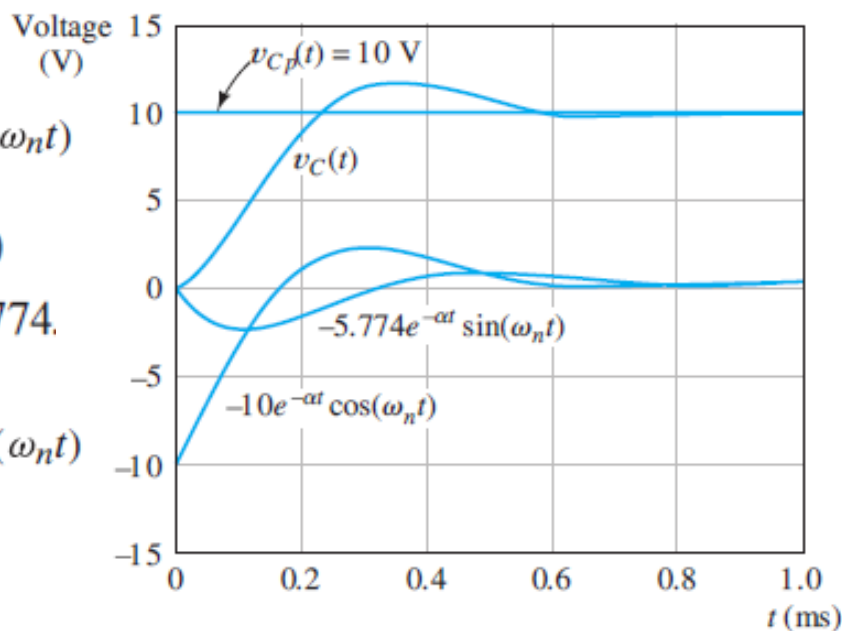
$$\Rightarrow v_C(t) = 10 - 10e^{-\alpha t} \cos(\omega_n t) - 5.774e^{-\alpha t} \sin(\omega_n t)$$



4.5 SECOND-ORDER CIRCUITS

Example 4.5 Analysis of a Second-Order Circuit with a DC Source

❖ Comparison:

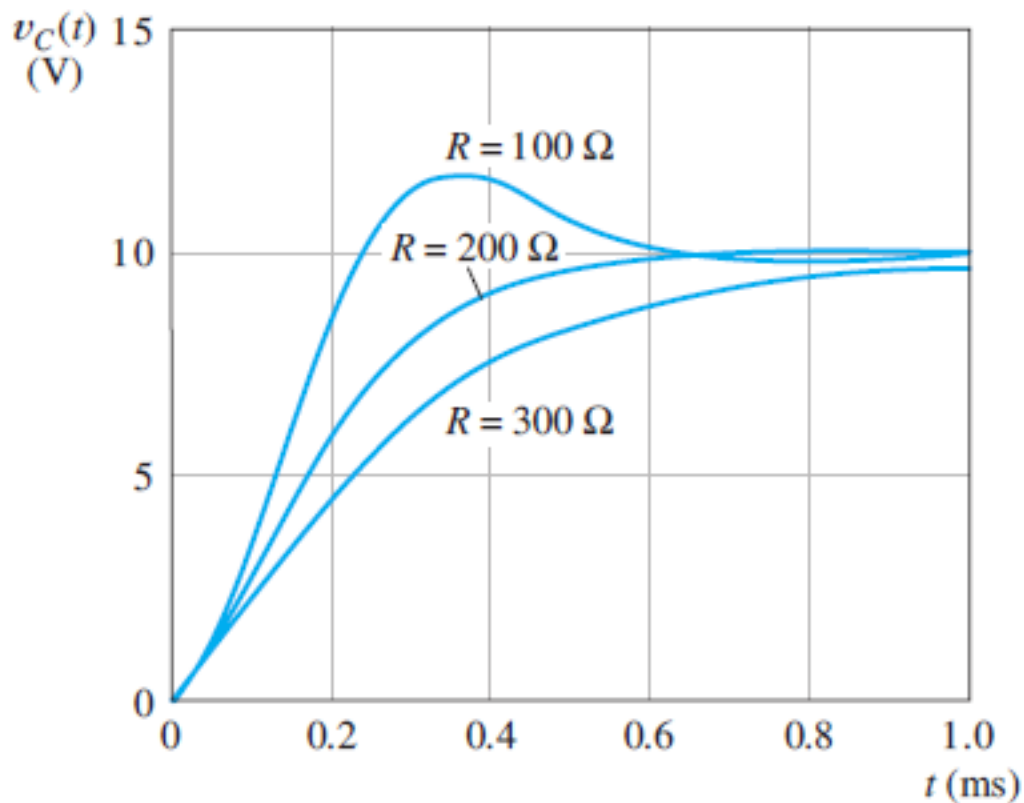


4.5 SECOND-ORDER CIRCUITS


□ Normalized Step Response of Second-Order Systems

❖ Step function

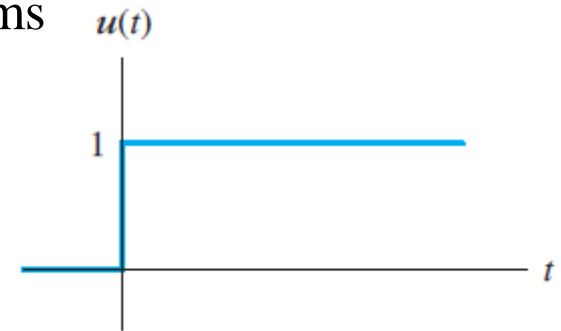
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$



$$v(t) = Au(t)$$

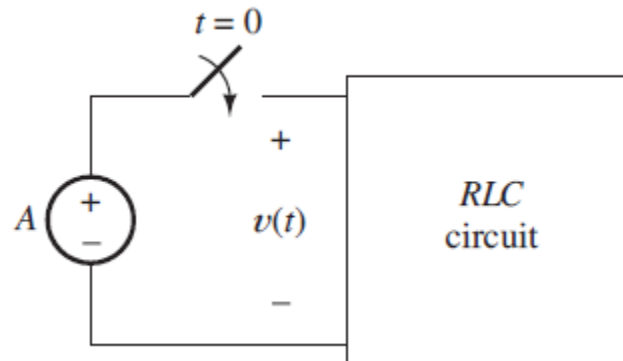

$$v(t) = Au(t)$$

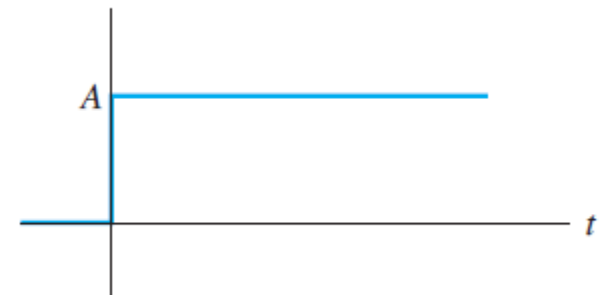

4.5 SECOND-ORDER CIRCUITS


Normalized Step Response of Second-Order Systems

$$\frac{d^2x(t)}{dt^2} + 2\alpha\frac{dx(t)}{dt} + \omega_0^2x(t) = Au(t)$$

undamped resonant frequency ω_0


damping ratio $\zeta = \alpha/\omega_0$.

- ❖ Overshoot
- ❖ Ringing

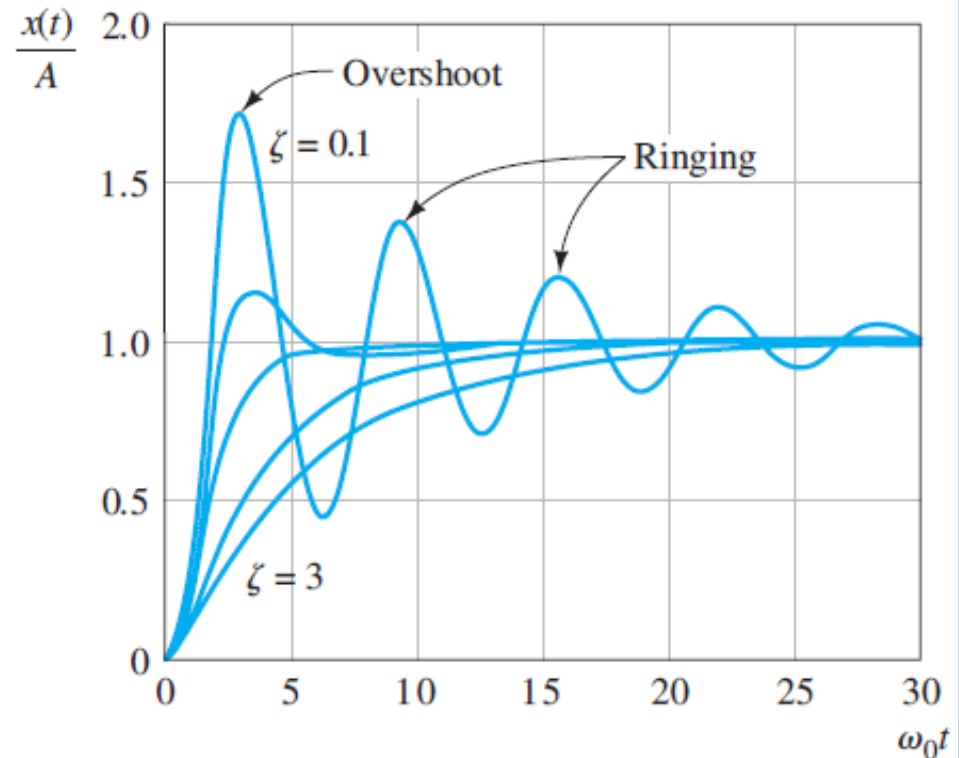

4.5 SECOND-ORDER CIRCUITS

□ Circuits with Parallel L and C

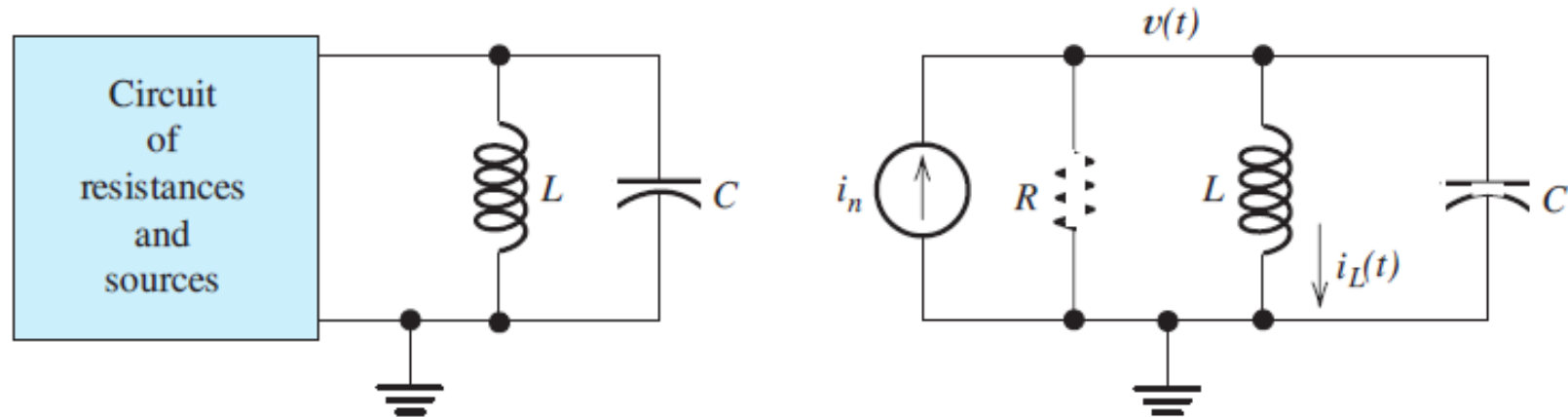

❖ Writing a KCL equation at the top node:

$$C \frac{dv(t)}{dt} + \frac{1}{R}v(t) + \frac{1}{L} \int_0^t v(t) dt + i_L(0) = i_n(t)$$

4.5 SECOND-ORDER CIRCUITS

❖ Simplification

$$C \frac{dv(t)}{dt} + \frac{1}{R}v(t) + \frac{1}{L} \int_0^t v(t) dt + i_L(0) = i_n(t)$$

$$\Rightarrow C \frac{d^2v(t)}{dt^2} + \frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L}v(t) = \frac{di_n(t)}{dt}$$

$$\Rightarrow \frac{d^2v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC}v(t) = \frac{1}{C} \frac{di_n(t)}{dt}$$

✓ Damping coefficient

$$\alpha = \frac{1}{2RC}$$

✓ Undamped resonant frequency

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

✓ Forcing function


$$f(t) = \frac{1}{C} \frac{di_n(t)}{dt}$$

$$\Rightarrow \frac{d^2v(t)}{dt^2} + 2\alpha \frac{dv(t)}{dt} + \omega_0^2 v(t) = f(t)$$



4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.9

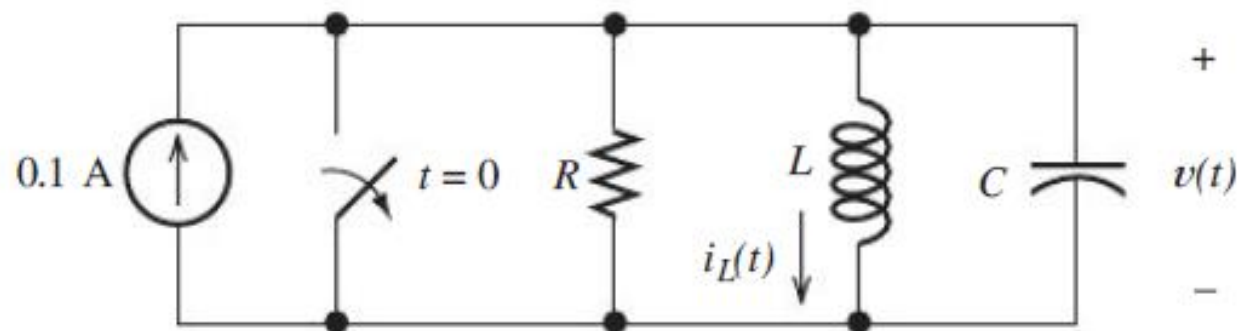

$$R = 25 \Omega. \quad L = 1 \text{ mH} \quad C = 0.1 \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 10^{-7}}} = 10^5 \quad \alpha = \frac{1}{2RC} = 2 \times 10^5 \quad \zeta = \frac{\alpha}{\omega_0} = 2$$

At $t = 0+$, the KCL equation

$$0.1 = \frac{v(0+)}{R} + i_L(0+) + Cv'(0+)$$

4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.9

$$\begin{aligned} v(0+) = v(0-) = 0 & \quad \longrightarrow \quad v'(0+) = 10^6 \text{ V/s} \\ i_L(0+) = i_L(0-) = 0 & \end{aligned}$$

particular solution \longrightarrow steady-state conditions $\longrightarrow v_p(t) = 0$

homogeneous solution \longrightarrow circuit is overdamped ($\zeta > 1$).

$$\begin{aligned} s_1 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -373.2 \times 10^3 \\ \longrightarrow s_2 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -26.79 \times 10^3 \end{aligned}$$



4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.9

$$\Rightarrow v(t) = K_1 \exp(s_1 t) + K_2 \exp(s_2 t)$$

initial conditions

$$v(0+) = 0 = K_1 + K_2 \quad v'(0+) = 10^6 = K_1 s_1 + K_2 s_2$$


$$\Rightarrow K_1 = -2.887 \text{ and } K_2 = 2.887$$

$$\Rightarrow v(t) = 2.887[\exp(s_2 t) - \exp(s_1 t)]$$



4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.10

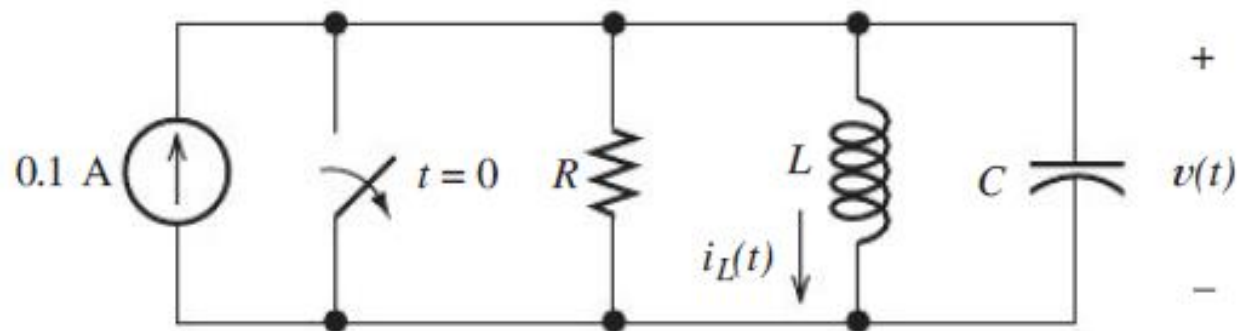

$$R = 50 \, \Omega \quad L = 1 \, \text{mH} \quad C = 0.1 \, \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 10^{-7}}} = 10^5 \quad \alpha = \frac{1}{2RC} = 10^5 \quad \zeta = \frac{\alpha}{\omega_0} = 1$$

At $t = 0+$, the KCL equation

$$0.1 = \frac{v(0+)}{R} + i_L(0+) + Cv'(0+)$$

4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.10

$$\begin{aligned} v(0+) = v(0-) = 0 & \quad \implies v'(0+) = 10^6 \text{ V/s} \\ i_L(0+) = i_L(0-) = 0 & \end{aligned}$$

particular solution \implies steady-state conditions $\implies v_p(t) = 0$

homogeneous solution

$$\implies s_1 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -10^5 \quad s_2 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -10^5$$



4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.10

$$\Rightarrow v(t) = K_1 \exp(s_1 t) + K_2 t \exp(s_1 t)$$

initial conditions

$$v(0+) = 0 = K_1 \quad v'(0+) = 10^6 = K_1 s_1 + K_2$$


$$\Rightarrow K_2 = 10^6$$

$$\Rightarrow v(t) = 10^6 t \exp(-10^5 t)$$



4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.11

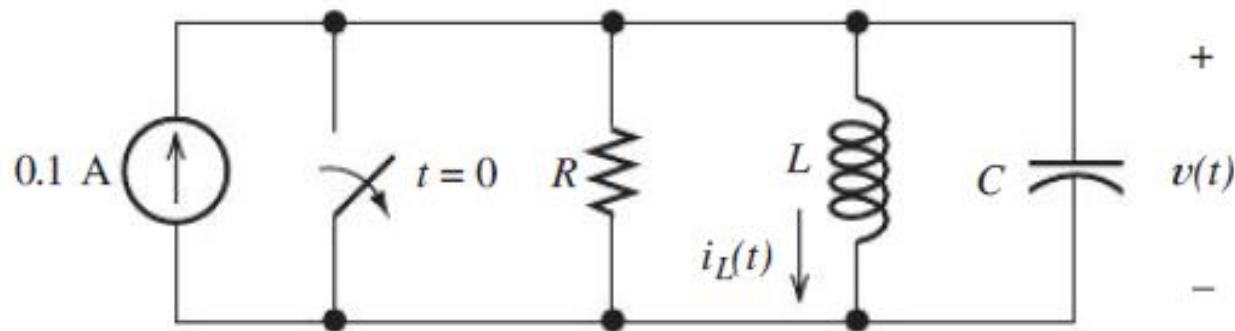

$$R = 250 \, \Omega \quad L = 1 \, \text{mH} \quad C = 0.1 \, \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 10^{-7}}} = 10^5 \quad \alpha = \frac{1}{2RC} = 2 \times 10^4 \quad \zeta = \frac{\alpha}{\omega_0} = 0.2$$

At $t = 0+$, the KCL equation

$$0.1 = \frac{v(0+)}{R} + i_L(0+) + Cv'(0+)$$

4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.11

$$\begin{aligned} v(0+) = v(0-) = 0 & \quad \longrightarrow \quad v'(0+) = 10^6 \text{ V/s} \\ i_L(0+) = i_L(0-) = 0 & \end{aligned}$$

particular solution \longrightarrow steady-state conditions $\longrightarrow v_p(t) = 0$

homogeneous solution

$$\longrightarrow \omega_n = \sqrt{\omega_0^2 - \alpha^2} = 97.98 \times 10^3$$



4.5 SECOND-ORDER CIRCUITS

□ Exercise 4.11

$$\Rightarrow v(t) = K_1 \exp(-\alpha t) \cos(\omega_n t) + K_2 \exp(-\alpha t) \sin(\omega_n t)$$

initial conditions

$$v(0+) = 0 = K_1 \quad v'(0+) = 10^6 = -\alpha K_1 + \omega_n K_2$$


$$\Rightarrow K_2 = 10.21$$

$$\Rightarrow v(t) = 10.21 \exp(-2 \times 10^4 t) \sin(97.98 \times 10^3 t) \text{ V}$$



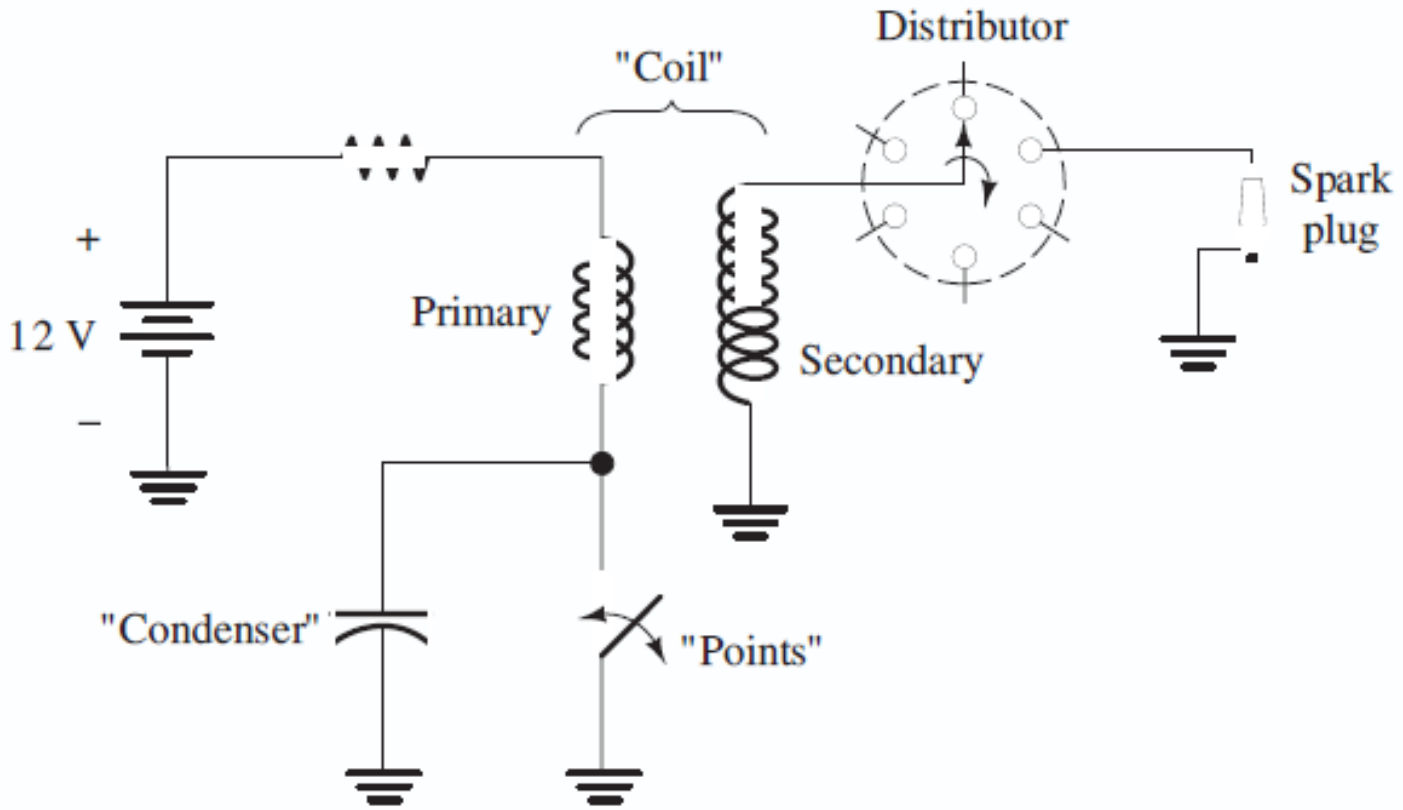4.5 SECOND-ORDER CIRCUITS

- Classic ignition for an internal-combustion engine



EXERCISES

 P4.4 P4.5 P4.21 P4.22 P4.23 P4.33 P4.34 P4.45 P4.46 P4.47 P4.61 P4.62 P4.63 T4.1 T4.2 T4.3