



دانشگاه سمنان

Semnan University  
Faculty of Mechanical Engineering

دانشکده مهندسی مکانیک



دانشکده مهندسی مکانیک

درس مبانی برق ۱


نیمسال اول ۹۸-۹۹

# ELECTRICAL ENGINEERING

PRINCIPLES AND APPLICATIONS

Allan R. Hambley

5<sup>th</sup> Edition

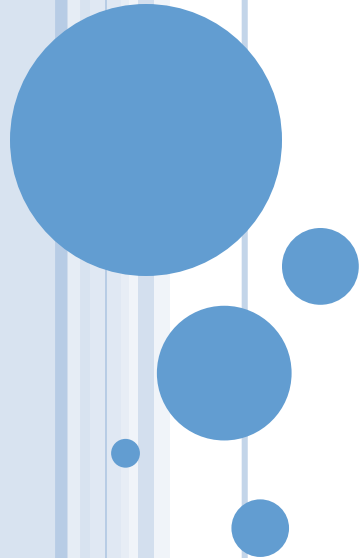

### □ CONTENTS:

- ❖ Chapter 1: Introduction
- ❖ Chapter 2: Resistive Circuits
- ❖ Chapter 3: **Inductance and Capacitance**
- ❖ Chapter 4: Transients
- ❖ Chapter 5: Steady-State Sinusoidal Analysis




## INTRODUCTION

- ❑ Find the  $I$  ( $V$ ) for a capacitance or inductance given the  $V$  ( $I$ )
- ❑ Compute the capacitances of parallel-plate capacitors.
- ❑ Compute the energies stored in capacitances or inductances
- ❑ Describe typical physical construction of capacitors and inductors
- ❑ Mutually coupled inductances


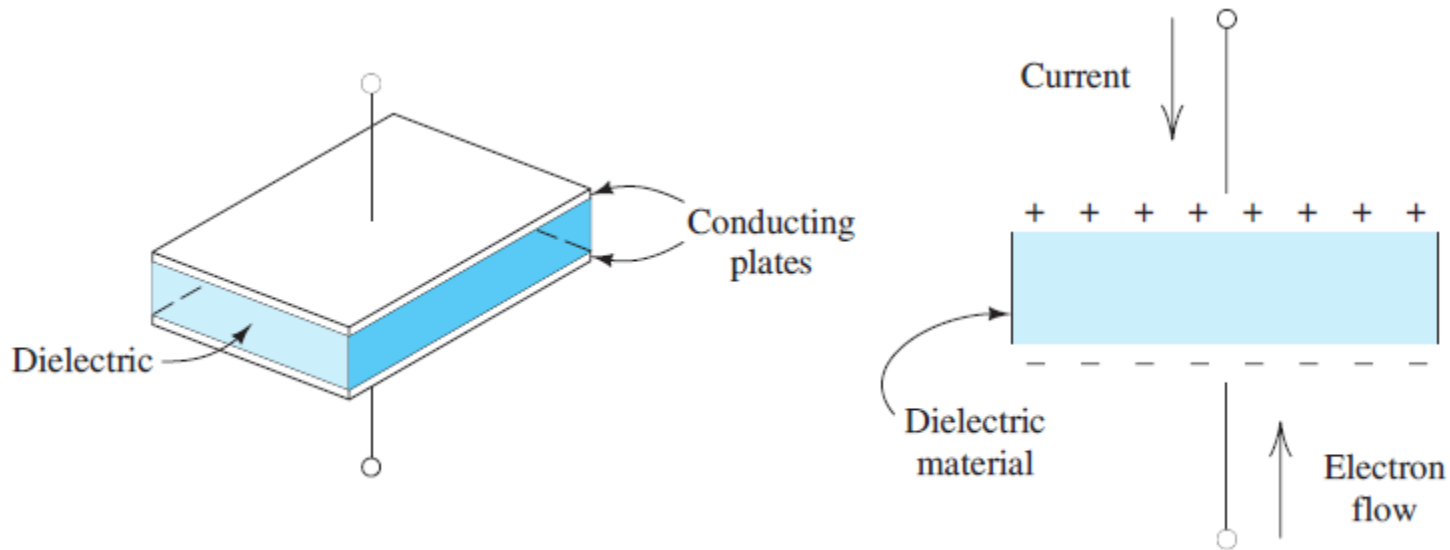
### 3.1 CAPACITANCE

- Separating two sheets of conductor by a thin layer of insulating material



### 3.1 CAPACITANCE

#### □ Stored Charge in Terms of Voltage

$$q = Cv$$

❖ Unit: Farads (F)

❖ In most applications: a few picofarads ( $1 \text{ pF} = 10^{-12} \text{ F}$ ) up to  $0.01 \text{ F}$

#### □ Current in Terms of Voltage


$$i = \frac{dq}{dt} = \frac{d}{dt}(Cv)$$

$$i = C \frac{dv}{dt}$$
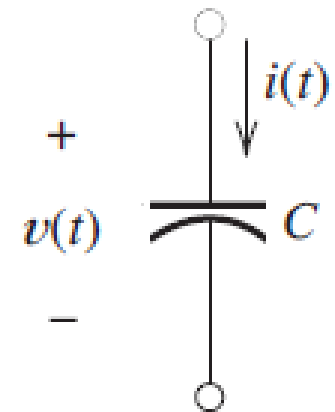
#### □ Voltage in Terms of Current





$$q(t) = \int_{t_0}^t i(t) dt + q(t_0)$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$$





## 3.1 CAPACITANCE
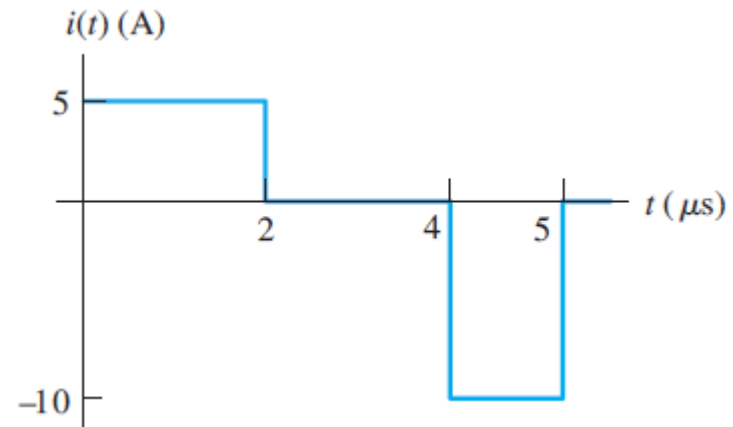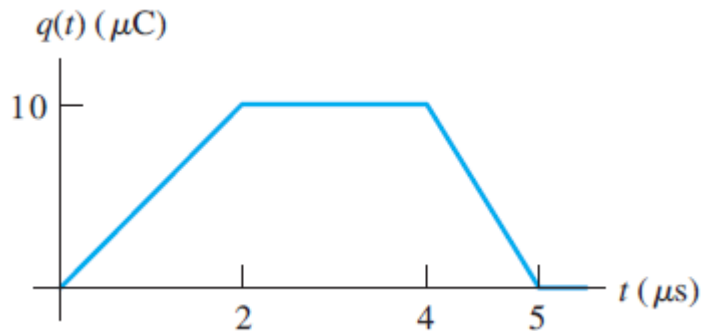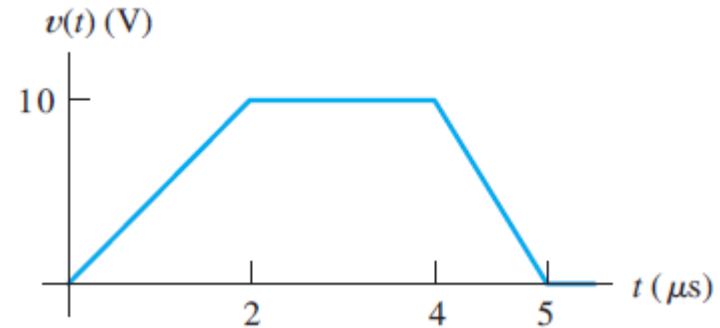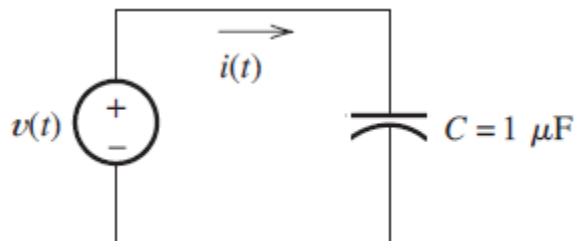
## Example 3.1 Determining Current for a Capacitance Given Voltage




## 3.1 CAPACITANCE
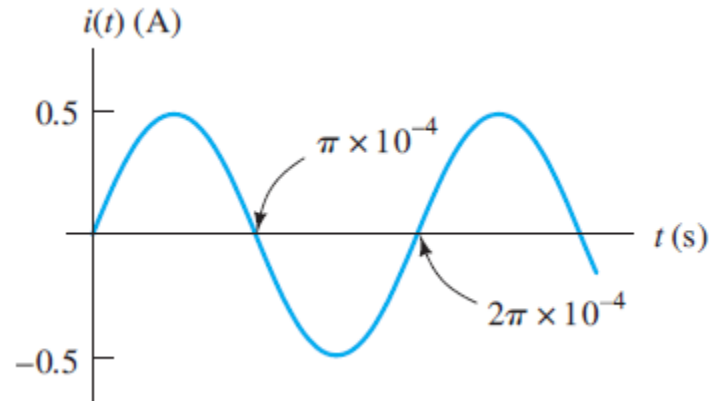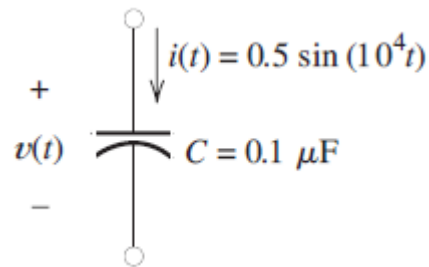
## Example 3.2 Determining Voltage for a Capacitance Given Current




$$\begin{aligned} q(t) &= \int_0^t i(t) dt + q(0) \\ &= \int_0^t 0.5 \sin(10^4 t) dt \\ &= -0.5 \times 10^{-4} \cos(10^4 t) \Big|_0^t \\ &= 0.5 \times 10^{-4} [1 - \cos(10^4 t)] \end{aligned}$$

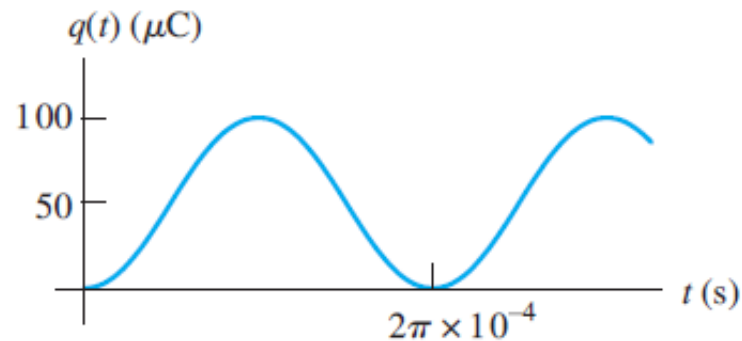


## 3.1 CAPACITANCE
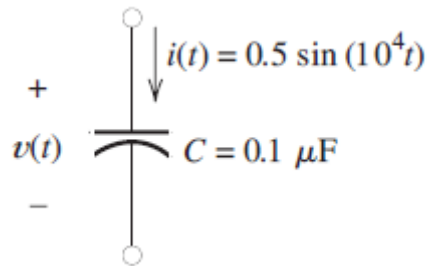
## Example 3.2 Determining Voltage for a Capacitance Given Current



$$v(t) = \frac{q(t)}{C} = \frac{q(t)}{10^{-7}}$$

$$= 500[1 - \cos(10^4 t)]$$

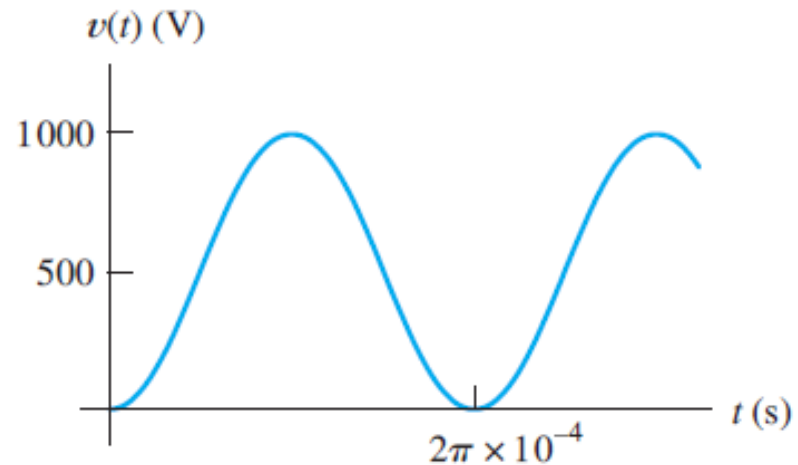



## 3.1 CAPACITANCE

### □ Stored Energy

$$p(t) = v(t)i(t) = Cv \frac{dv}{dt}$$

$$w(t) = \int_{t_0}^t p(t) dt = \int_{t_0}^t Cv \frac{dv}{dt} dt = \int_0^{v(t)} Cv dv$$

$$\rightarrow w(t) = \frac{1}{2}Cv^2(t)$$

$$w(t) = \frac{1}{2}v(t)q(t)$$

$$w(t) = \frac{q^2(t)}{2C}$$




## 3.1 CAPACITANCE
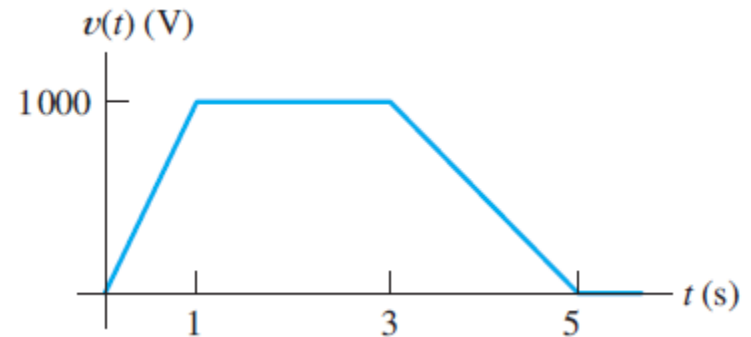
### Example 3.3 Current, Power, and Energy for a Capacitance


10- $\mu$ F capacitance

$$v(t) = \begin{cases} 1000t \text{ V} & \text{for } 0 < t < 1 \\ 1000 \text{ V} & \text{for } 1 < t < 3 \\ 500(5 - t) \text{ V} & \text{for } 3 < t < 5 \end{cases}$$



$$i(t) = C \frac{dv(t)}{dt}$$
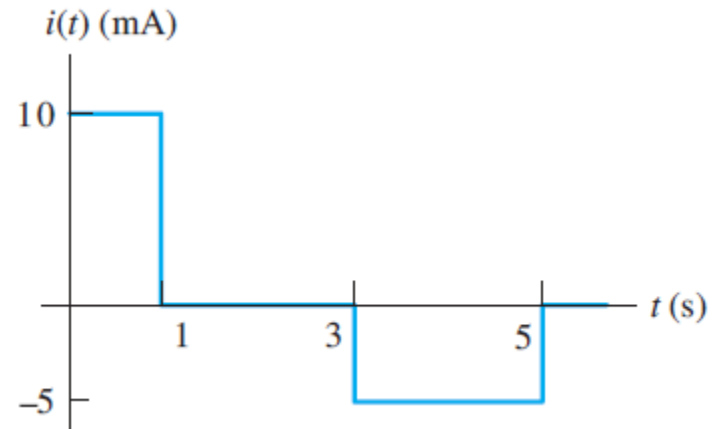
$$i(t) = \begin{cases} 10 \times 10^{-3} \text{ A} & \text{for } 0 < t < 1 \\ 0 \text{ A} & \text{for } 1 < t < 3 \\ -5 \times 10^{-3} \text{ A} & \text{for } 3 < t < 5 \end{cases}$$



## 3.1 CAPACITANCE



## Example 3.3 Current, Power, and Energy for a Capacitance

$$p(t) = v(t)i(t)$$

$$p(t) = \begin{cases} 10t \text{ W} & \text{for } 0 < t < 1 \\ 0 \text{ W} & \text{for } 1 < t < 3 \\ 2.5(t - 5) \text{ W} & \text{for } 3 < t < 5 \end{cases}$$

$$w(t) = \frac{1}{2}Cv^2(t)$$


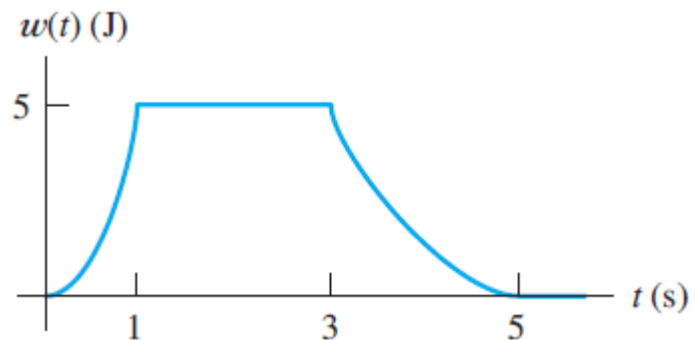
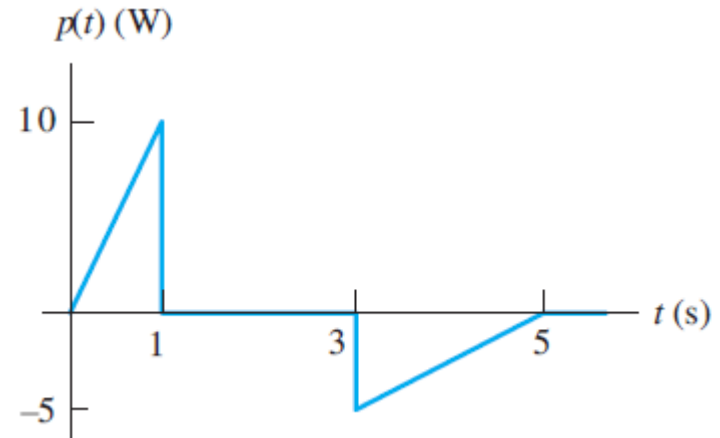
$$w(t) = \begin{cases} 5t^2 \text{ J} & \text{for } 0 < t < 1 \\ 5 \text{ J} & \text{for } 1 < t < 3 \\ 1.25(5 - t)^2 \text{ J} & \text{for } 3 < t < 5 \end{cases}$$



### 3.1 CAPACITANCE

#### □ Exercise




$0.1\text{-}\mu\text{F}$  capacitor

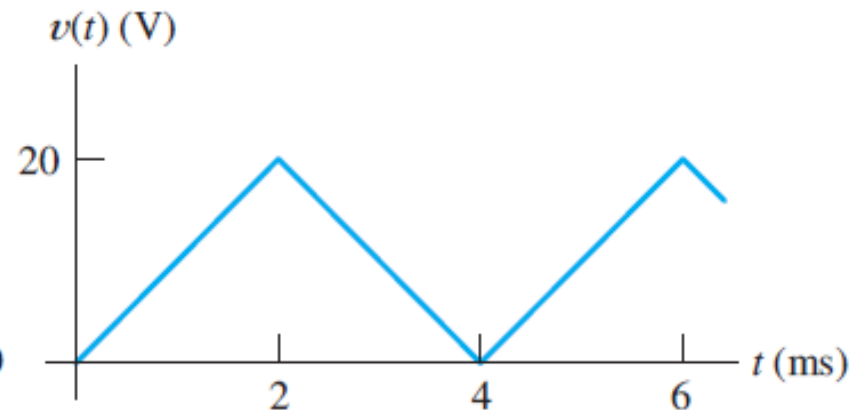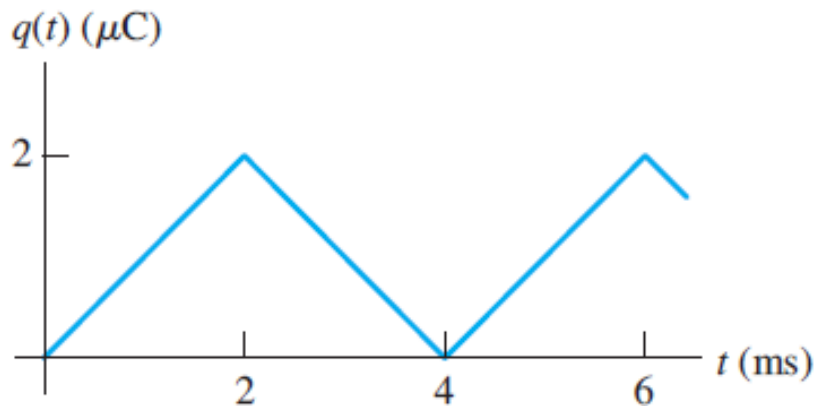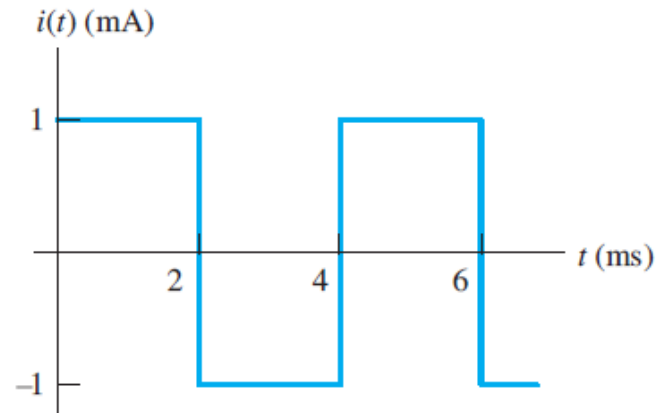

### 3.1 CAPACITANCE

#### □ Exercise

$0.1\text{-}\mu\text{F}$  capacitor

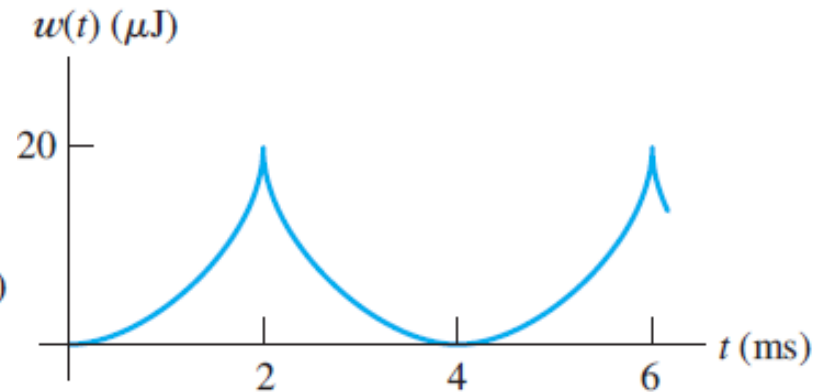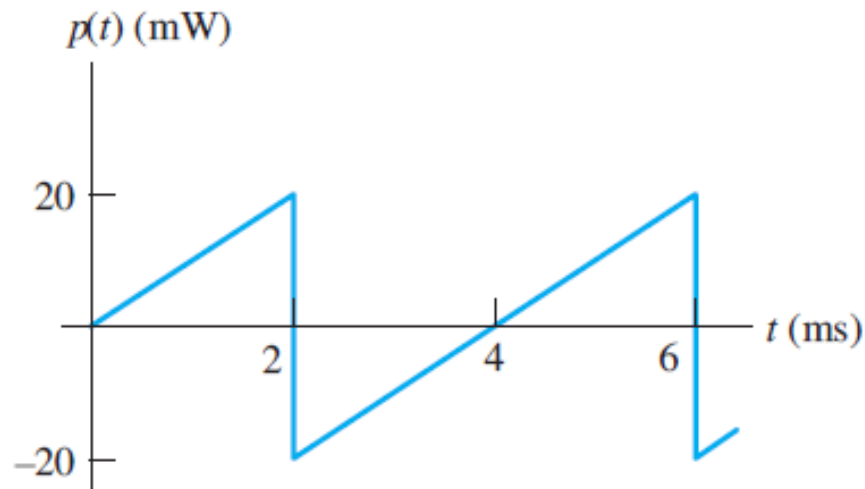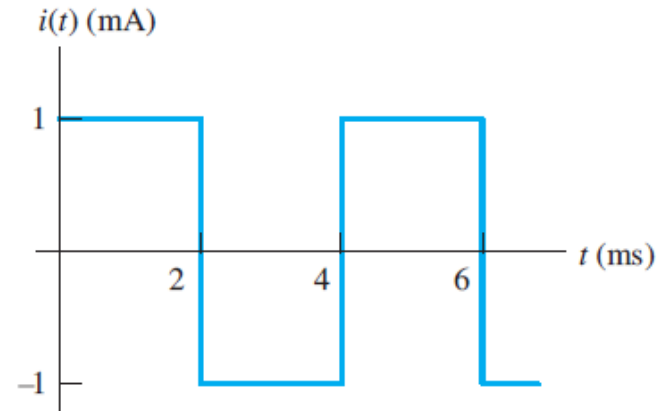


## 3.2 CAPACITANCES IN SERIES AND PARALLEL

### □ Capacitances in Parallel

$$i_1 = C_1 \frac{dv}{dt}$$

$$i_2 = C_2 \frac{dv}{dt}$$

$$i_3 = C_3 \frac{dv}{dt}$$

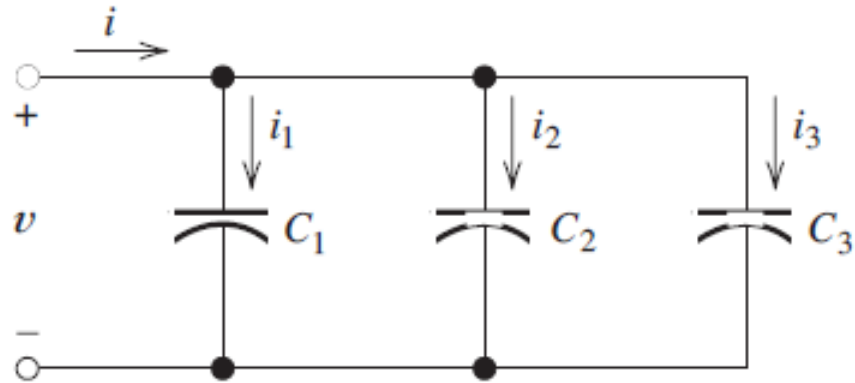


$$i = i_1 + i_2 + i_3 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} = (C_1 + C_2 + C_3) \frac{dv}{dt}$$

$$\Rightarrow C_{eq} = C_1 + C_2 + C_3 \quad i = C_{eq} \frac{dv}{dt}$$

## 3.2 CAPACITANCES IN SERIES AND PARALLEL
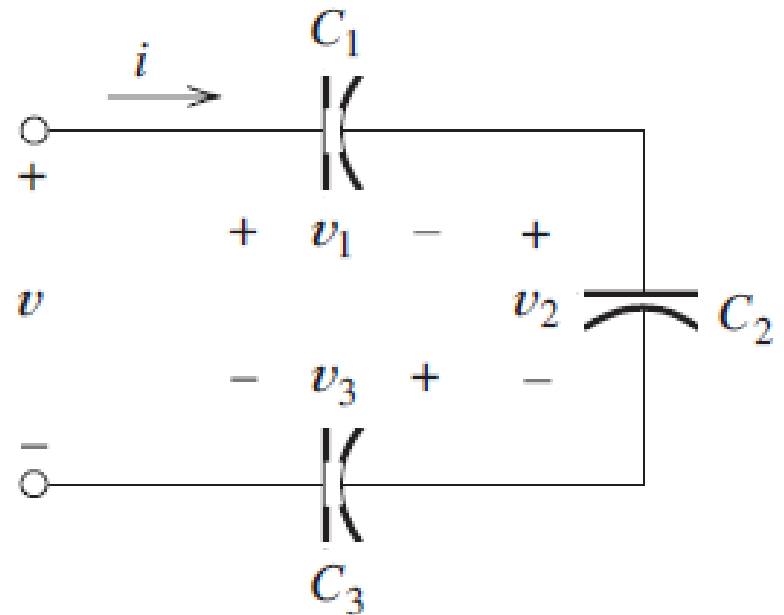
### □ Capacitances in Series

$$C_{eq} = \frac{1}{1/C_1 + 1/C_2 + 1/C_3}$$



### 3.3 PHYSICAL CHARACTERISTICS OF CAPACITORS

#### □ Capacitance of the Parallel-Plate Capacitor


$$C = \frac{\epsilon A}{d}$$

$\epsilon$  is the **dielectric constant**

For vacuum  $\epsilon = \epsilon_0 \cong 8.85 \times 10^{-12} \text{ F/m}$

For other materials,  $\epsilon = \epsilon_r \epsilon_0$

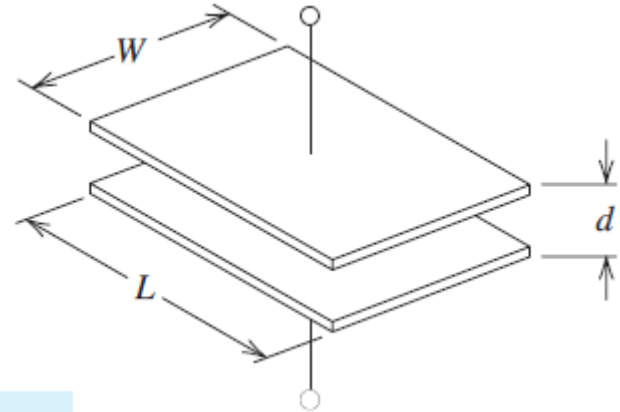$\epsilon_r$  is the **relative dielectric constant**.





### 3.3 PHYSICAL CHARACTERISTICS OF CAPACITORS

- Relative dielectric constant

**Table 3.1. Relative Dielectric Constants for Selected Materials**

Air	1.0
Diamond	5.5
Mica	7.0
Polyester	3.4
Quartz	4.3
Silicon dioxide	3.9
Water	78.5

### 3.3 PHYSICAL CHARACTERISTICS OF CAPACITORS

#### Example 3.4 Calculating Capacitance Given Physical Parameters

rectangular plates 10 cm by 20 cm

distance of 0.1 mm

dielectric is air.

$$A = L \times W = (10 \times 10^{-2}) \times (20 \times 10^{-2}) = 0.02 \text{ m}^2$$

relative dielectric constant of air is 1.00

$$\epsilon = \epsilon_r \epsilon_0 = 1.00 \times 8.85 \times 10^{-12} \text{ F/m}$$


$$C = \frac{\epsilon A}{d} = \frac{8.85 \times 10^{-12} \times 0.02}{10^{-4}} = 1770 \times 10^{-12} \text{ F}$$



### 3.3 PHYSICAL CHARACTERISTICS OF CAPACITORS
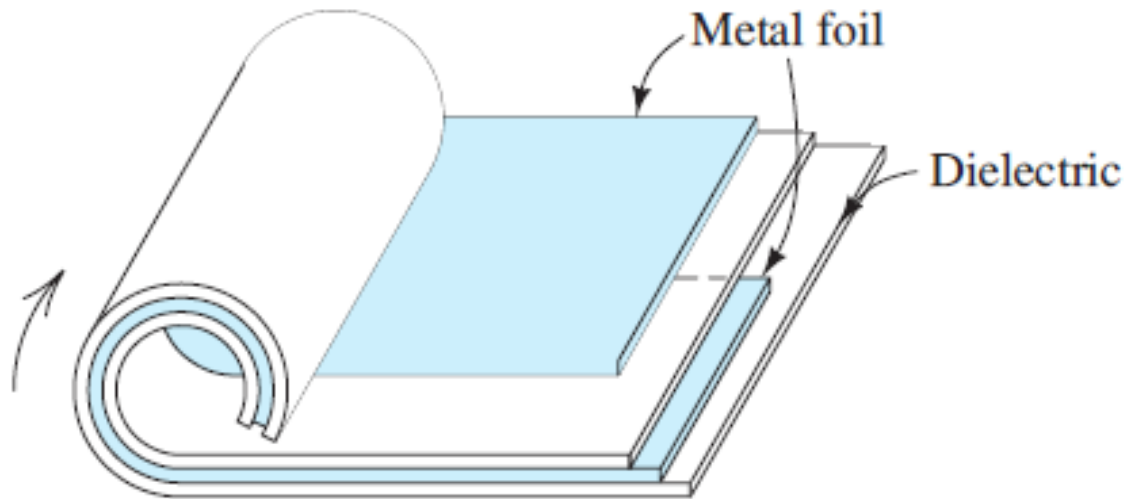
#### □ Practical Capacitors


- ❖ The dimensions of parallel-plate capacitors are too large
- ❖ Rolled to fit in a smaller area
- ❖ Real capacitors have maximum voltage ratings



### 3.3 PHYSICAL CHARACTERISTICS OF CAPACITORS

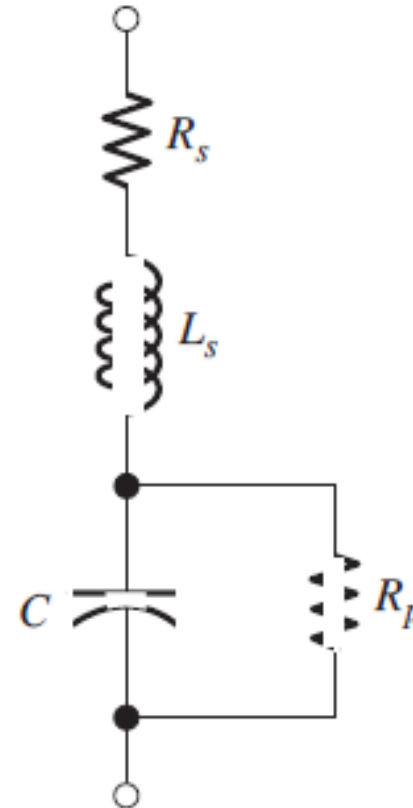
#### □ Parasitic Effects

- ❖ Resistivity of the material composing the plates
- ❖ Magnetic field in capacitor
- ❖ No practical material is a perfect insulator



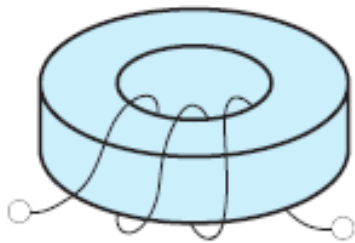
## 3.4 INDUCTANCE


- ❑ Coiling a wire around some type of form
- ❑ Coil creates a magnetic field or flux
- ❑ Faraday's law of electromagnetic induction



(a) Toroidal inductor

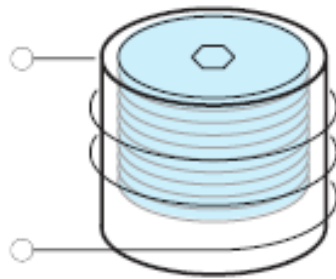

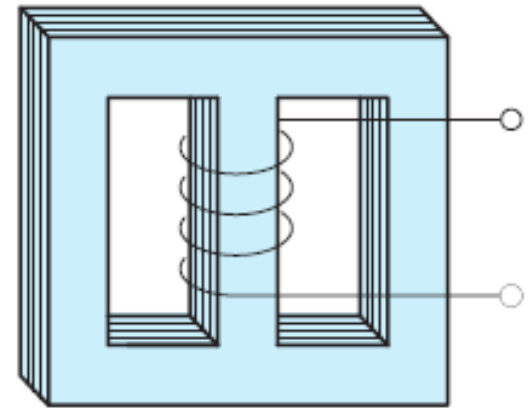(b) Coil with an iron-oxide slug that can be screwed in or out to adjust the inductance




(c) Inductor with a laminated iron core

## 3.4 INDUCTANCE

### □ Voltage and current relation

$$v(t) = L \frac{di}{dt}$$

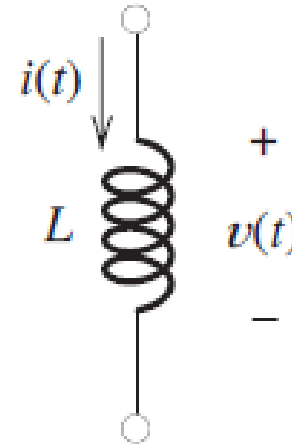

- ❖ Unit: Henries (H) (volt seconds per ampere)
- ❖ Typically: from  $\mu\text{H}$  to several tens of Henries

### □ Current in Terms of Voltage

$$di = \frac{1}{L} v(t) dt$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

## 3.4 INDUCTANCE

### □ Stored energy

$$p(t) = v(t)i(t) = Li(t)\frac{di}{dt}$$

$$w(t) = \int_{t_0}^t p(t) dt = \int_{t_0}^t Li\frac{di}{dt} dt = \int_0^{i(t)} Li di$$



$$w(t) = \frac{1}{2}Li^2(t)$$



## 3.4 INDUCTANCE

## Example 3.6 Voltage, Power, and Energy for an Inductance

5-H inductance


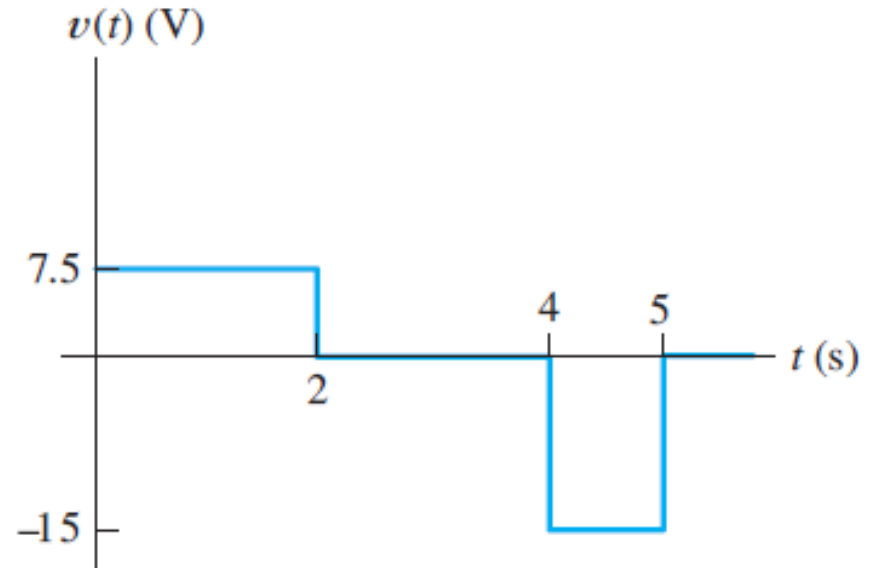
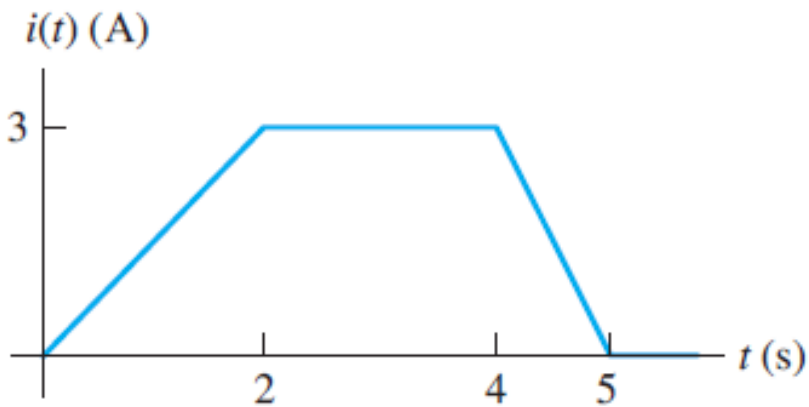




## 3.4 INDUCTANCE


## Example 3.6 Voltage, Power, and Energy for an Inductance

5-H inductance

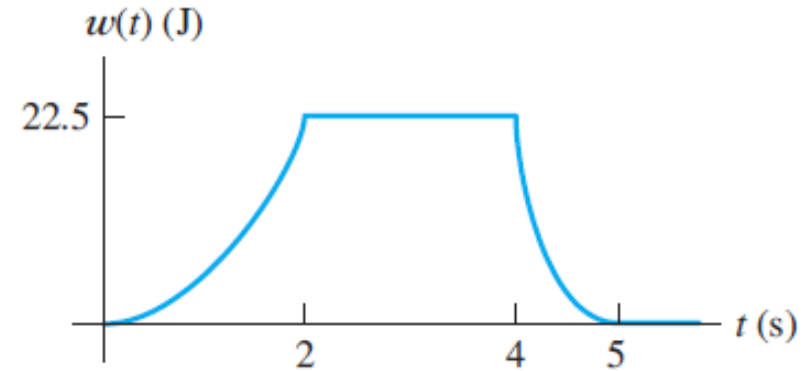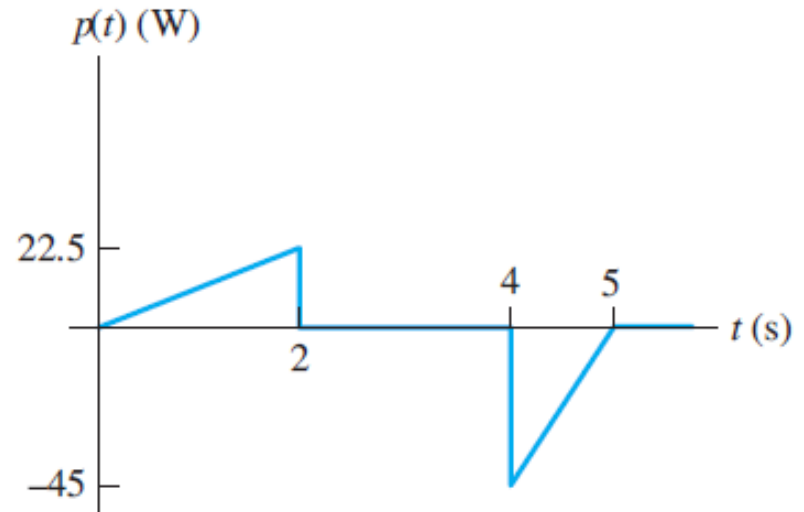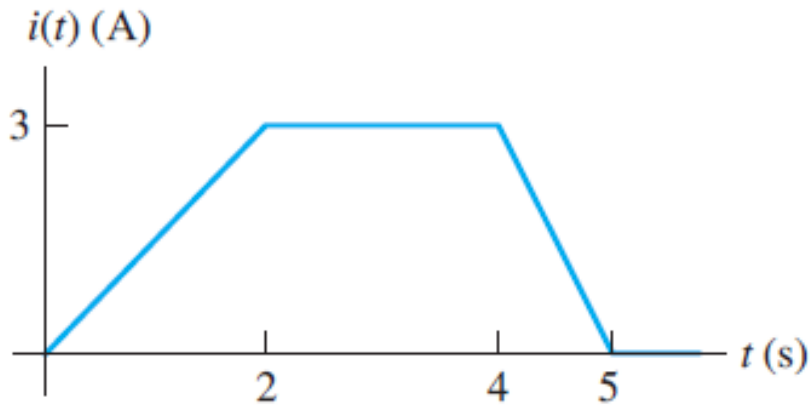


## 3.4 INDUCTANCE
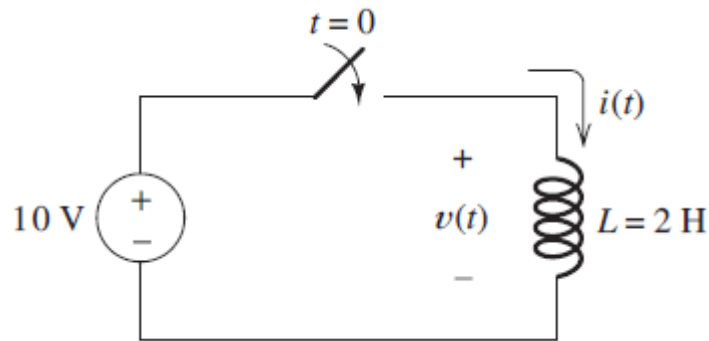
## Example 3.7 Inductor Current with Constant Applied Voltage



$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0) = \frac{1}{2} \int_0^t 10 dt$$
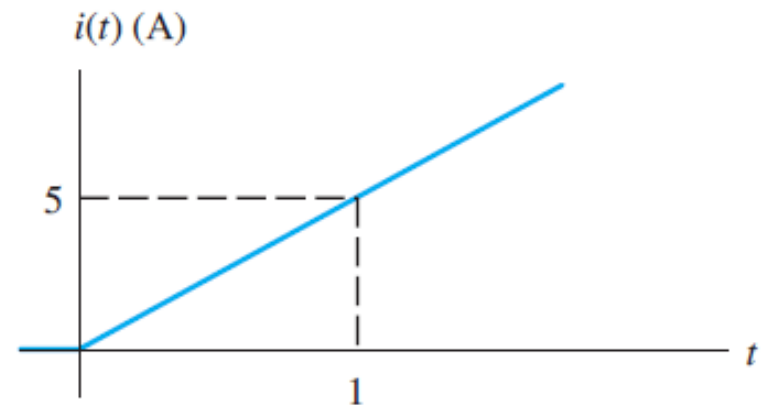
$$\Rightarrow i(t) = 5t \text{ A} \quad \text{for } t > 0$$



❖ What happens if we open switch at  $t=1\text{s}$ ??

## 3.4 INDUCTANCE

### □ Exercise

10-mH inductance

$$i(t) = 0.1 \cos(10^4 t) \text{ A.}$$

$$v(t) = L \frac{di(t)}{dt} = (10 \times 10^{-3}) \frac{d}{dt} [0.1 \cos(10^4 t)] = -10 \sin(10^4 t) \text{ V}$$

$$w(t) = \frac{1}{2} L i^2(t) = 5 \times 10^{-3} \times [0.1 \cos(10^4 t)]^2 = 50 \times 10^{-6} \cos^2(10^4 t) \text{ J}$$



## 3.4 INDUCTANCE

□ Exercise 150- $\mu$ H inductance

$$i(t) = \frac{1}{L} \int_0^t v(x) dx + i(0) = \frac{1}{150 \times 10^{-6}} \int_0^t v(x) dx$$

for  $0 \leq t \leq 2 \mu\text{s}$



$$= 6667 \int_0^t 7.5 \times 10^6 x dx = 25 \times 10^9 t^2 \text{ V}$$

for  $2 \mu\text{s} \leq t \leq 4 \mu\text{s}$

$$= 6667 \int_0^{2 \times 10^{-6}} 7.5 \times 10^6 x dx = 0.1 \text{ V}$$


for  $4 \mu\text{s} \leq t \leq 5 \mu\text{s}$
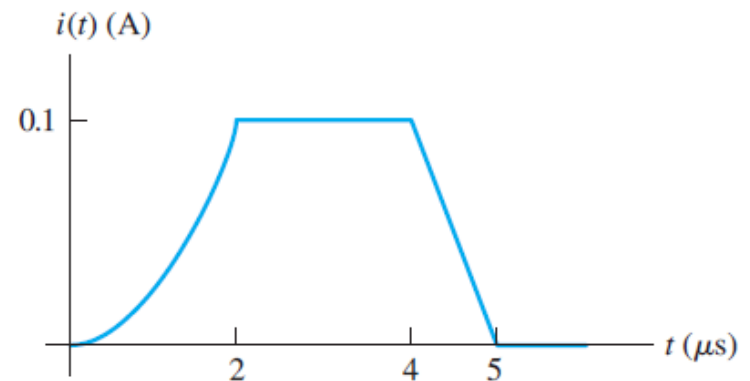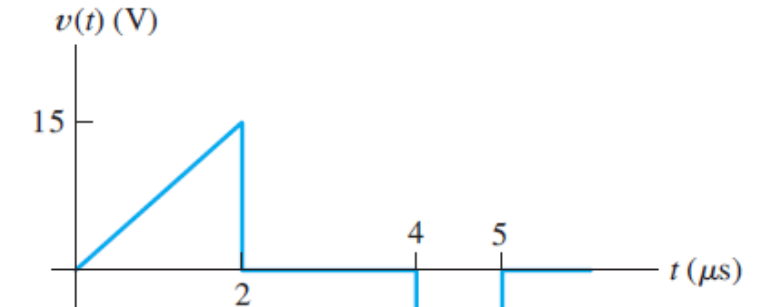
$$= 6667 \left( \int_0^{2 \times 10^{-6}} 7.5 \times 10^6 x dx + \int_{4 \times 10^{-6}}^t (-15) dx \right) = 0.5 - 10^5 t \text{ V}$$




### 3.5 INDUCTANCES IN SERIES AND PARALLEL

#### □ Series inductances

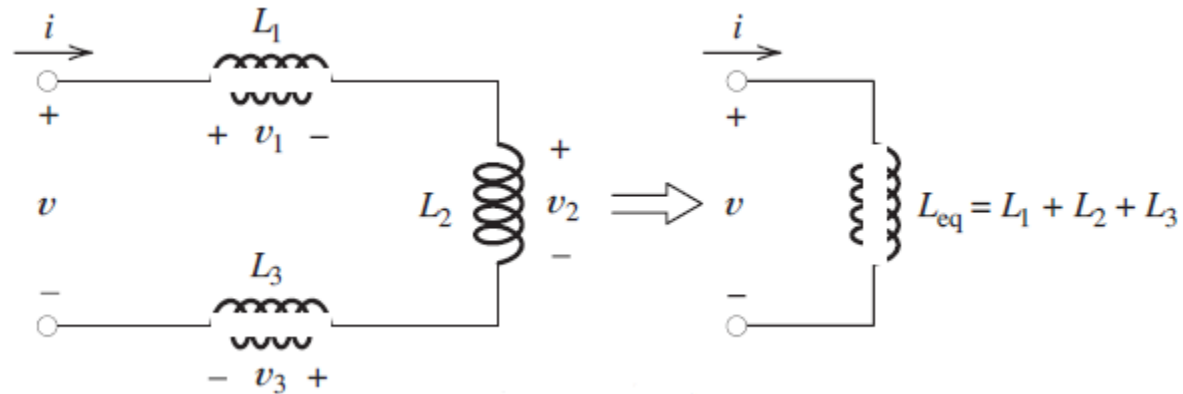


#### □ Parallel inductances

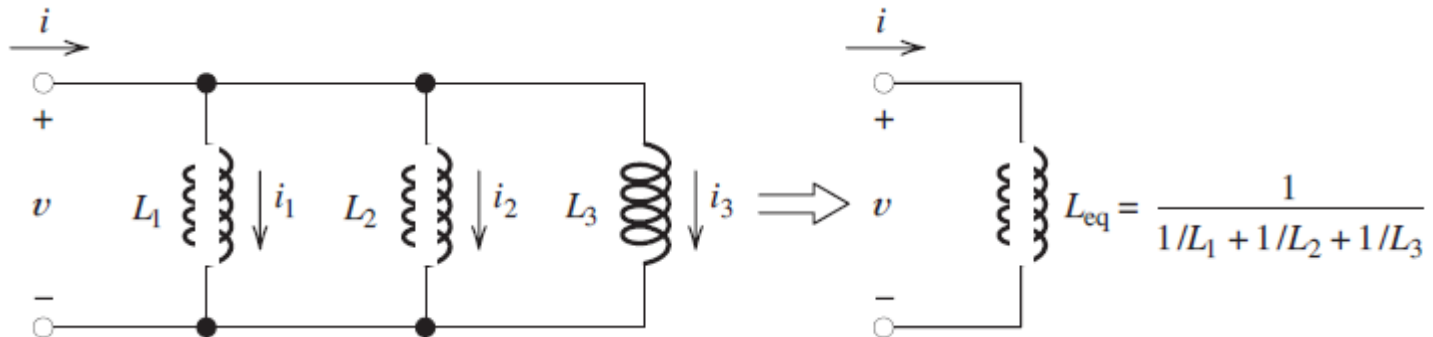


### 3.5 INDUCTANCES IN SERIES AND PARALLEL

#### □ Exercise

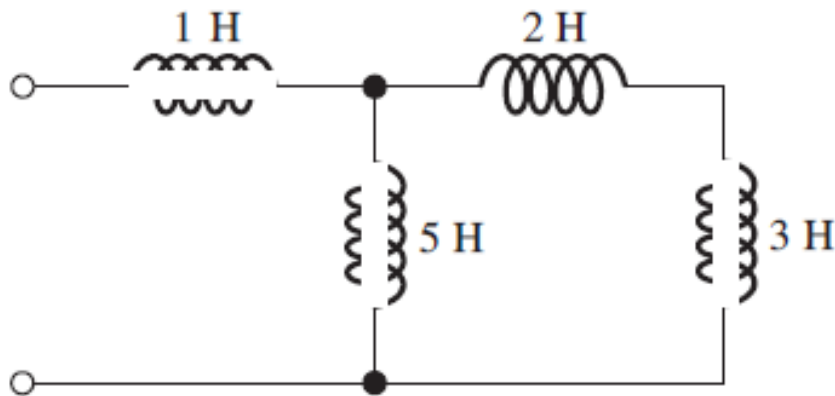

(a)

**a. 3.5 H;**

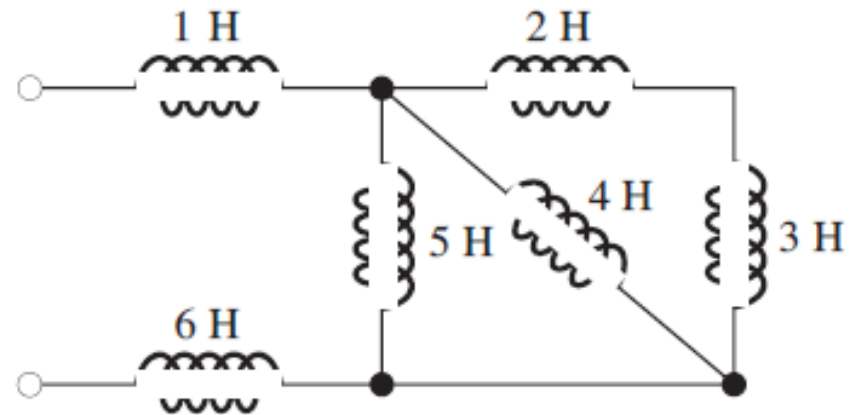


(b)

**b. 8.54 H.**

## 3.6 PRACTICAL INDUCTORS
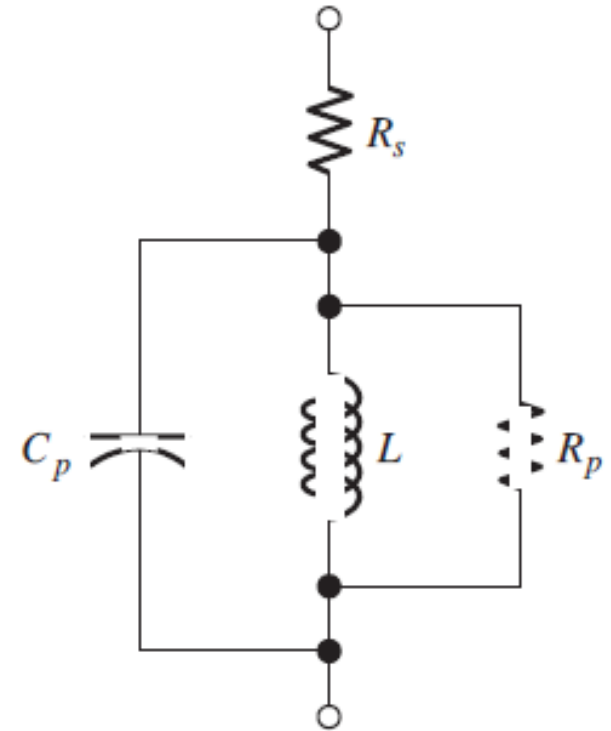
### □ Parasitic Effects

- ❖ Resistivity of the material composing the wire
- ❖ Electric field in the dielectric between the coils
- ❖ Core loss (e.g. eddy currents)




## 3.6 PRACTICAL INDUCTORS



## PRACTICAL APPLICATION 3.1

## Electronic Photo Flash

Thévenin model  
of battery

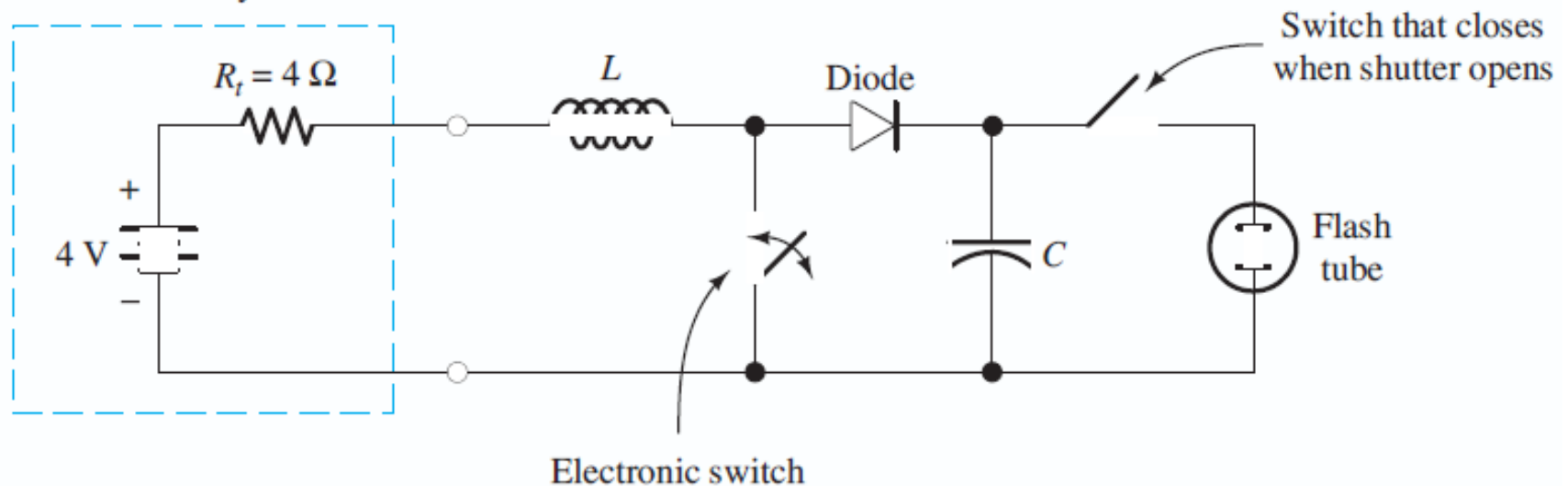




### 3.7 MUTUAL INDUCTANCE

- ❑ Several coils are wound on the same form
- ❑ Magnetic flux produced by one coil links the others
- ❑ Time-varying current in one coil induces voltages in the others
- ❑ Can either aid or oppose the flux produced by the other coil


❖ **Self inductances: L**

**Mutual inductances: M**

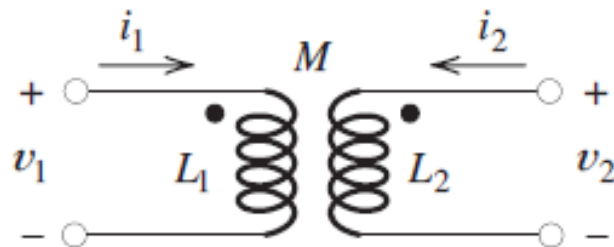

$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
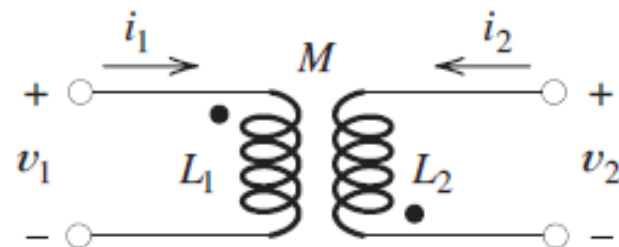
$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

### 3.7 MUTUAL INDUCTANCE

#### □ Linear Variable Differential Transformer (LVDT)


❖ Application of mutual inductance in a position transducer

When the iron core is centered

$$v_o(t) = 0.$$

As the core moves

$$v_o(t) = Kx \cos(\omega t)$$

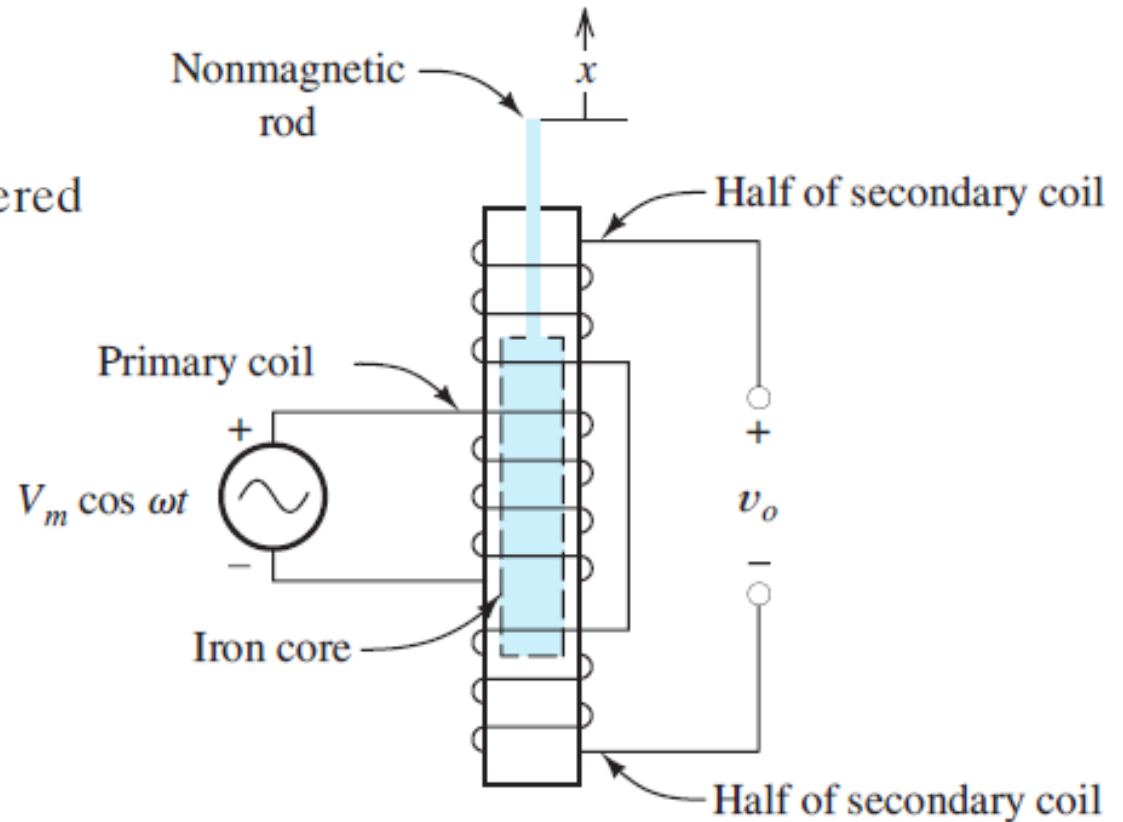

## EXERCISES

□ P3.5

□ P3.16

□ P3.24

□ P3.32

□ P3.43

□ P3.44

□ P3.45

□ P3.60

□ P3.61

□ P3.72

□ T3.1

□ T3.2

□ T3.3

□ T3.4

□ T3.5

□ T3.6

