



دانشگاه سمنان

Semnan University  
Faculty of Mechanical Engineering

دانشکده مهندسی مکانیک



دانشکده مهندسی مکانیک

درس مبانی برق ۱


نیمسال اول ۹۸-۹۹

# ELECTRICAL ENGINEERING

PRINCIPLES AND APPLICATIONS

Allan R. Hambley

5<sup>th</sup> Edition

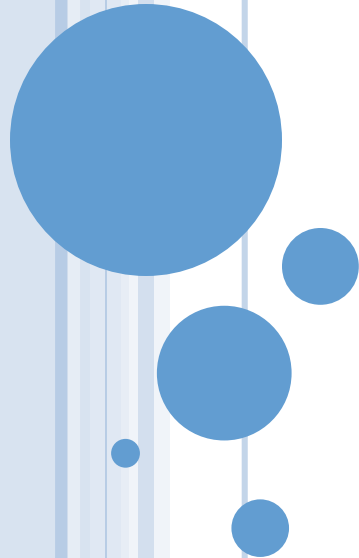

□ **CONTENTS:**

- ❖ Chapter 1: Introduction
- ❖ Chapter 2: **Resistive Circuits**
- ❖ Chapter 3: Inductance and Capacitance
- ❖ Chapter 4: Transients
- ❖ Chapter 5: Steady-State Sinusoidal Analysis



## INTRODUCTION

- ❑ Network analysis
- ❑ Voltage-division and current-division principles
- ❑ Node-voltage technique
- ❑ Mesh-current technique
- ❑ Thévenin and Norton equivalents
- ❑ Use MATLAB<sup>®</sup> to solve circuit equations
- ❑ Superposition principle



## 2.1 RESISTANCES IN SERIES AND PARALLEL

### □ Series Resistances

$$v_1 = R_1 i$$

$$v_2 = R_2 i$$


$$v_3 = R_3 i$$

#### ❖ KVL:

$$v = v_1 + v_2 + v_3$$

$$= R_1 i + R_2 i + R_3 i$$

$$= (R_1 + R_2 + R_3) i$$

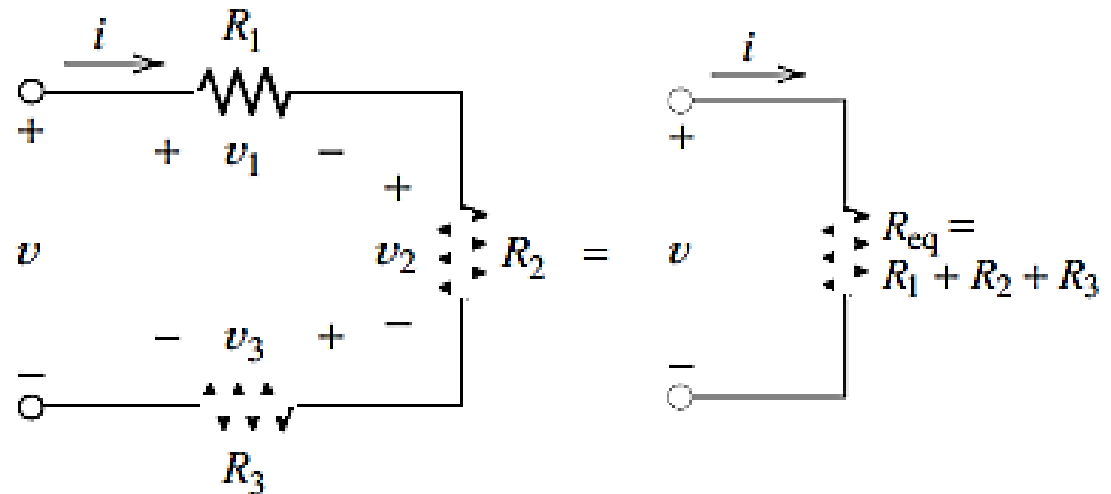

#### ❖ Equivalent Resistance:

$$v = R_{eq} i$$

$$R_{eq} = R_1 + R_2 + R_3$$

## 2.1 RESISTANCES IN SERIES AND PARALLEL

### □ Parallel Resistances

$$i_1 = \frac{v}{R_1}$$

$$i_2 = \frac{v}{R_2}$$

$$i_3 = \frac{v}{R_3}$$

❖ KCL:

$$i = i_1 + i_2 + i_3 = \frac{v}{R_1} + \frac{v}{R_2} + \frac{v}{R_3}$$



$$= \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v$$

❖ Equivalent Resistance

$$i = \frac{1}{R_{eq}} v$$


$$R_{eq} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

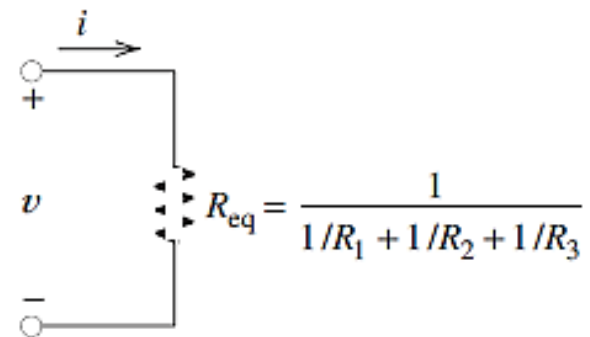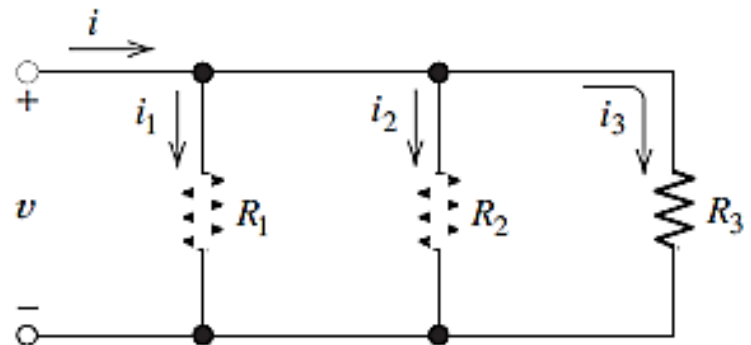


## 2.1 RESISTANCES IN SERIES AND PARALLEL

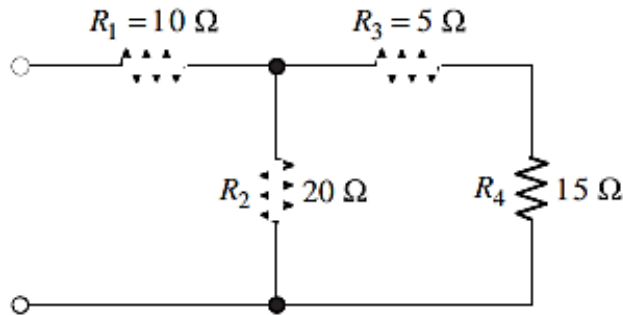
### Example 2.1 Combining Resistances in Series and Parallel




(a) Original network

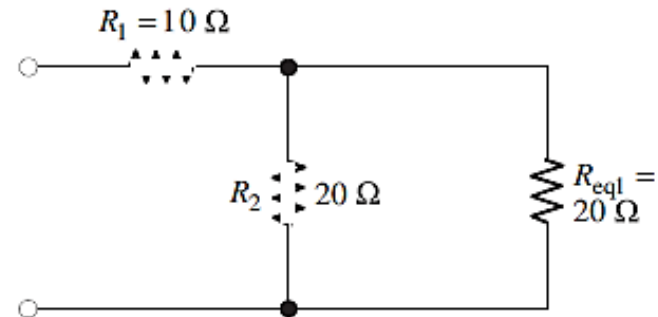

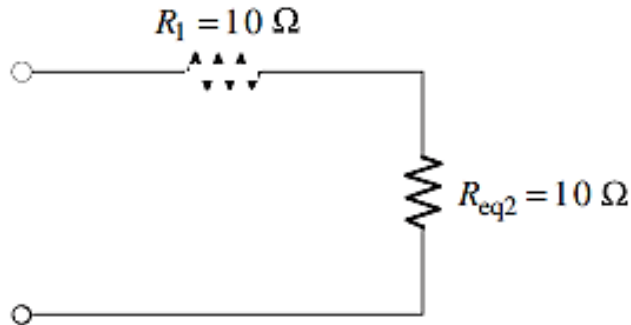(b) Network after replacing  $R_3$  and  $R_4$  by their equivalent resistance






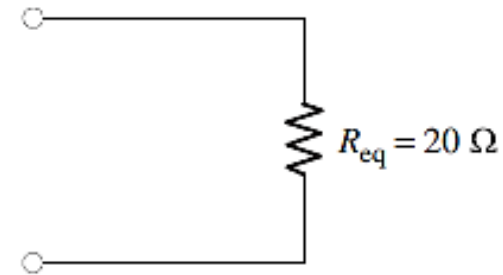
(c) Network after replacing  $R_2$  and  $R_{eq1}$  by their equivalent



(d) Combining  $R_1$  and  $R_{eq2}$  in series yields the equivalent resistance of the entire network

## 2.1 RESISTANCES IN SERIES AND PARALLEL

### □ Exercise

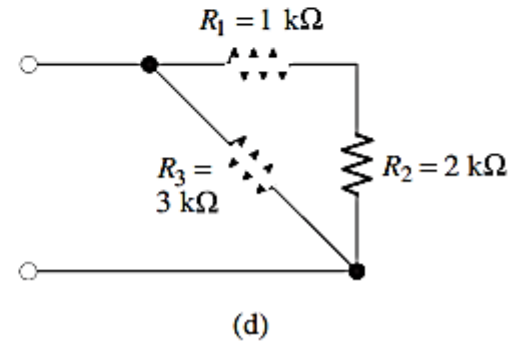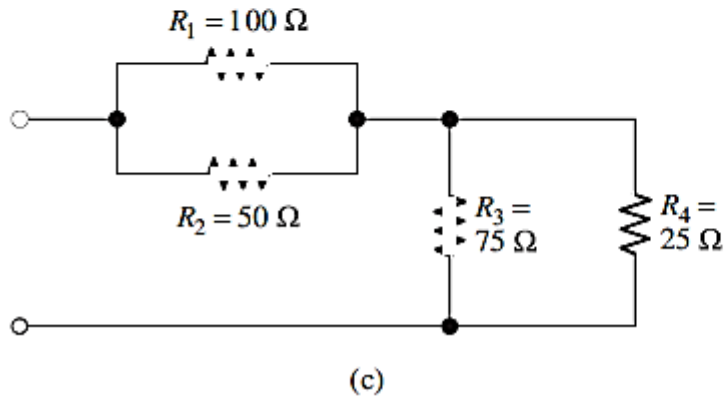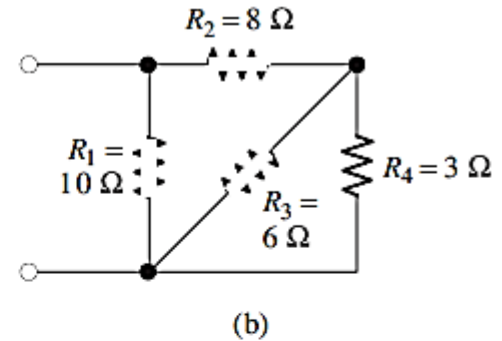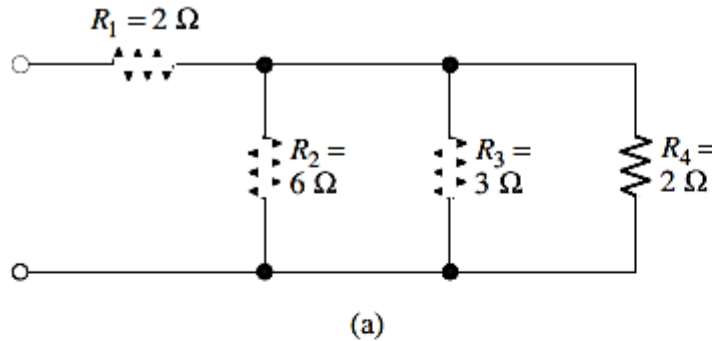

**a.  $3 \Omega$ ; b.  $5 \Omega$ ; c.  $52.1 \Omega$ ; d.  $1.5 \text{ k}\Omega$ .**

## 2.1 RESISTANCES IN SERIES AND PARALLEL

### □ Conductances in Series and Parallel

#### ❖ Series

$$G_{\text{eq}} = \frac{1}{1/G_1 + 1/G_2 + \cdots + 1/G_n}$$

#### ❖ Parallel

$$G_{\text{eq}} = G_1 + G_2 + \cdots + G_n$$

### □ Series versus Parallel Circuits

#### ❖ Parallel: Distribute power from single voltage source

#### ❖ Series





## 2.2 NETWORK ANALYSIS BY USING SERIES AND PARALLEL EQUIVALENTS


### □ Circuit Analysis Using Series/Parallel Equivalents

- ❖ 1. Locating a combination of series or parallel resistances
- ❖ 2. Redraw the circuit with the equivalent resistances
- ❖ 3. Repeat steps 1 and 2
- ❖ 4. Solve final equivalent circuit, transfer results back
- ❖ 5. Check your results for KCL and KVL







## 2.2 NETWORK ANALYSIS BY USING SERIES AND PARALLEL EQUIVALENTS
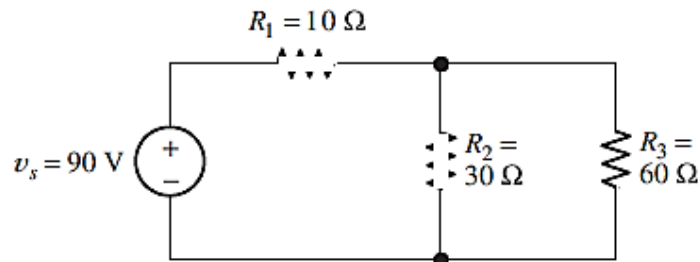
### Example 2.2 Circuit Analysis Using Series/Parallel Equivalents




(a) Original circuit

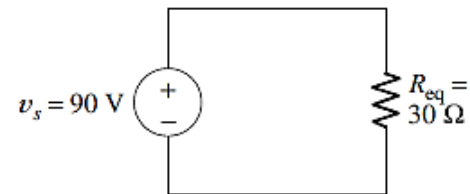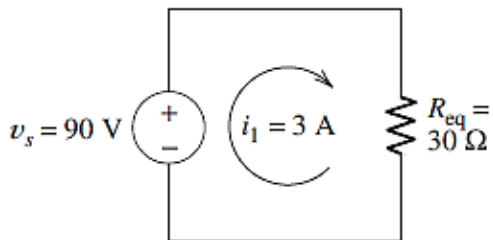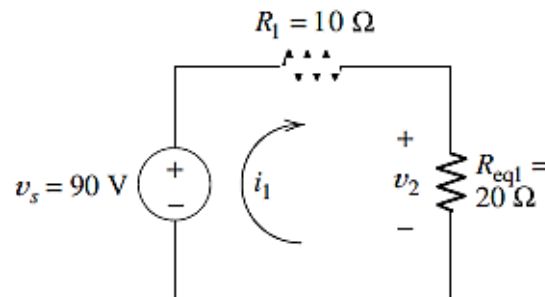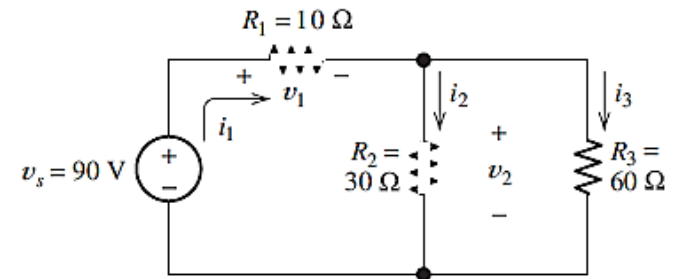(c) Circuit after replacing  $R_1$  and  $R_{eq1}$  by their equivalent(c) First, we solve for  $i_1 = \frac{v_s}{R_{eq}} = 3 \text{ A}$ (b) Second, we find  $v_2 = R_{eq1} i_1 = 60 \text{ V}$ (a) Third, we use known values of  $i_1$  and  $v_2$  to solve for the remaining currents and voltages


## 2.2 NETWORK ANALYSIS BY USING SERIES AND PARALLEL EQUIVALENTS

### □ Exercise

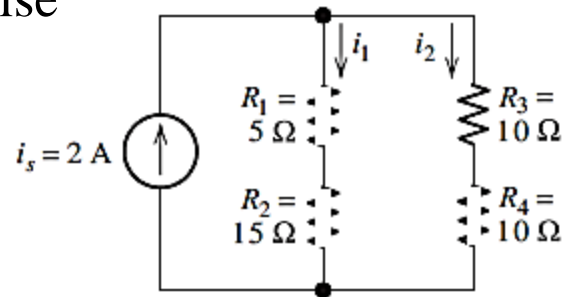


(b)

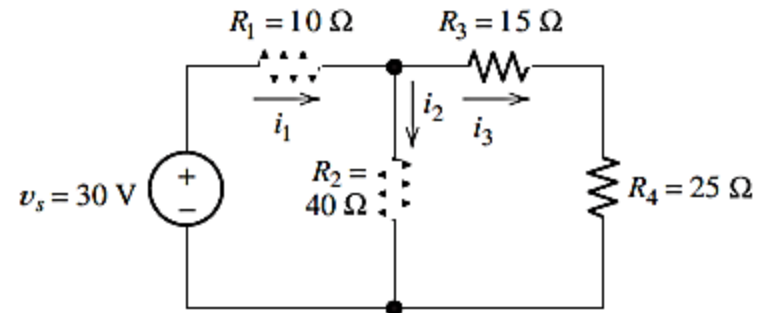**b.**  $i_1 = 1 \text{ A}, i_2 = 1 \text{ A}$



(c)

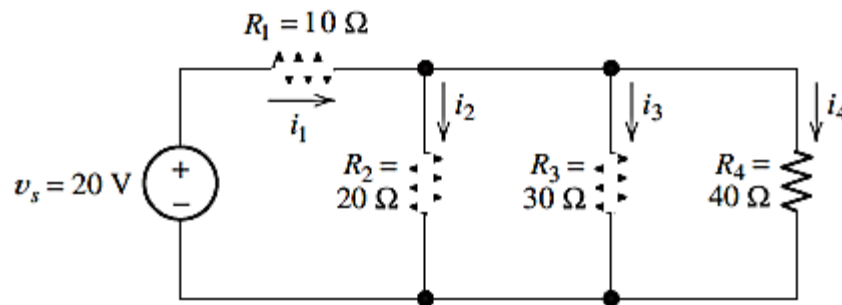**c.**  $i_1 = 1 \text{ A}, i_2 = 0.5 \text{ A}, i_3 = 0.5 \text{ A}$ .



(a)

**a.**  $i_1 = 1.04 \text{ A}, i_2 = 0.480 \text{ A}, i_3 = 0.320 \text{ A}, i_4 = 0.240 \text{ A}$

## 2.3 VOLTAGE-DIVIDER AND CURRENT-DIVIDER CIRCUITS


### □ Voltage Division

$$i = \frac{v_{\text{total}}}{R_{\text{eq}}} = \frac{v_{\text{total}}}{R_1 + R_2 + R_3}$$

$$v_1 = R_1 i = \frac{R_1}{R_1 + R_2 + R_3} v_{\text{total}}$$

$$v_2 = R_2 i = \frac{R_2}{R_1 + R_2 + R_3} v_{\text{total}}$$
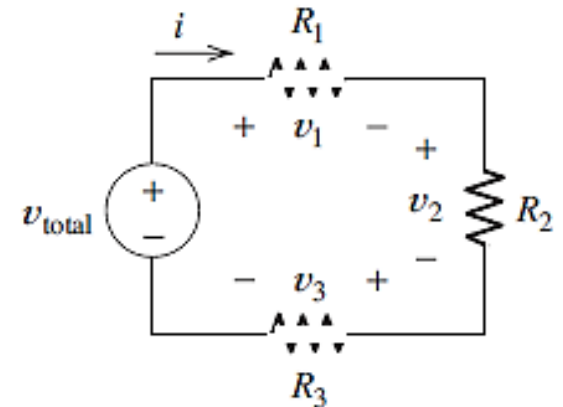
$$v_3 = R_3 i = \frac{R_3}{R_1 + R_2 + R_3} v_{\text{total}}$$




#### ❖ Voltage-division principle:

The Voltage fraction that appears across a given resistance in a series circuit is the ratio of the given resistance to the total series resistance.

## 2.3 VOLTAGE-DIVIDER AND CURRENT-DIVIDER CIRCUITS
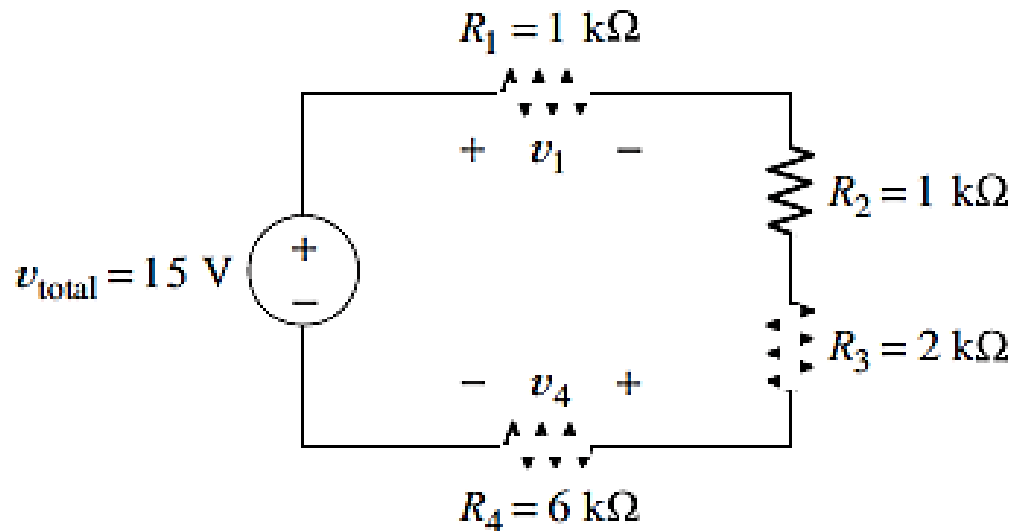
### Example 2.3 Application of the Voltage-Division Principle



$$V_1 = 1.5\text{ V}$$

$$V_2 = 1.5\text{ V}$$

$$V_1 = 3\text{ V}$$

$$V_1 = 9\text{ V}$$


## 2.3 VOLTAGE-DIVIDER AND CURRENT-DIVIDER CIRCUITS

### □ Current Division

$$v = R_{eq} i_{total} = \frac{R_1 R_2}{R_1 + R_2} i_{total}$$

$$i_1 = \frac{v}{R_1} = \frac{R_2}{R_1 + R_2} i_{total}$$
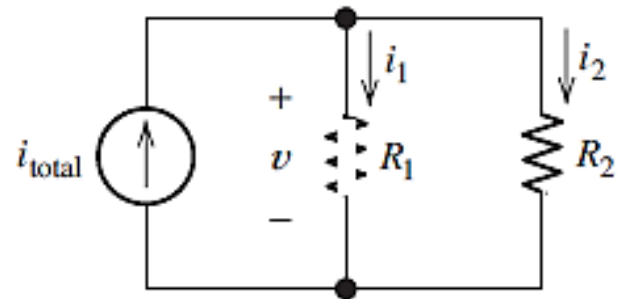
$$i_2 = \frac{v}{R_2} = \frac{R_1}{R_1 + R_2} i_{total}$$



#### ❖ Current-division principle:

The fraction of the total current owing in a resistance is the ratio of the other resistance to the sum of the two resistances.


#### ❖ Using Conductances:

$$i_1 = \frac{G_1}{G_1 + G_2 + \dots + G_n} i_{total}$$


$$i_2 = \frac{G_2}{G_1 + G_2 + \dots + G_n} i_{total}$$

## 2.3 VOLTAGE-DIVIDER AND CURRENT-DIVIDER CIRCUITS
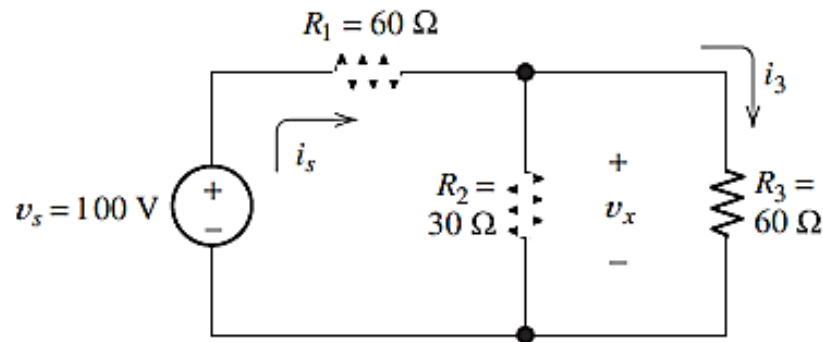
## Example 2.4 Applying the Current- and Voltage-Division Principles



(a) Original circuit

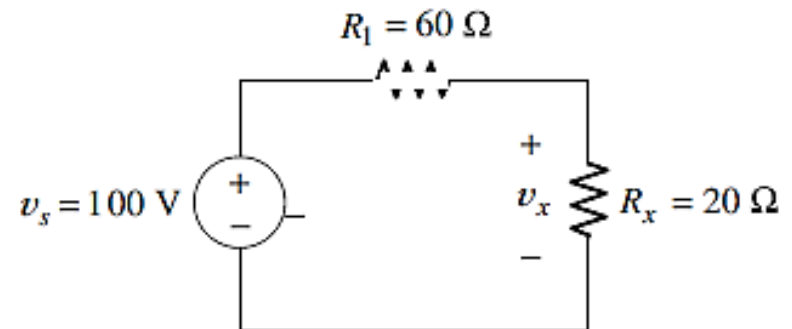


$$R_x = \frac{R_2 R_3}{R_2 + R_3} = \frac{30 \times 60}{30 + 60} = 20 \, \Omega \quad \Rightarrow \quad v_x = \frac{R_x}{R_1 + R_x} v_s = \frac{20}{60 + 20} \times 100 = 25 \, \text{V}$$

$$i_s = \frac{v_s}{R_1 + R_x} = \frac{100}{60 + 20} = 1.25 \, \text{A} \quad \Rightarrow \quad i_3 = \frac{R_2}{R_2 + R_3} i_s = \frac{30}{30 + 60} \times 1.25 = 0.417 \, \text{A}$$

## 2.3 VOLTAGE-DIVIDER AND CURRENT-DIVIDER CIRCUITS
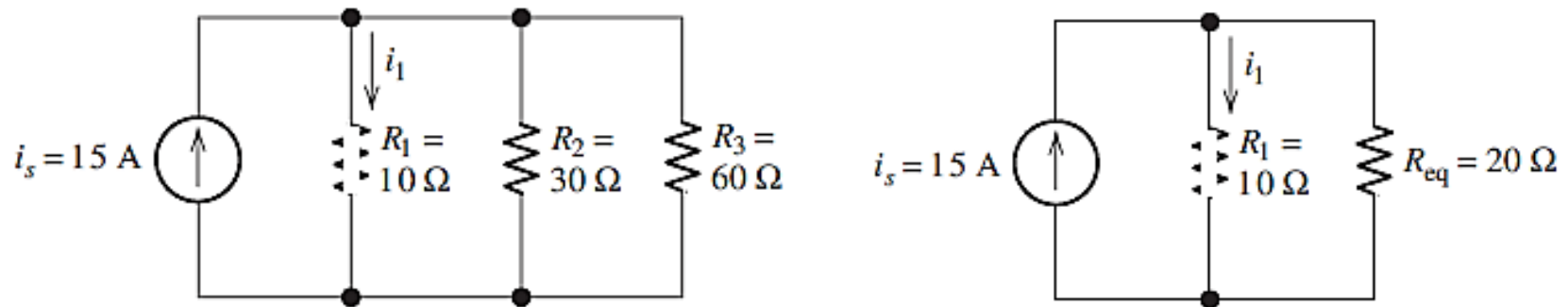
## Example 2.5 Application of the Current-Division Principle



$$R_{eq} = \frac{R_2 R_3}{R_2 + R_3} = \frac{30 \times 60}{30 + 60} = 20 \, \Omega \quad \Rightarrow \quad i_1 = \frac{R_{eq}}{R_1 + R_{eq}} i_s = \frac{20}{10 + 20} 15 = 10 \, \text{A}$$

$$G_1 = \frac{1}{R_1} = 100 \, \text{mS}, \quad G_2 = \frac{1}{R_2} = 33.33 \, \text{mS}, \quad \text{and} \quad G_3 = \frac{1}{R_3} = 16.67 \, \text{mS}$$

$$\Rightarrow i_1 = \frac{G_1}{G_1 + G_2 + G_3} i_s = \frac{100}{100 + 33.33 + 16.67} 15 = 10 \, \text{A}$$






## 2.3 VOLTAGE-DIVIDER AND CURRENT-DIVIDER CIRCUITS

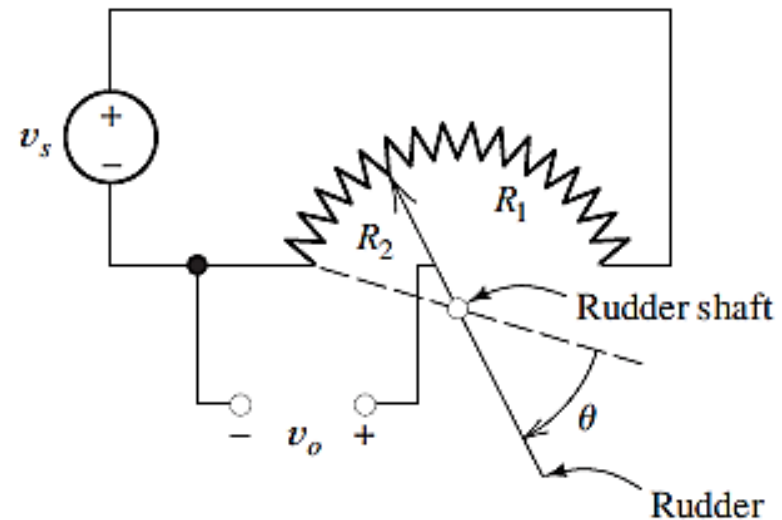
### □ Position Transducers Based on the Voltage-Division Principle

$$v_o = v_s \frac{R_2}{R_1 + R_2} = K\theta$$




## 2.3 VOLTAGE-DIVIDER AND CURRENT-DIVIDER CIRCUITS

## □ Exercise

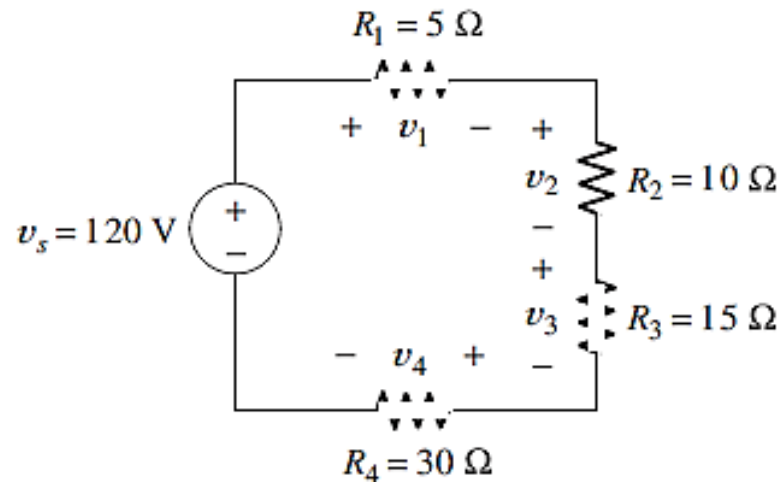

(a)

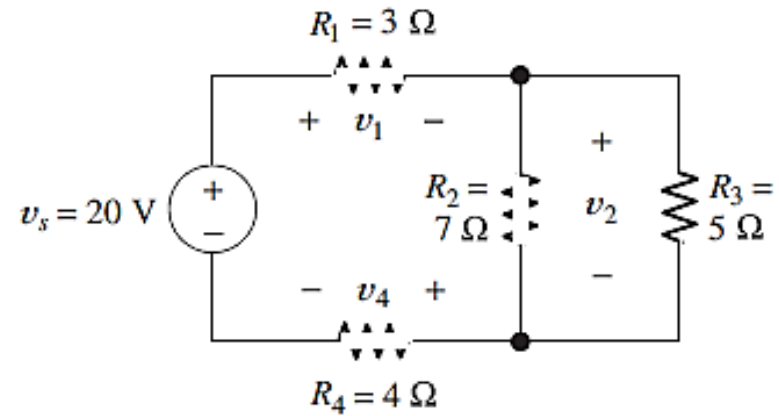a.  $v_1 = 10\text{ V}$ ,  $v_2 = 20\text{ V}$ ,  $v_3 = 30\text{ V}$ ,  $v_4 = 60\text{ V}$ ;




(b)

b.  $v_1 = 6.05\text{ V}$ ,  $v_2 = 5.88\text{ V}$ ,  $v_4 = 8.07\text{ V}$ .


## 2.3 VOLTAGE-DIVIDER AND CURRENT-DIVIDER CIRCUITS

## □ Exercise

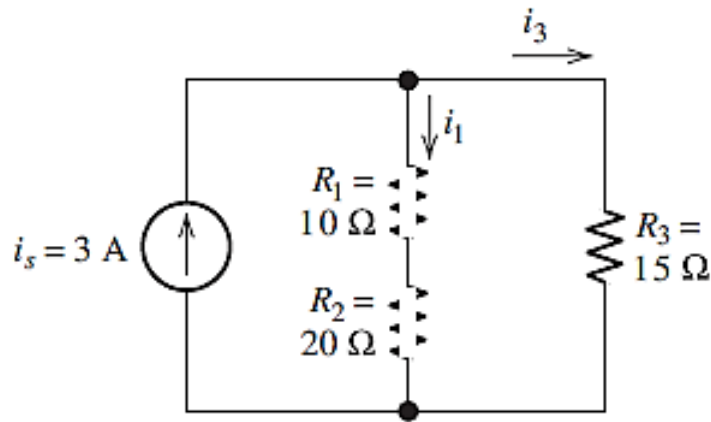

(a)

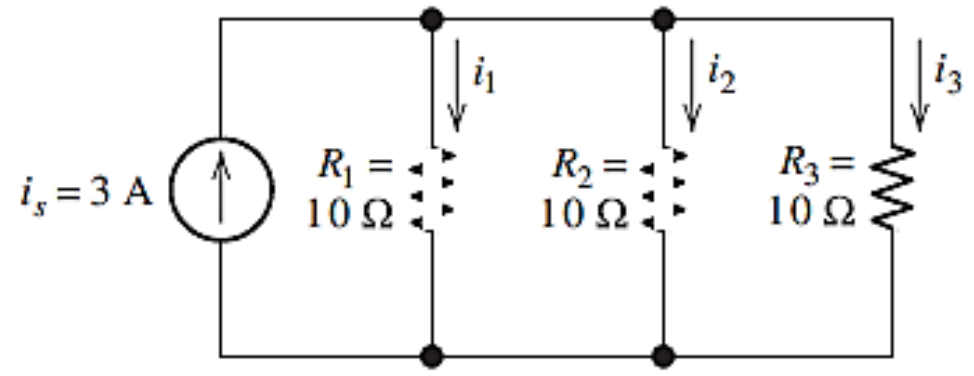**a.**  $i_1 = 1 \text{ A}, i_3 = 2 \text{ A}$



(b)


**b.**  $i_1 = i_2 = i_3 = 1 \text{ A}$ .

## 2.4 NODE-VOLTAGE ANALYSIS

- ❑ Selecting the Reference Node
- ❑ Assigning Node Voltages
- ❑ Finding Element Voltages in Terms of the Node Voltages
- ❑ Writing KCL Equations in Terms of the Node Voltages

$$v_x = v_2 - v_3$$

$$\frac{v_n - v_k}{R}$$

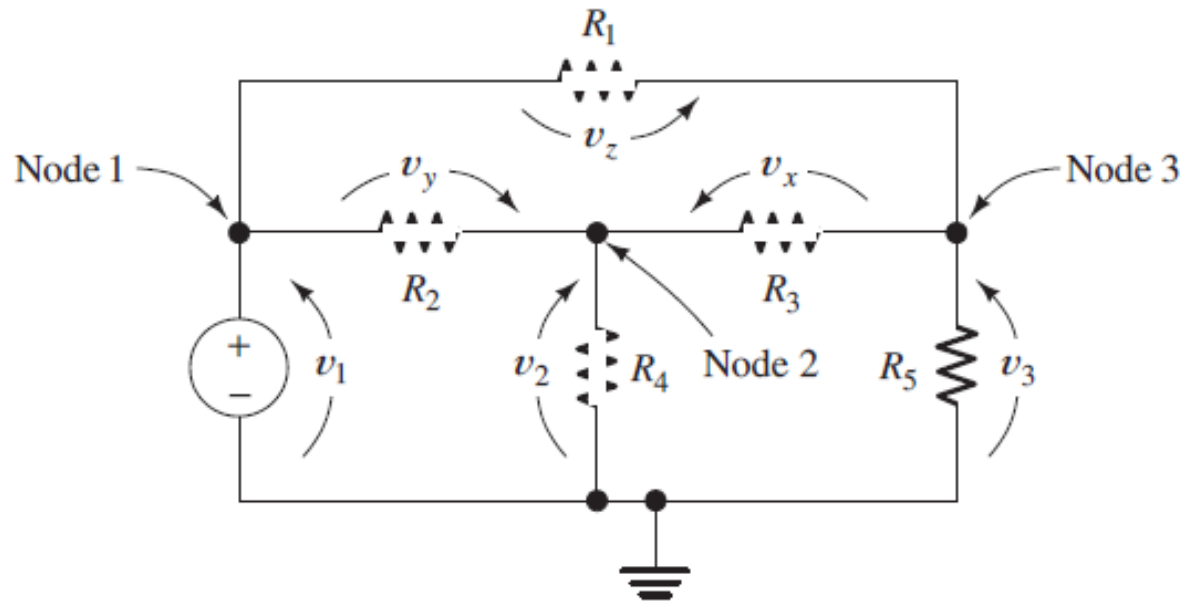

## 2.4 NODE-VOLTAGE ANALYSIS


### Example 2.6 Node-Voltage Analysis

❖ KCL for nodes 1, 2 and 3:

$$\frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} + i_s = 0$$


$$\frac{v_2 - v_1}{R_2} + \frac{v_2}{R_3} + \frac{v_2 - v_3}{R_4} = 0$$
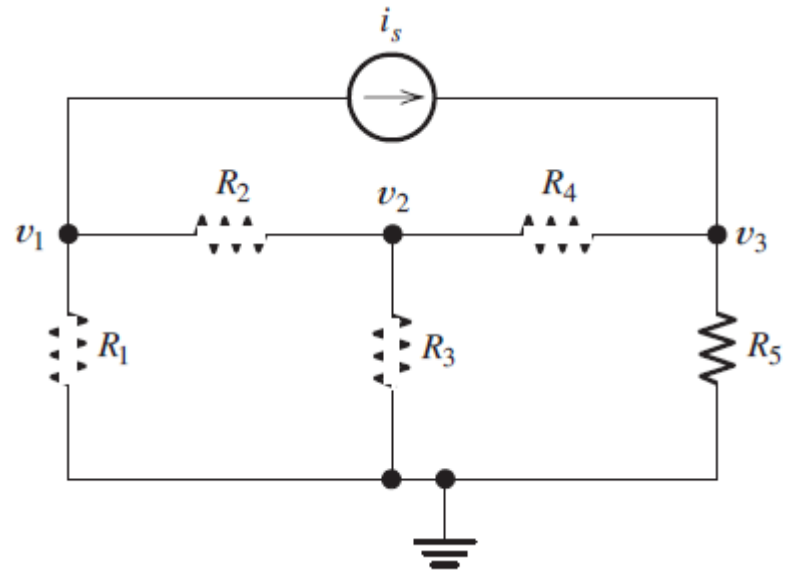
$$\frac{v_3}{R_5} + \frac{v_3 - v_2}{R_4} = i_s$$



## 2.4 NODE-VOLTAGE ANALYSIS

### □ Exercise

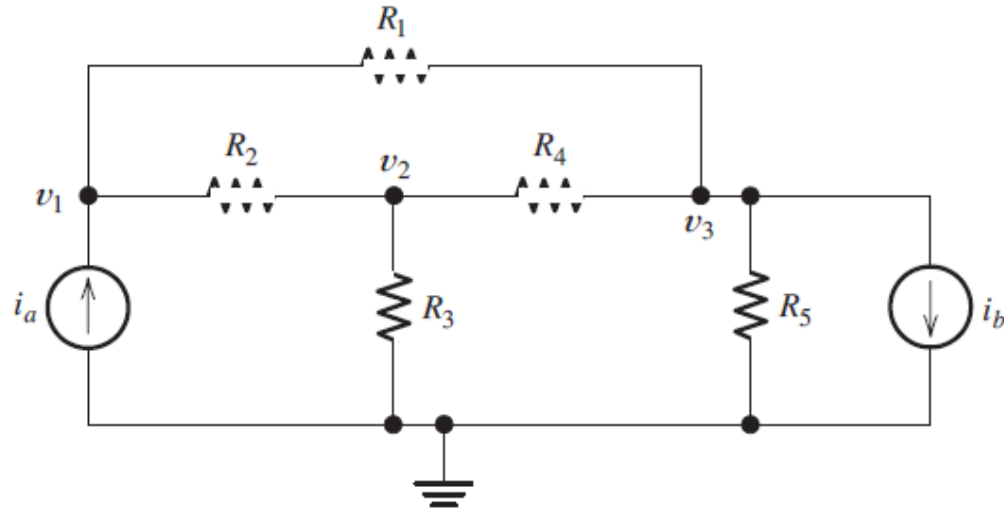

$$\text{Node 1: } \frac{v_1 - v_3}{R_1} + \frac{v_1 - v_2}{R_2} = i_a$$

$$\text{Node 2: } \frac{v_2 - v_1}{R_2} + \frac{v_2}{R_3} + \frac{v_2 - v_3}{R_4} = 0$$

$$\text{Node 3: } \frac{v_3}{R_5} + \frac{v_3 - v_2}{R_4} + \frac{v_3 - v_1}{R_1} + i_b = 0$$

## 2.4 NODE-VOLTAGE ANALYSIS

### □ Circuit Equations in Standard Form

❖ For two node voltages:

$$g_{11}v_1 + g_{12}v_2 = i_1$$

$$g_{21}v_1 + g_{22}v_2 = i_2$$

❖ For three node voltages:

$$g_{11}v_1 + g_{12}v_2 + g_{13}v_3 = i_1$$

$$g_{21}v_1 + g_{22}v_2 + g_{23}v_3 = i_2$$

$$g_{31}v_1 + g_{32}v_2 + g_{33}v_3 = i_3$$

❖ Matrix form:


$$\mathbf{GV} = \mathbf{I} \qquad \mathbf{V} = \mathbf{G}^{-1}\mathbf{I}$$



## 2.4 NODE-VOLTAGE ANALYSIS
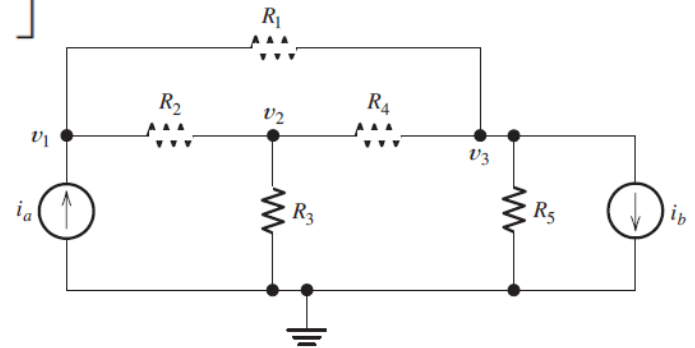
### □ A Shortcut to Writing the Matrix Equations

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & -\frac{1}{R_1} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ -\frac{1}{R_1} & -\frac{1}{R_4} & \frac{1}{R_1} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} i_a \\ 0 \\ -i_b \end{bmatrix}$$




- ❖ Diagonal elements: sum of the conductances connected to node
- ❖ Off-diagonal terms: negative of the conductance connected between node  $j$  and  $k$
- ❖ Terms in  $\mathbf{I}$  matrix: currents pushed into corresponding nodes by current sources



## 2.4 NODE-VOLTAGE ANALYSIS

### □ Exercise

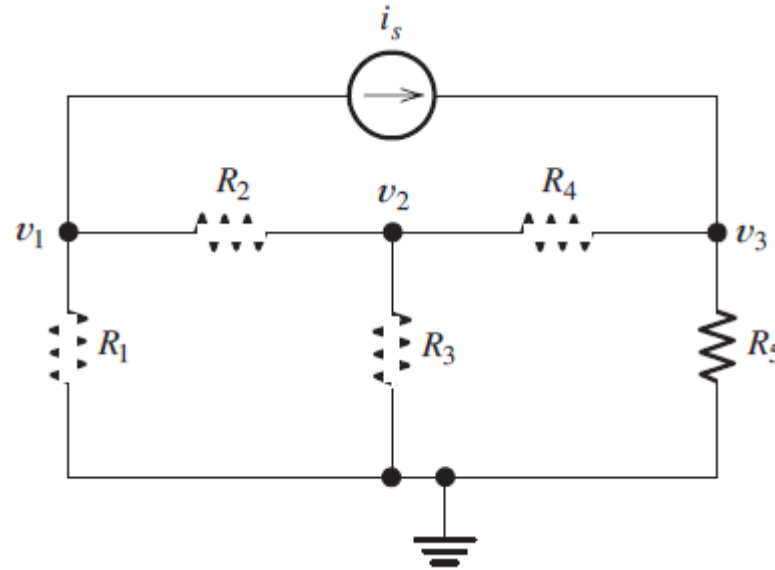

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ 0 & -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -i_s \\ 0 \\ i_s \end{bmatrix}$$


## 2.4 NODE-VOLTAGE ANALYSIS

### Example 2.7 Node-Voltage Analysis

$$\frac{v_1}{5} + \frac{v_1 - v_2}{4} + 3.5 = 0$$

$$\frac{v_2 - v_1}{4} + \frac{v_2}{2.5} + \frac{v_2 - v_3}{5} = 3.5$$
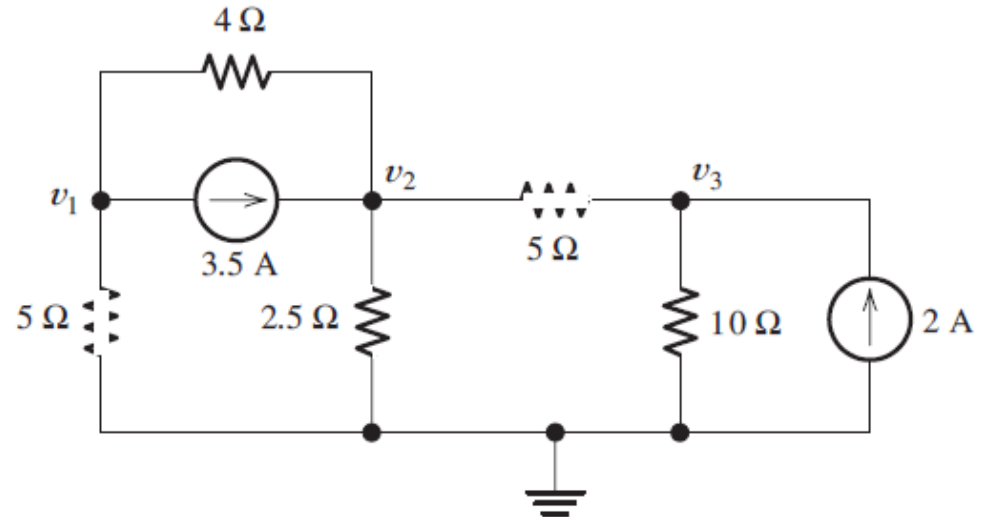
$$\frac{v_3 - v_2}{5} + \frac{v_3}{10} = 2$$



$$0.45v_1 - 0.25v_2 = -3.5$$

$$-0.25v_1 + 0.85v_2 - 0.2v_3 = 3.5$$

$$-0.2v_2 + 0.35v_3 = 2$$

$$\begin{bmatrix} 0.45 & -0.25 & 0 \\ -0.25 & 0.85 & -0.20 \\ 0 & -0.20 & 0.30 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -3.5 \\ 3.5 \\ 2 \end{bmatrix}$$

## 2.4 NODE-VOLTAGE ANALYSIS

### □ Using MATLAB to Solve Network Equations

```

>> I = [-3.5; 3.5; 2]
I =
-3.5000
 3.5000
 2.0000

>> G = [0.45 -0.25 0; -0.25 0.85 -0.2; 0 -0.2 0.30]
G =
 0.4500 -0.2500 0
-0.2500 0.8500 -0.2000
 0 -0.2000 0.3000

>> V = G\I
V =
-5.0000
 5.0000
10.0000

```

$$\begin{bmatrix} 0.45 & -0.25 & 0 \\ -0.25 & 0.85 & -0.20 \\ 0 & -0.20 & 0.30 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -3.5 \\ 3.5 \\ 2 \end{bmatrix}$$


## 2.4 NODE-VOLTAGE ANALYSIS

### Example 2.8 Node-Voltage Analysis

$$\text{Node 1: } \frac{v_1}{10} + \frac{v_1 - v_2}{5} + \frac{v_1 - v_3}{20} = 0$$


$$\text{Node 2: } \frac{v_2 - v_1}{5} + \frac{v_2 - v_3}{10} = 10$$

$$\text{Node 3: } \frac{v_3}{5} + \frac{v_3 - v_2}{10} + \frac{v_3 - v_1}{20} = 0$$

$$0.35v_1 - 0.2v_2 - 0.05v_3 = 0$$

$$\Rightarrow -0.2v_1 + 0.3v_2 - 0.10v_3 = 10$$

$$-0.05v_1 - 0.10v_2 + 0.35v_3 = 0$$

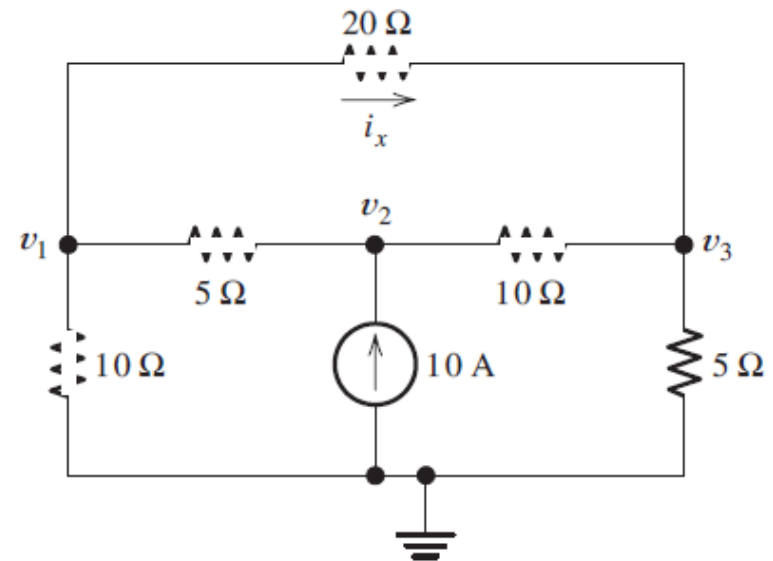

$$\Rightarrow \gg V = G \backslash I$$

$$V = \begin{matrix} 45.4545 \\ 72.7273 \\ 27.2727 \end{matrix}$$

$$\gg I_x = (V(1) - V(3)) / 20$$

$$I_x = 0.9091$$



## 2.4 NODE-VOLTAGE ANALYSIS

### □ Exercise

$$\frac{v_1 - v_3}{20} + \frac{v_1}{5} + \frac{v_1 - v_2}{10} = 0$$

$$\frac{v_2 - v_1}{10} + 10 + \frac{v_2 - v_3}{5} = 0$$


$$\frac{v_3 - v_1}{20} + \frac{v_3}{10} + \frac{v_3 - v_2}{5} = 0$$

$$0.35v_1 - 0.10v_2 - 0.05v_3 = 0$$

$$\Rightarrow -0.10v_1 + 0.30v_2 - 0.20v_3 = -10$$

$$-0.05v_1 - 0.20v_2 + 0.35v_3 = 0$$
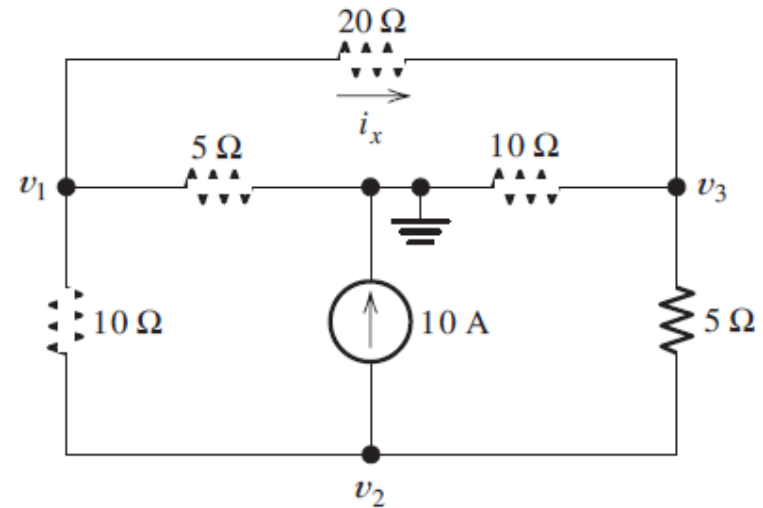
$$\Rightarrow v_1 = -27.27; v_2 = -72.73; v_3 = -45.45 \quad i_x = 0.909 \text{ A}$$



## 2.4 NODE-VOLTAGE ANALYSIS

### □ Circuits with Voltage Sources

- ❖ Pick reference node at one end of source, one less unknown node voltage


#### Example 2.9 Node-Voltage Analysis

$$\frac{v_1 - v_2}{5} + \frac{v_1 - 10}{2} = 1$$

$$\frac{v_2}{5} + \frac{v_2 - 10}{10} + \frac{v_2 - v_1}{5} = 0$$


$$\begin{aligned} \Rightarrow 0.7v_1 - 0.2v_2 &= 6 \\ -0.2v_1 + 0.5v_2 &= 1 \end{aligned}$$
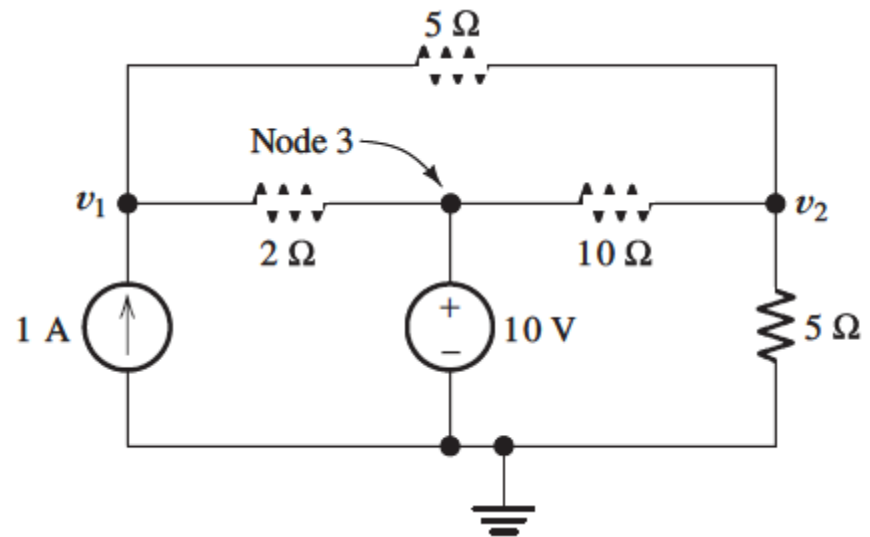
$$\Rightarrow v_1 = 10.32 \text{ V}; v_2 = 6.129 \text{ V.}$$



## 2.4 NODE-VOLTAGE ANALYSIS

### □ Exercise

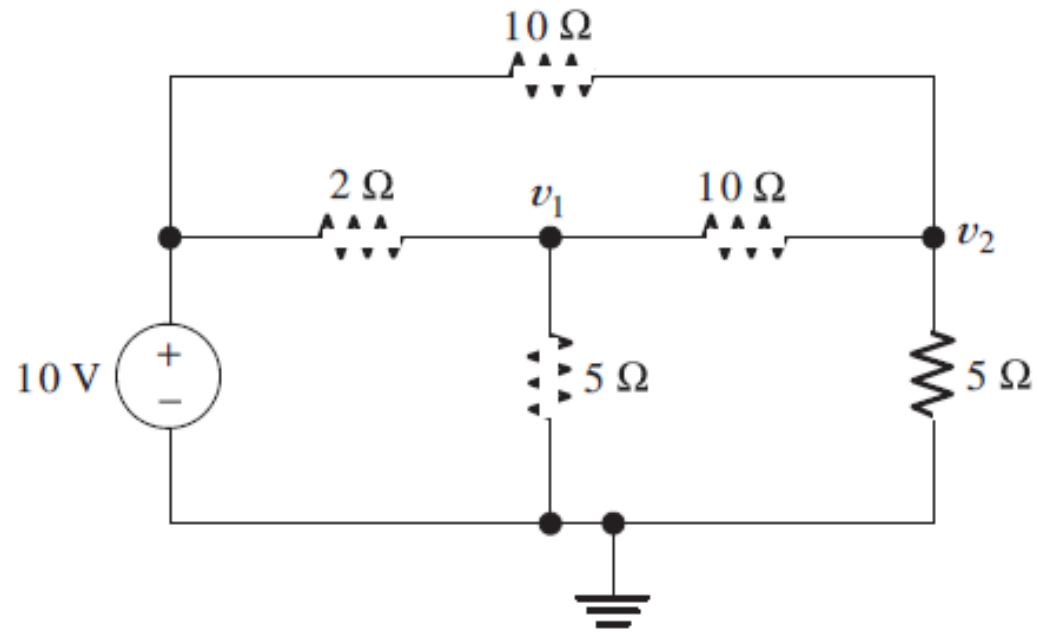


$$v_1 = 6.77 \text{ V}, v_2 = 4.19 \text{ V}.$$

## 2.4 NODE-VOLTAGE ANALYSIS
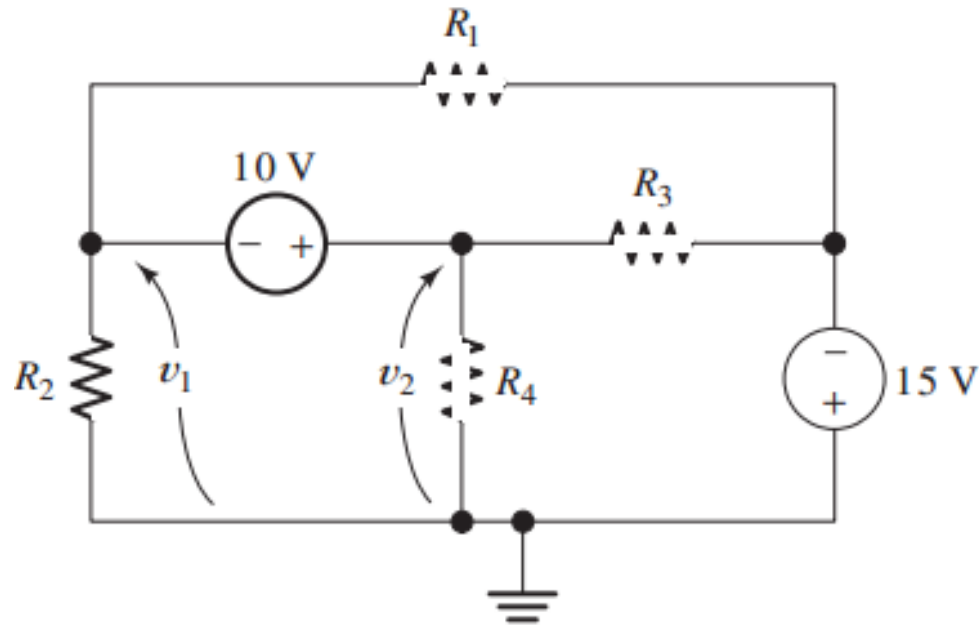
### □ Supernode


- ❖ Decrease equations order (ignore source current)
- ❖ Forming closed surface (Supernode)
- ❖ Writing KCL for Supernode





## 2.4 NODE-VOLTAGE ANALYSIS

### □ Supernode

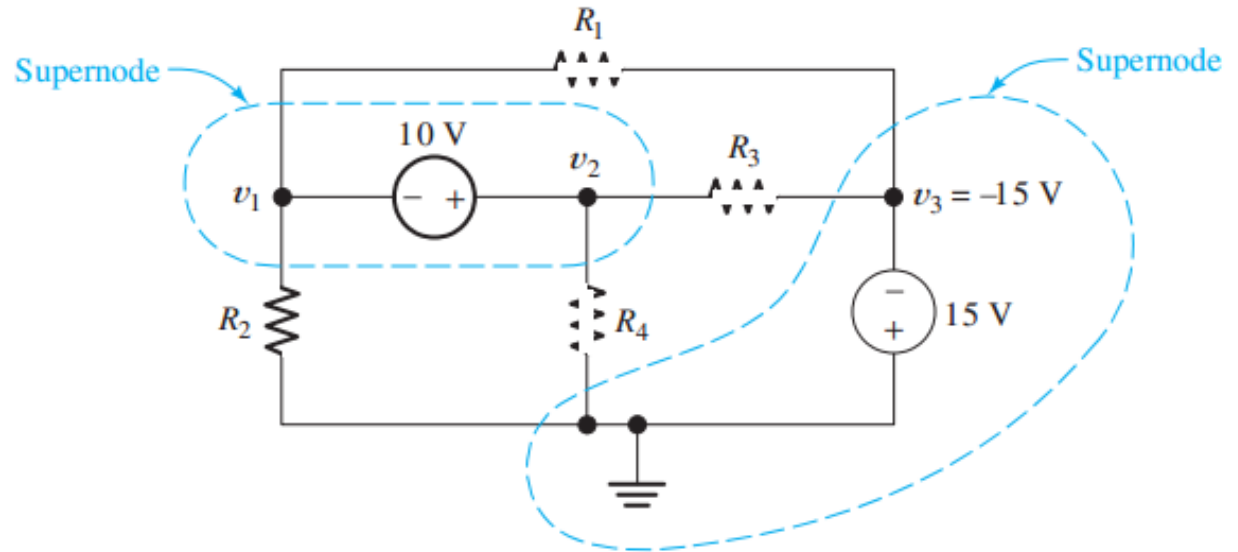

❖ KCL for Supernode:

$$\frac{v_1}{R_2} + \frac{v_1 - (-15)}{R_1} + \frac{v_2}{R_4} + \frac{v_2 - (-15)}{R_3} = 0$$

❖ KVL for 10V source:

$$-v_1 - 10 + v_2 = 0$$

## 2.4 NODE-VOLTAGE ANALYSIS

### □ Exercise:

KCL for the supernode enclosing the 10-V source:


$$\frac{v_1}{R_1} + \frac{v_1 - v_3}{R_2} + \frac{v_2 - v_3}{R_3} = 1$$

KCL for node 3:

$$\frac{v_3 - v_1}{R_2} + \frac{v_3 - v_2}{R_3} + \frac{v_3}{R_4} = 0$$

KCL at the reference node:
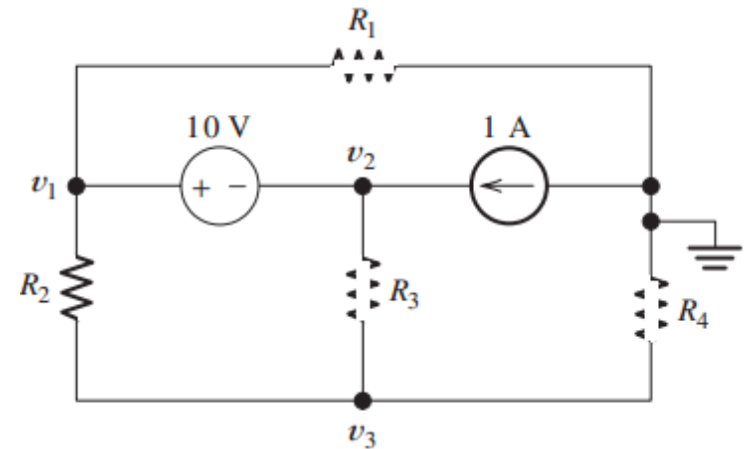
$$\frac{v_1}{R_1} + \frac{v_3}{R_4} = 1$$



$$-v_1 + 10 + v_2 = 0$$

## 2.4 NODE-VOLTAGE ANALYSIS

### □ Circuits with controlled sources


#### Example 2.10 Node-Voltage Analysis with a Dependent Source

❖ KCLs:

$$\frac{v_1 - v_2}{R_1} = i_s + 2i_x$$

$$\frac{v_2 - v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2 - v_3}{R_3} = 0$$
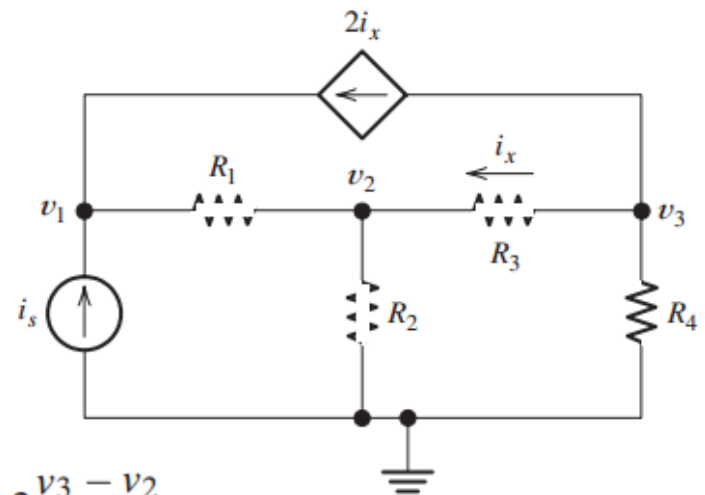
$$\frac{v_3 - v_2}{R_3} + \frac{v_3}{R_4} + 2i_x = 0$$



❖ Substituting:

$$i_x = \frac{v_3 - v_2}{R_3} \quad \Rightarrow$$

$$\frac{v_1 - v_2}{R_1} = i_s + 2 \frac{v_3 - v_2}{R_3}$$

$$\frac{v_2 - v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_2 - v_3}{R_3} = 0$$

$$\frac{v_3 - v_2}{R_3} + \frac{v_3}{R_4} + 2 \frac{v_3 - v_2}{R_3} = 0$$

## 2.4 NODE-VOLTAGE ANALYSIS

### Example 2.11 Node-Voltage Analysis with a Dependent Source


$$\frac{v_1}{R_2} + \frac{v_1 - v_3}{R_1} + \frac{v_2 - v_3}{R_3} = i_s$$

$$\frac{v_3}{R_4} + \frac{v_3 - v_2}{R_3} + \frac{v_3 - v_1}{R_1} = 0$$

$$\frac{v_1}{R_2} + \frac{v_3}{R_4} = i_s$$


$$-v_1 + 0.5v_x + v_2 = 0$$

$$v_x = v_3 - v_1$$

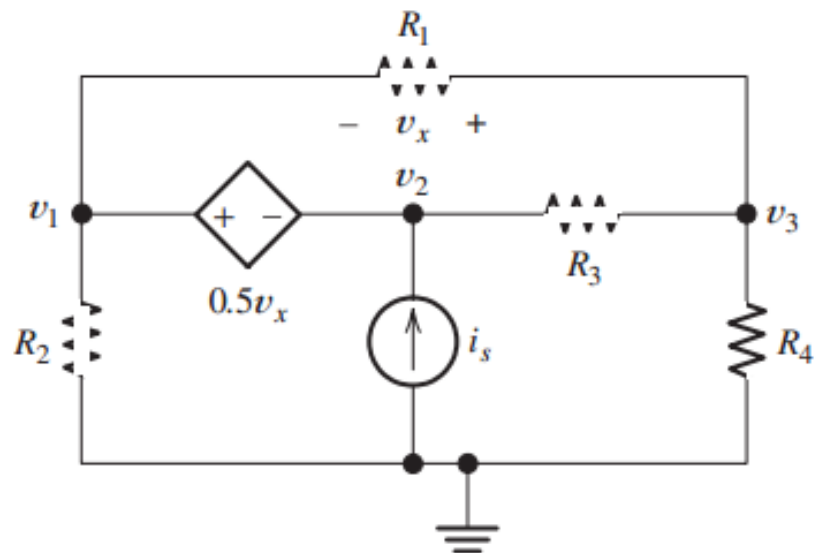


## 2.4 NODE-VOLTAGE ANALYSIS

### □ Exercise

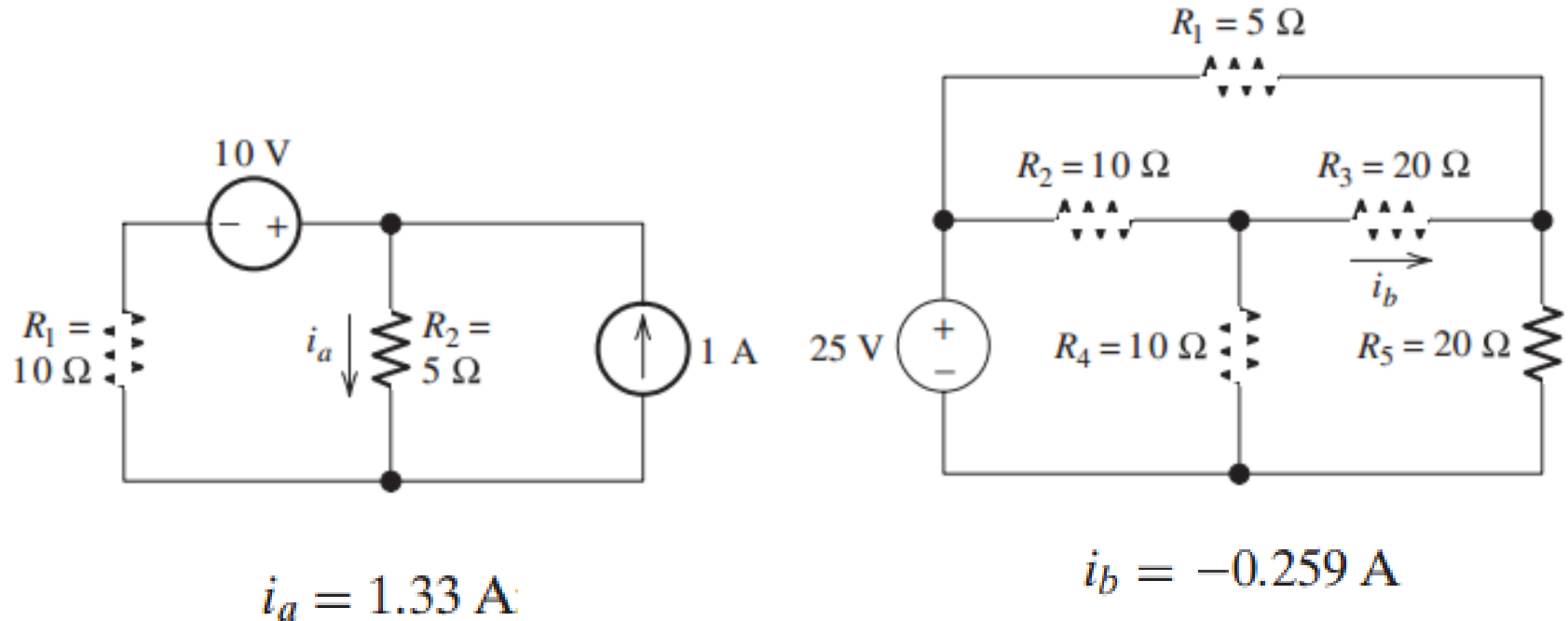


## 2.4 NODE-VOLTAGE ANALYSIS

### □ Exercise

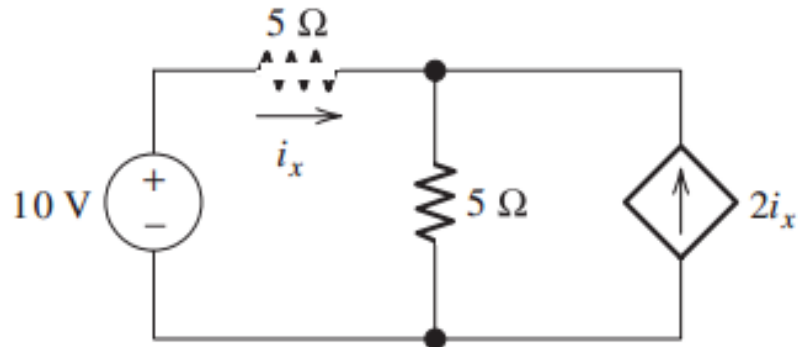


$$i_x = 0.5 \text{ A}$$

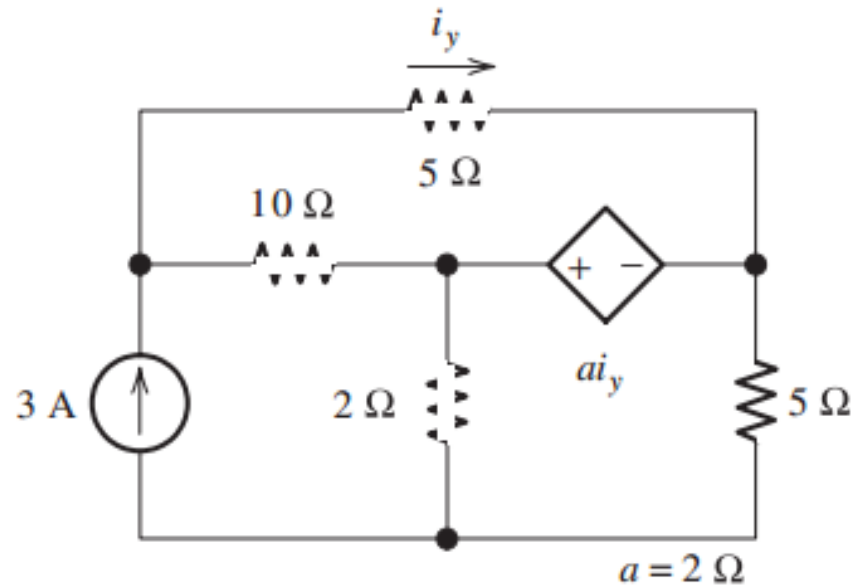


$$i_y = 2.31 \text{ A}$$
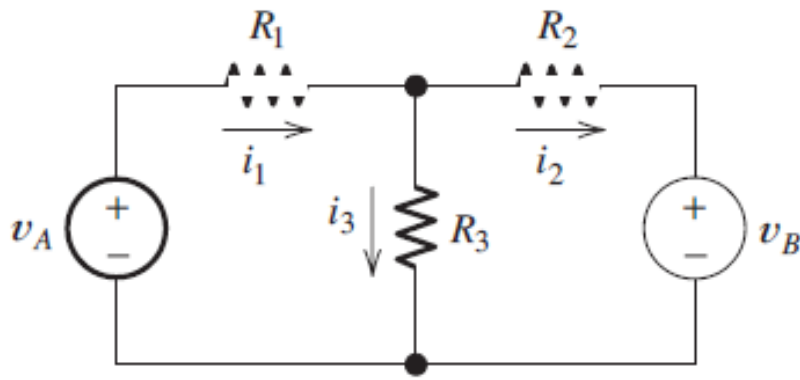
## 2.5 MESH-CURRENT ANALYSIS

- For solving currents
  - ❖ Branch currents
  - ❖ Mesh currents



(a) Circuit with branch currents

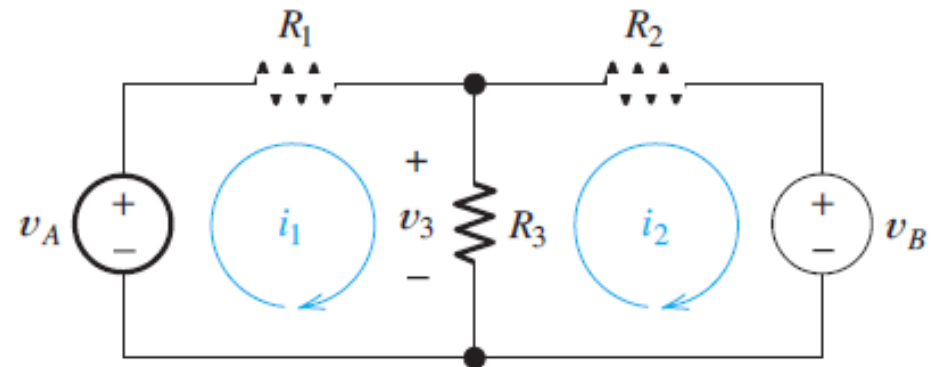

(b) Circuit with mesh currents


## 2.5 MESH-CURRENT ANALYSIS

- Normal KVL-KCL:

$$R_1 i_1 + R_3 i_3 = v_A$$

$$-R_3 i_3 + R_2 i_2 = -v_B$$

$$i_1 = i_2 + i_3$$

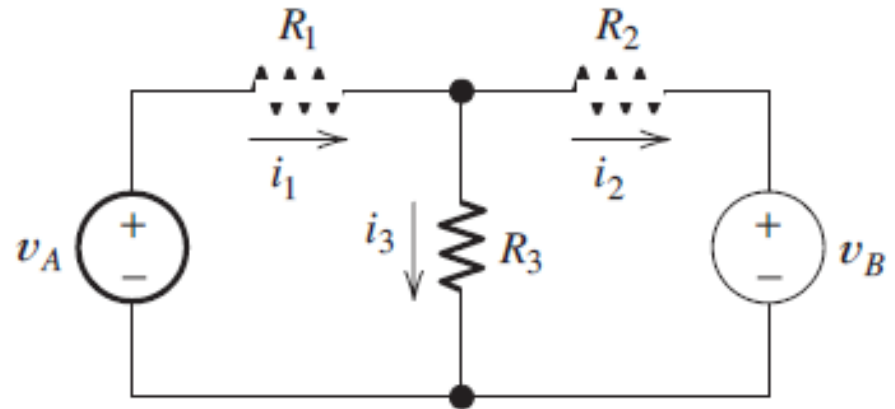


$$\Rightarrow R_1 i_1 + R_3(i_1 - i_2) = v_A$$

$$-R_3(i_1 - i_2) + R_2 i_2 = -v_B$$



## 2.5 MESH-CURRENT ANALYSIS

□ Mesh-Current Method:


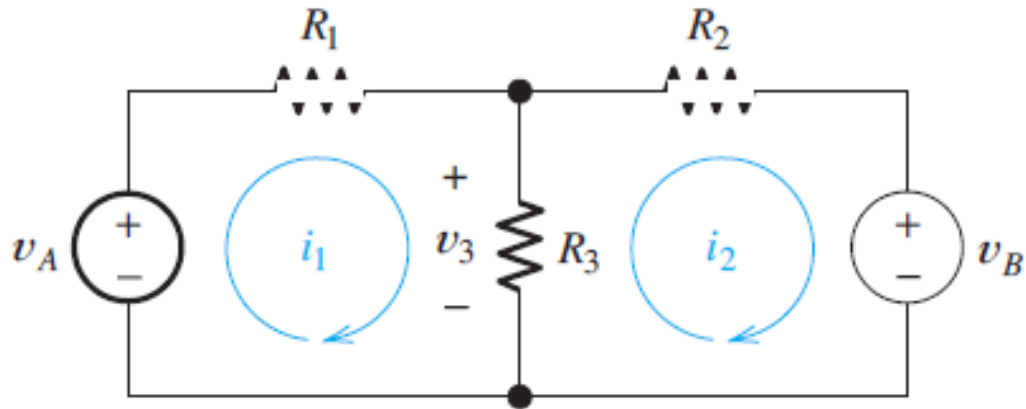


$$R_1 i_1 + R_3(i_1 - i_2) = v_A$$

$$-R_3(i_1 - i_2) + R_2 i_2 = -v_B$$

## 2.5 MESH-CURRENT ANALYSIS

### □ Example

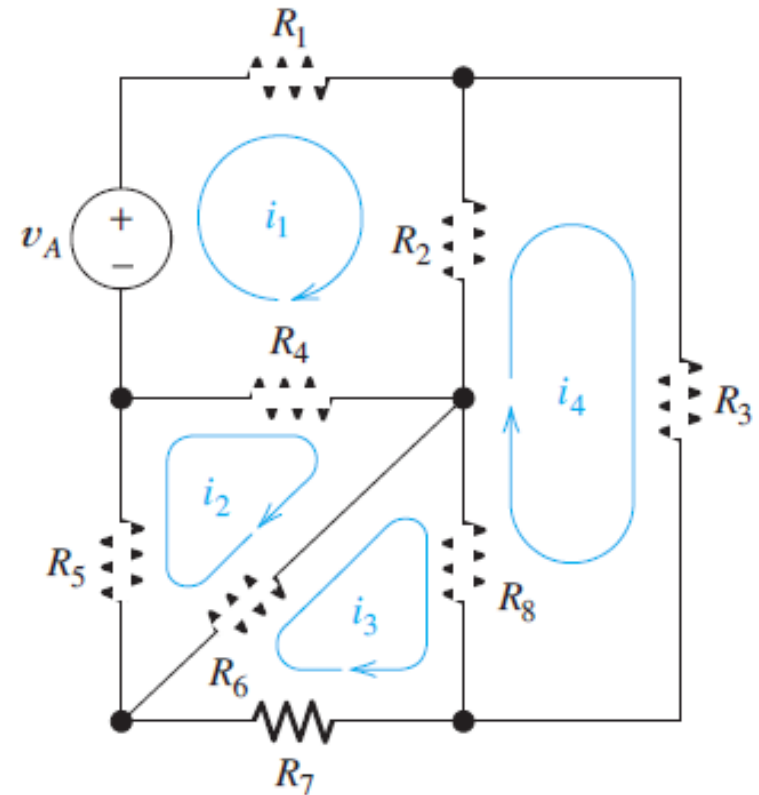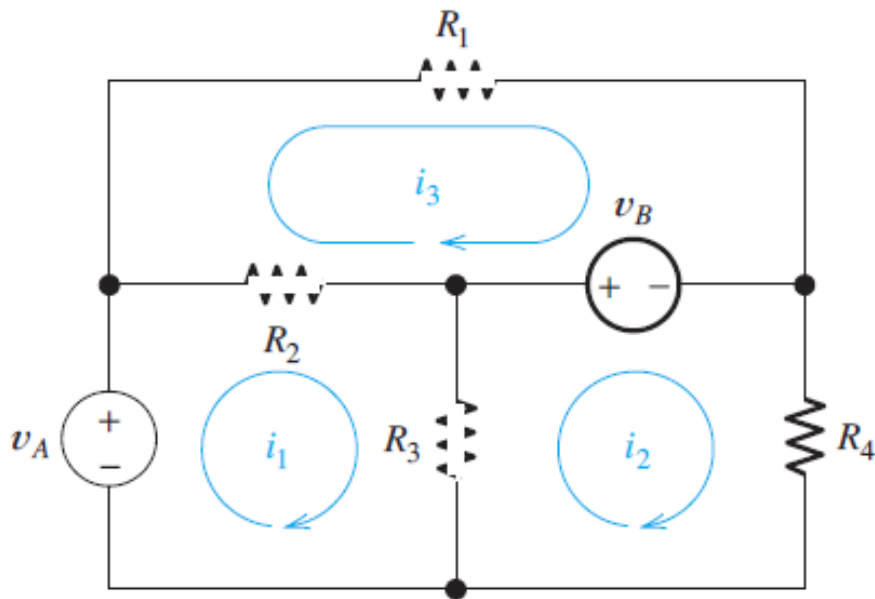


## 2.5 MESH-CURRENT ANALYSIS

### Example 2.12 Mesh-Current Analysis

$$R_2(i_1 - i_3) + R_3(i_1 - i_2) - v_A = 0$$

$$R_3(i_2 - i_1) + R_4i_2 + v_B = 0$$

$$R_2(i_3 - i_1) + R_1i_3 - v_B = 0$$

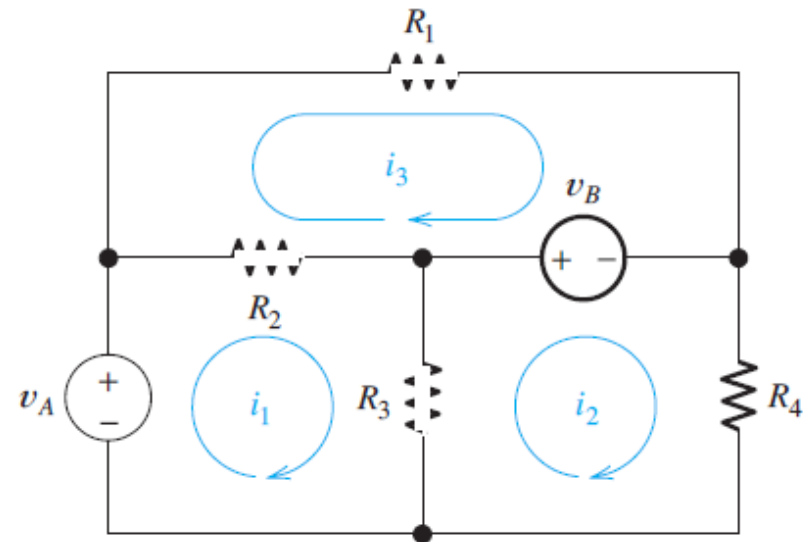

$$\Rightarrow \begin{bmatrix} (R_2 + R_3) & -R_3 & -R_2 \\ -R_3 & (R_3 + R_4) & 0 \\ -R_2 & 0 & (R_1 + R_2) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_A \\ -v_B \\ v_B \end{bmatrix}$$

## 2.5 MESH-CURRENT ANALYSIS


### □ Exercise

$$R_1 i_1 + R_2(i_1 - i_4) + R_4(i_1 - i_2) - v_A = 0$$

$$R_5 i_2 + R_4(i_2 - i_1) + R_6(i_2 - i_3) = 0$$

$$R_7 i_3 + R_6(i_3 - i_2) + R_8(i_3 - i_4) = 0$$
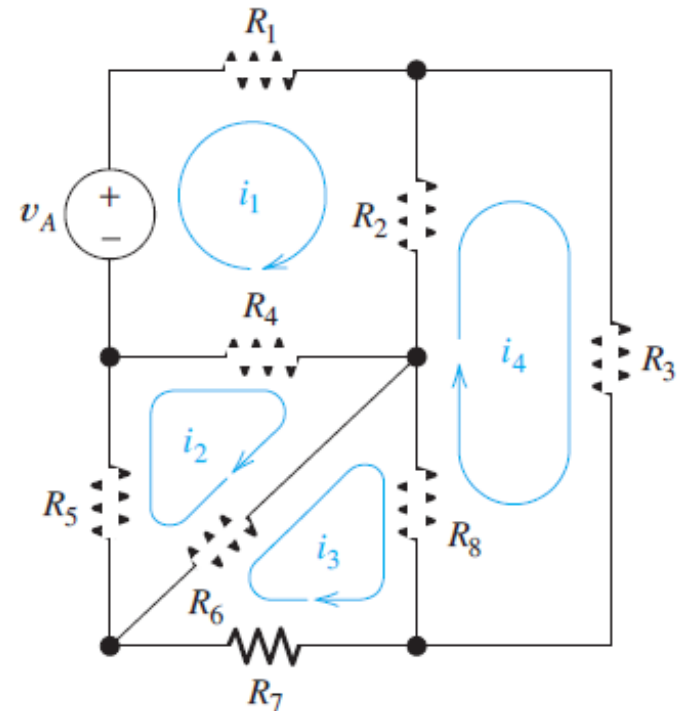
$$R_3 i_4 + R_2(i_4 - i_1) + R_8(i_4 - i_3) = 0$$



## 2.5 MESH-CURRENT ANALYSIS


### Example 2.13 Mesh-Current Analysis

$$20(i_1 - i_3) + 10(i_1 - i_2) - 70 = 0$$

$$10(i_2 - i_1) + 12(i_2 - i_3) + 42 = 0$$

$$20(i_3 - i_1) + 14i_3 + 12(i_3 - i_2) = 0$$
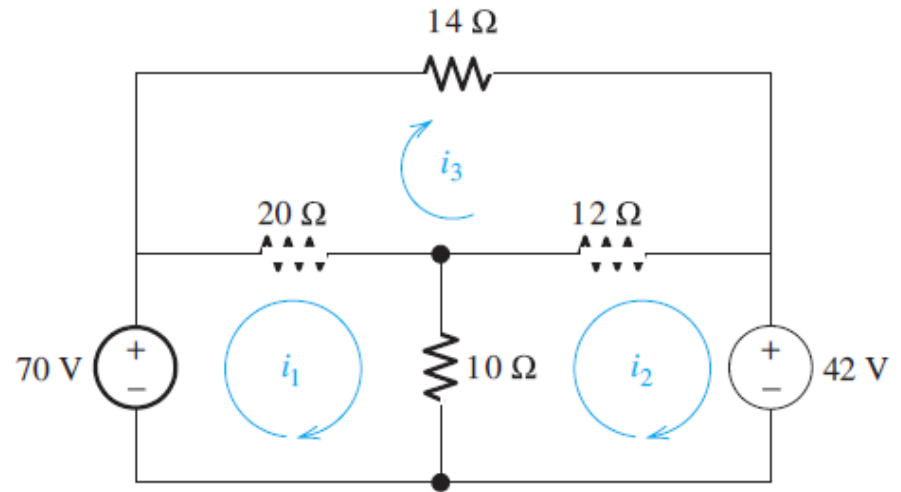
$$\begin{bmatrix} 30 & -10 & -20 \\ -10 & 22 & -12 \\ -20 & -12 & 46 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 70 \\ -42 \\ 0 \end{bmatrix}$$



```
>> R = [30 -10 -20; -10 22 -12; -20 -12 46];
```

```
>> V = [70; -42; 0];
```

```
>> I = R\V % Try to avoid using i, which represents the square root of
```

```
>> % -1 in MATLAB.
```

```
I =
```

```
4.0000
```

```
1.0000
```


```
2.0000
```



## 2.5 MESH-CURRENT ANALYSIS

### □ Exercise

- ❖ Current flowing through the 10 ohm

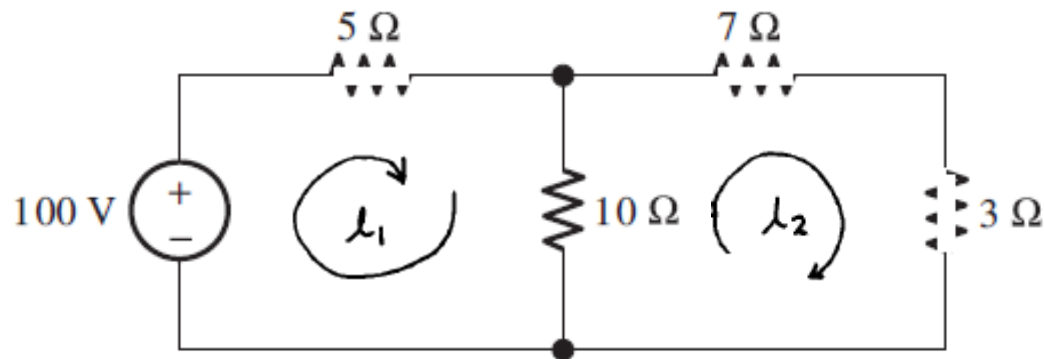


$$5i_1 + 10(i_1 - i_2) = 100 \quad \text{and} \quad 10(i_2 - i_1) + 7i_2 + 3i_2 = 0$$

$$\Rightarrow i_1 - i_2 = 5 \text{ A.}$$
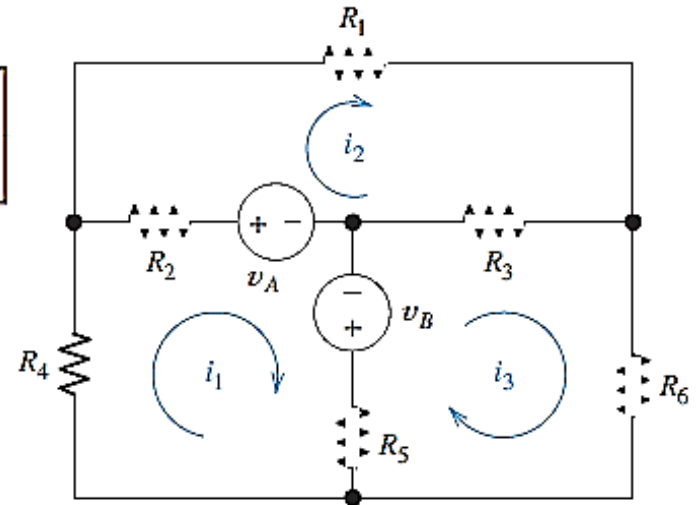
## 2.5 MESH-CURRENT ANALYSIS

□ A Shortcut to Writing the Matrix Equations:  $\mathbf{R} \cdot \mathbf{I} = \mathbf{V}$


$$\begin{bmatrix} (R_2 + R_4 + R_5) & -R_2 & -R_5 \\ -R_2 & (R_1 + R_2 + R_3) & -R_3 \\ -R_5 & -R_3 & (R_3 + R_5 + R_6) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} -v_A + v_B \\ v_A \\ -v_B \end{bmatrix}$$



- ❖ Diagonal elements: sum of the resistances in mesh
- ❖ Off-diagonal terms: negative of the resistance shared between mesh  $j$  and  $k$
- ❖ Terms in  $\mathbf{V}$  matrix: mesh voltage sources (+ or -)

## 2.5 MESH-CURRENT ANALYSIS

### □ Exercise

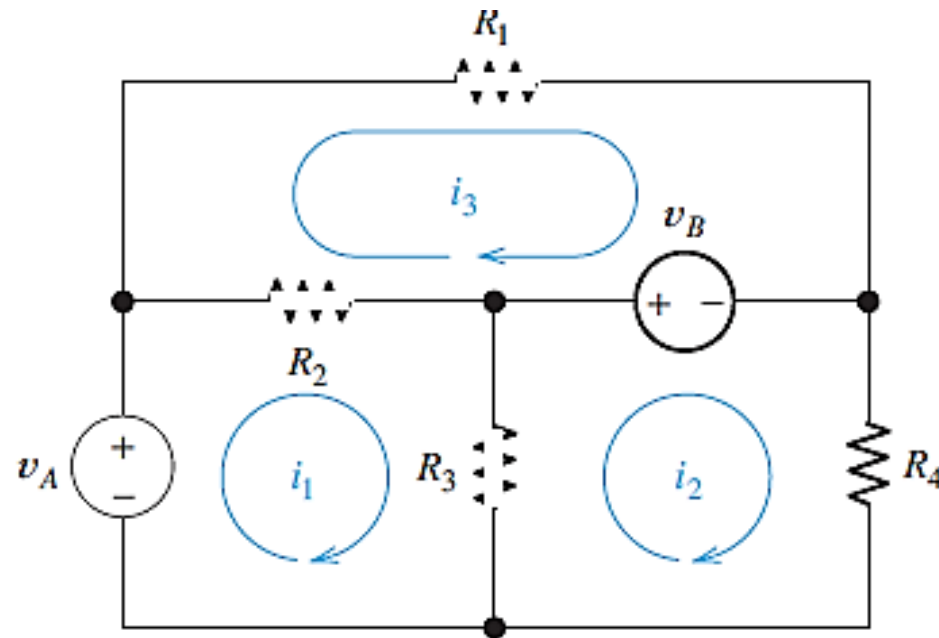


$$\begin{bmatrix} (R_2 + R_3) & -R_3 & -R_2 \\ -R_3 & (R_3 + R_4) & 0 \\ -R_2 & 0 & (R_1 + R_2) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} v_A \\ -v_B \\ v_B \end{bmatrix}$$



## 2.5 MESH-CURRENT ANALYSIS
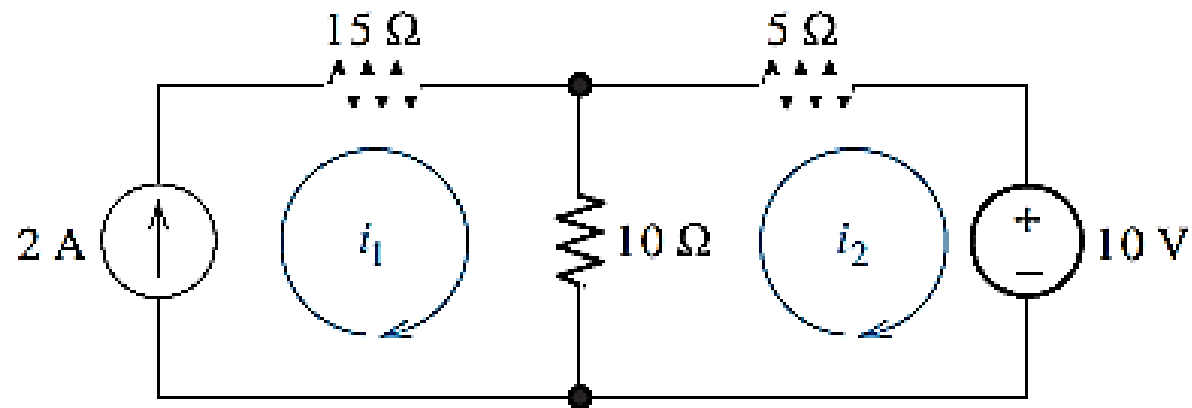
### □ Mesh Currents in Circuits Containing Current Sources



$$i_1 = 2 \text{ A}$$

$$10(i_2 - i_1) + 5i_2 + 10 = 0$$

## 2.5 MESH-CURRENT ANALYSIS


### □ Supermesh

- ❖ Write a KVL equation around the periphery of meshes 1 and 2 combined

$$i_1 + 2(i_1 - i_3) + 4(i_2 - i_3) + 10 = 0$$

$$3i_3 + 4(i_3 - i_2) + 2(i_3 - i_1) = 0$$

$$i_2 - i_1 = 5$$

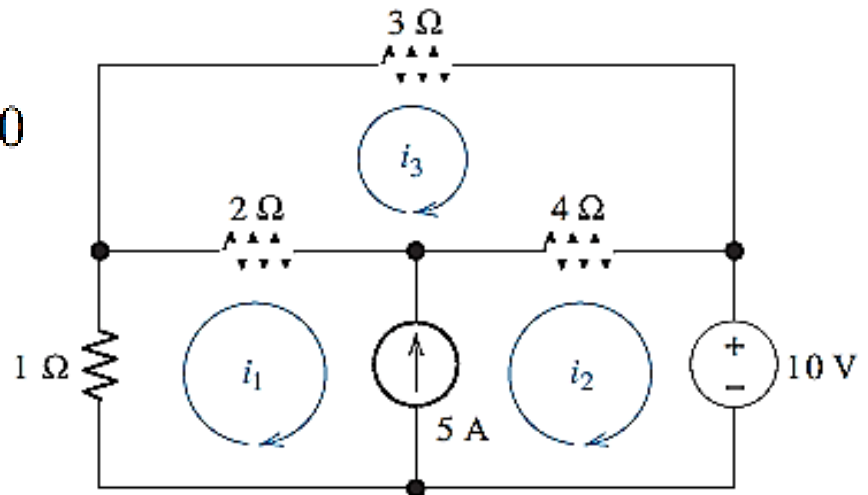


## 2.5 MESH-CURRENT ANALYSIS

### □ Exercise


$$i_1 = -5 \text{ A}$$

$$10(i_2 - i_1) + 5i_2 - 100 = 0$$

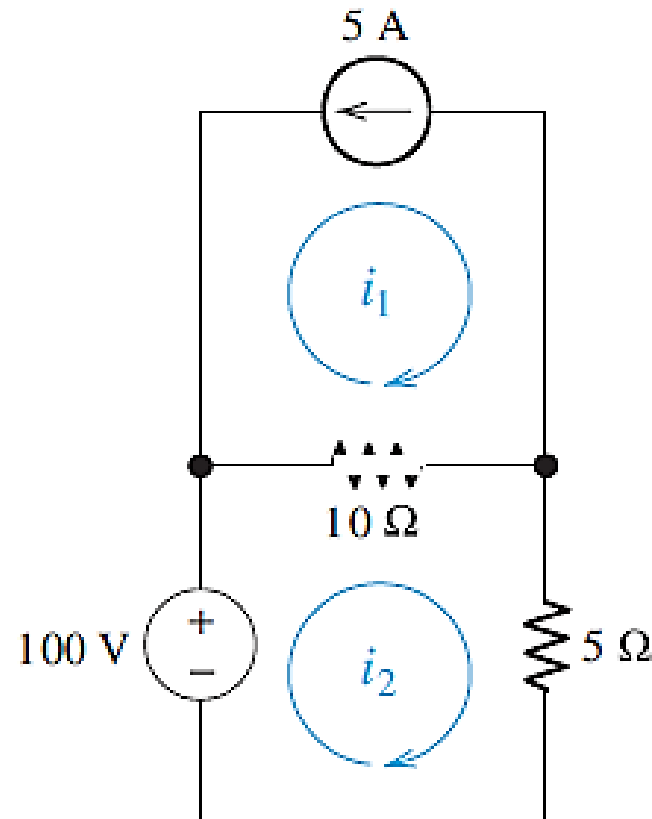

## 2.5 MESH-CURRENT ANALYSIS

### □ Exercise

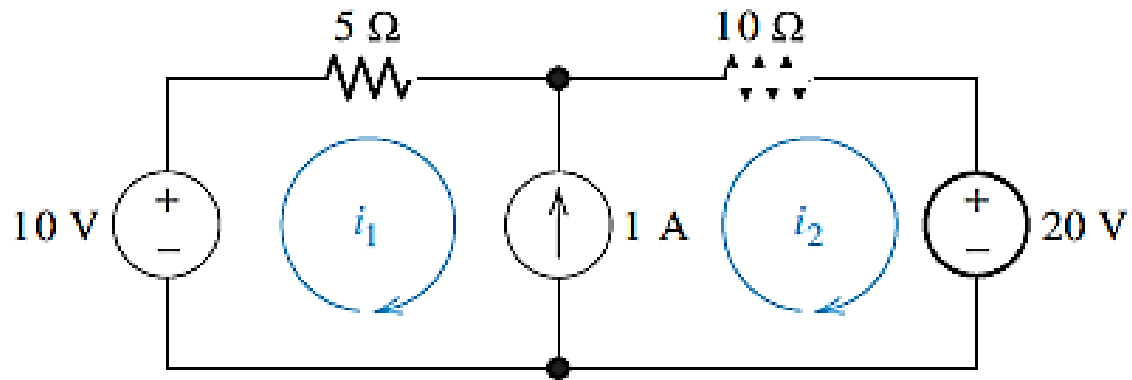

$$5i_1 + 10i_2 + 20 - 10 = 0.$$

$$i_2 - i_1 = 1$$

## 2.5 MESH-CURRENT ANALYSIS


### □ Circuits with Controlled Sources

#### Example 2.15 Mesh-Current Analysis with Controlled Sources

$$-20 + 4i_1 + 6i_2 + 2i_2 = 0$$

$$av_x = 0.25v_x = i_2 - i_1$$

$$v_x = 2i_2$$

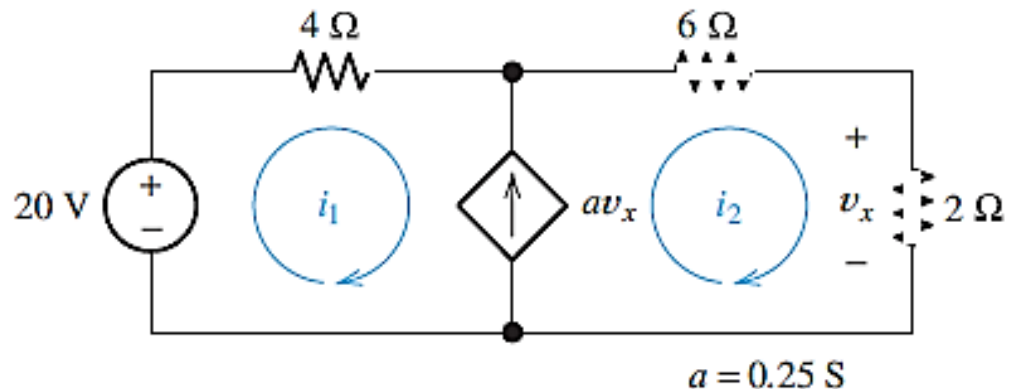


$$\rightarrow \frac{i_2}{2} = i_2 - i_1$$

$$\rightarrow \begin{aligned} 4i_1 + 8i_2 &= 20 \\ i_1 - \frac{i_2}{2} &= 0 \end{aligned}$$

$$\rightarrow \begin{aligned} i_1 &= 1 \text{ A} \\ i_2 &= 2 \text{ A} \end{aligned}$$
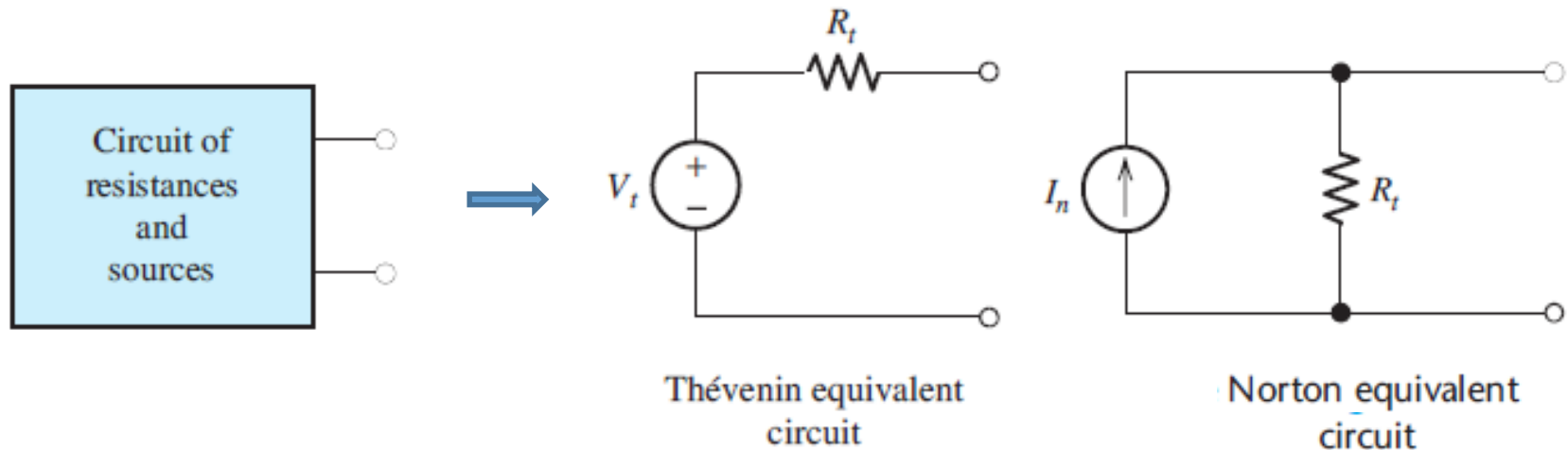
## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

- Replace two-terminal circuits containing resistances and sources




## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

### □ Thévenin Equivalent Circuits


#### ❖ Open circuit

$$V_t = v_{oc}$$

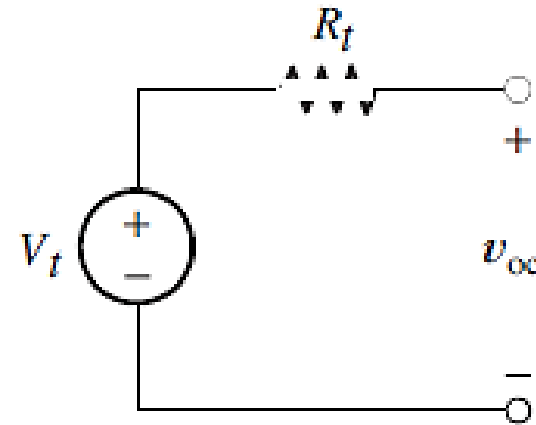

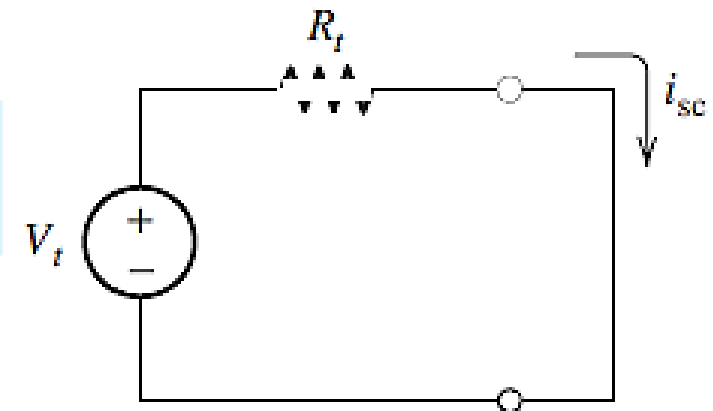
#### ❖ Short circuit

$$i_{sc} = \frac{V_t}{R_t} \quad \Rightarrow \quad R_t = \frac{V_t}{i_{sc}} \quad \Rightarrow \quad R_t = \frac{v_{oc}}{i_{sc}}$$




## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
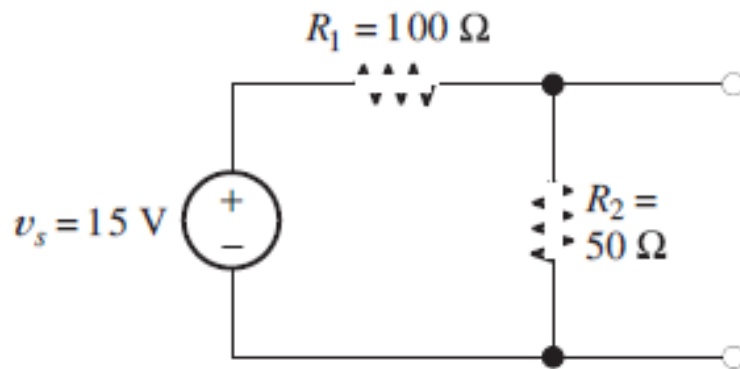
### Example 2.16 Determining the Thévenin Equivalent Circuit



(a) Original circuit

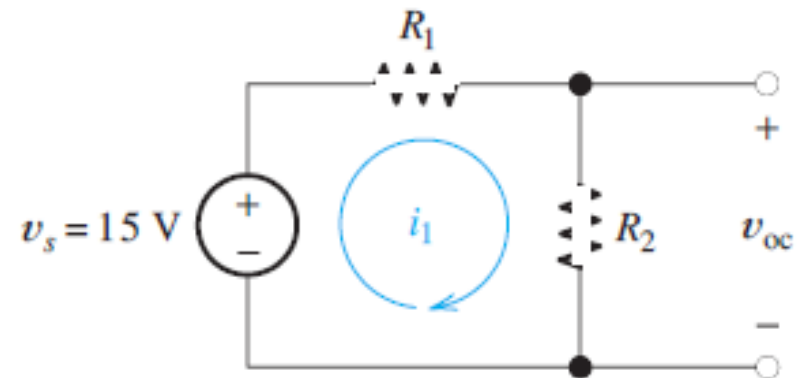

(b) Analysis with an open circuit


$$i_1 = \frac{v_s}{R_1 + R_2} = \frac{15}{100 + 50} = 0.10\text{ A}$$

$$v_{oc} = R_2 i_1 = 50 \times 0.10 = 5\text{ V}$$




## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
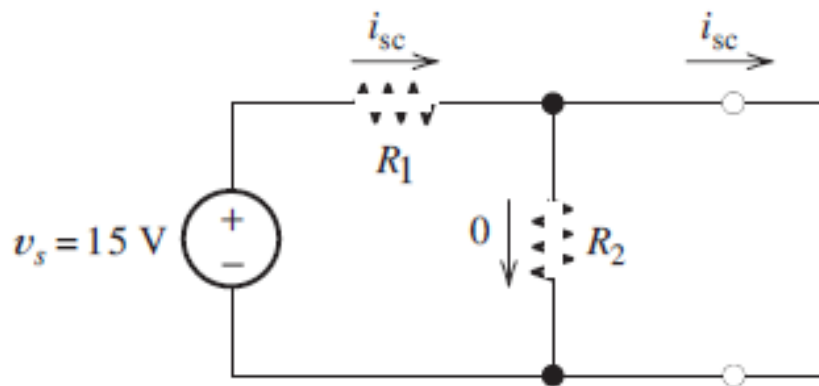
### Example 2.16 Determining the Thévenin Equivalent Circuit



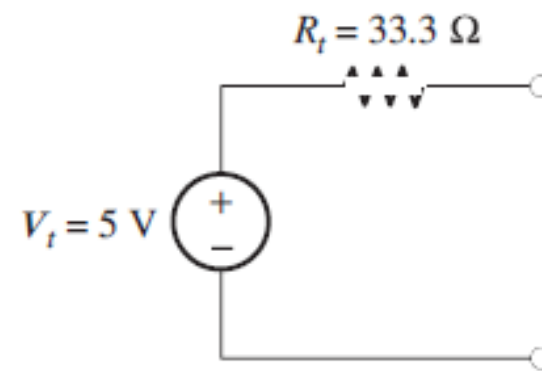(c) Analysis with a short circuit

$$i_{sc} = \frac{v_s}{R_1} = \frac{15}{100} = 0.15\text{ A}$$




(d) Thévenin equivalent

$$R_t = \frac{v_{oc}}{i_{sc}} = \frac{5\text{ V}}{0.15\text{ A}} = 33.3\ \Omega$$

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

### □ Exercise

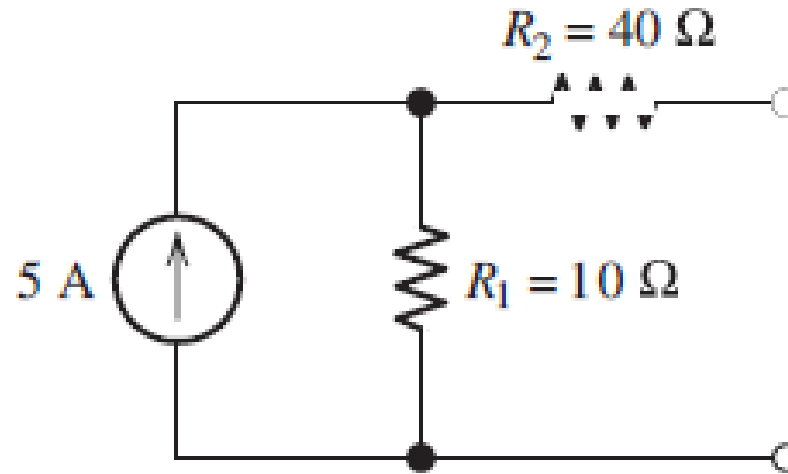


$$V_t = 50\ \text{V}, R_t = 50\ \Omega.$$

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

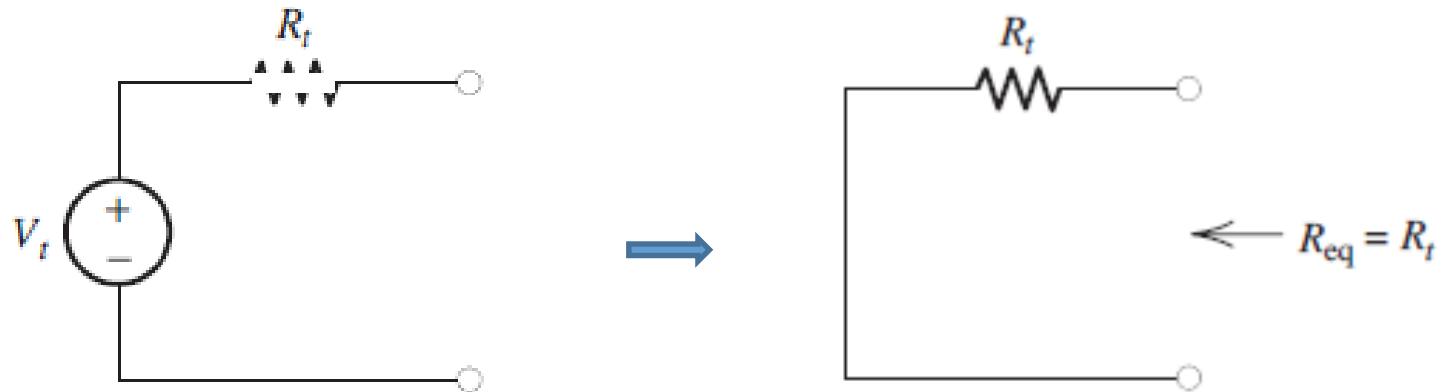
### □ Finding the Thévenin Resistance Directly

- ❖ If network contains no dependent sources
- ❖ Zero the sources
  - ✓ Voltage source: Short circuit
  - ✓ Current source: Open circuit
- ❖ Find the Req




## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
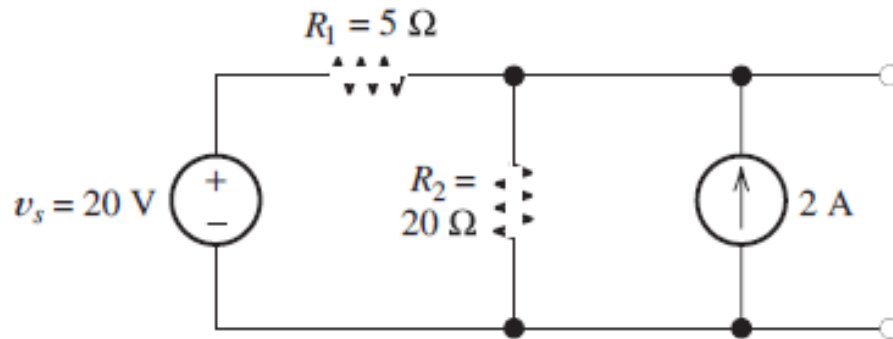
### Example 2.17 Zeroing Sources to Find Thévenin Resistance



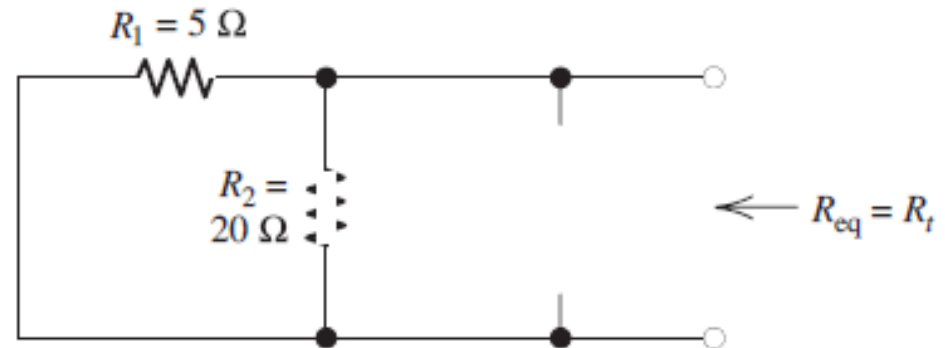(a) Original circuit


$$R_t = R_{eq} = \frac{1}{1/R_1 + 1/R_2} = \frac{1}{1/5 + 1/20} = 4 \Omega$$



(b) Circuit with sources zeroed

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
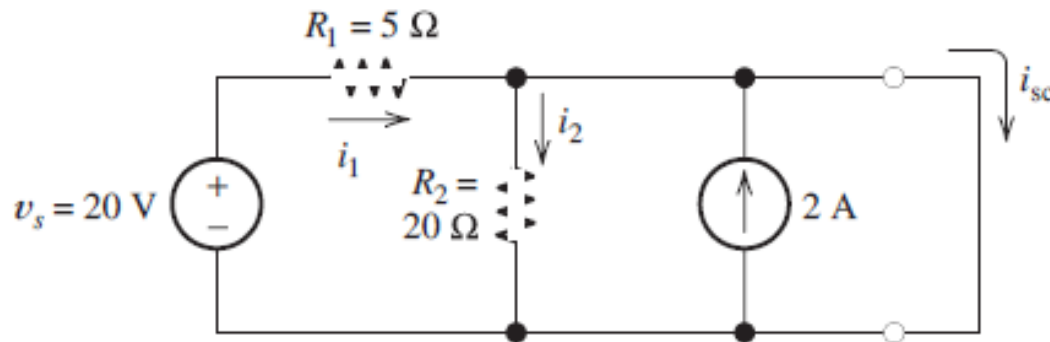
### Example 2.17 Zeroing Sources to Find Thévenin Resistance




(c) Circuit with a short circuit

$$i_2 = 0$$

$$i_1 = \frac{v_s}{R_1} = \frac{20}{5} = 4\text{ A}$$

$$i_1 + 2 = i_2 + i_{sc}$$

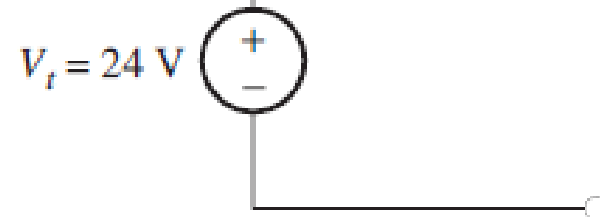
$$V_t = R_t i_{sc} = 4 \times 6 = 24\text{ V}$$




(d) Thévenin equivalent circuit

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

### □ Exercise

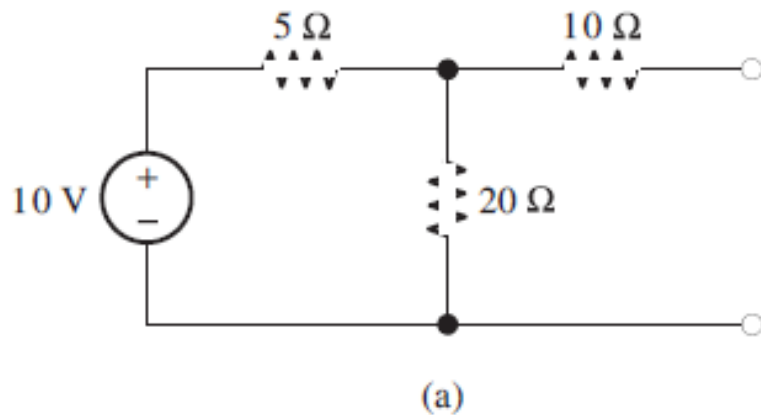


**a.  $R_t = 14 \Omega$ ;**

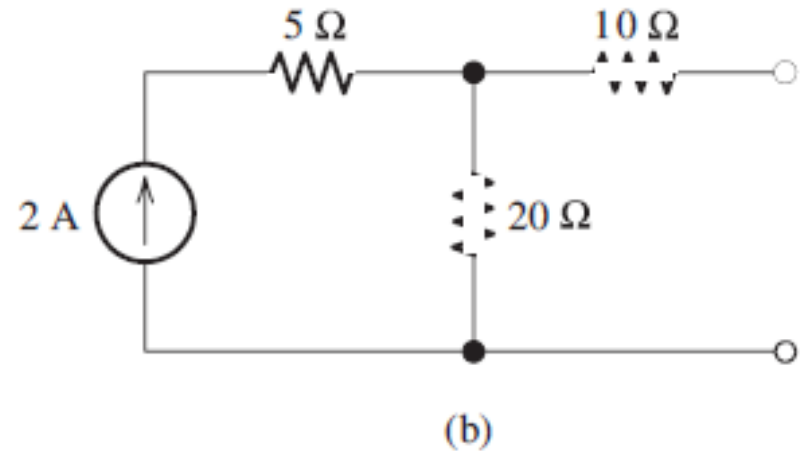

**b.  $R_t = 30 \Omega$ ;**

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS


### □ Exercise

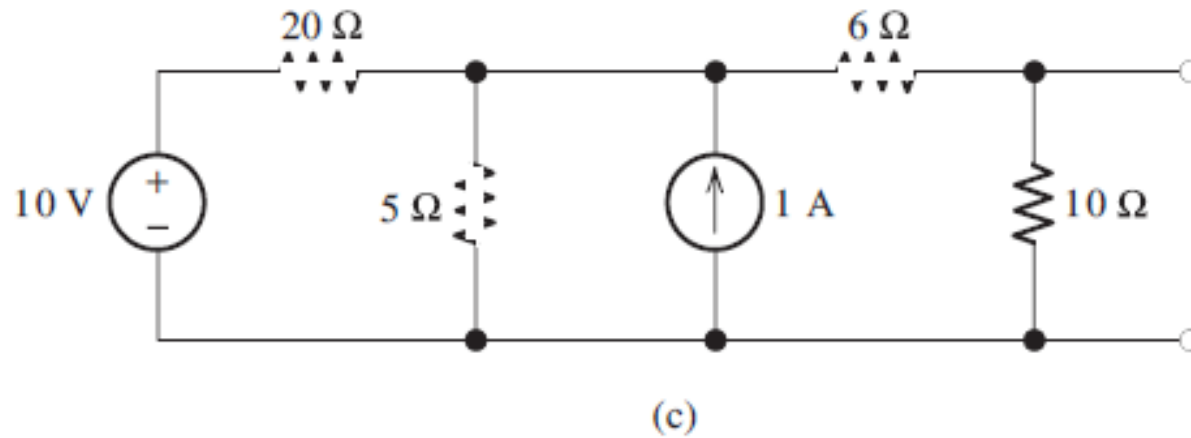


$$\mathbf{c. R_t = 5 \Omega}$$

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
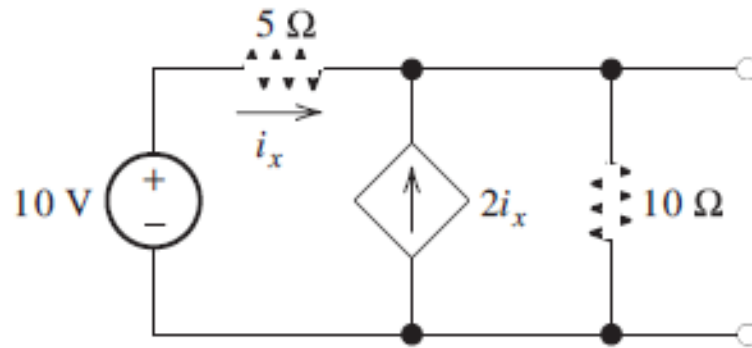
### Example 2.18 Thévenin Equivalent of a Circuit with a Dependent Source



(a) Original circuit

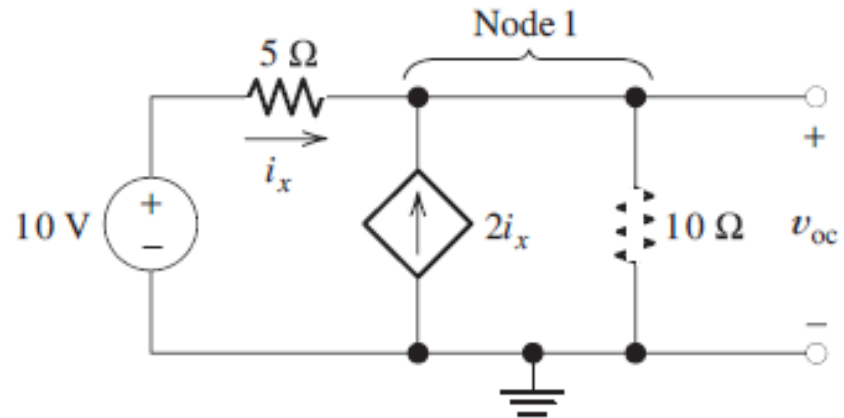

(b) Circuit with an open circuit


$$i_x + 2i_x = \frac{v_{oc}}{10} \quad i_x = \frac{10 - v_{oc}}{5}$$

$$\Rightarrow 3 \frac{10 - v_{oc}}{5} = \frac{v_{oc}}{10} \quad \Rightarrow v_{oc} = 8.57 \text{ V.}$$




## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
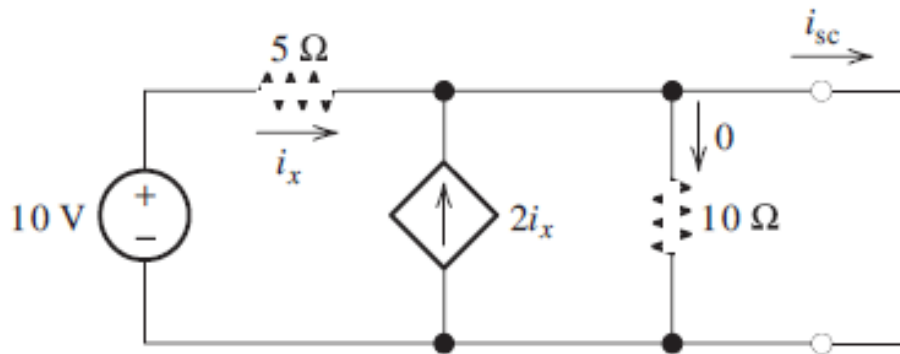
### Example 2.18 Thévenin Equivalent of a Circuit with a Dependent Source



(c) Circuit with a short circuit

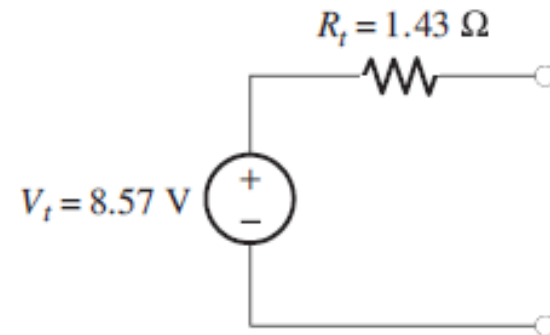

(d) Thévenin equivalent

$$i_x = \frac{10 \text{ V}}{5 \Omega} = 2 \text{ A}$$


$$i_{sc} = 3i_x = 6 \text{ A}$$

$$\Rightarrow R_t = \frac{v_{oc}}{i_{sc}} = \frac{8.57 \text{ V}}{6 \text{ A}} = 1.43 \Omega$$

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
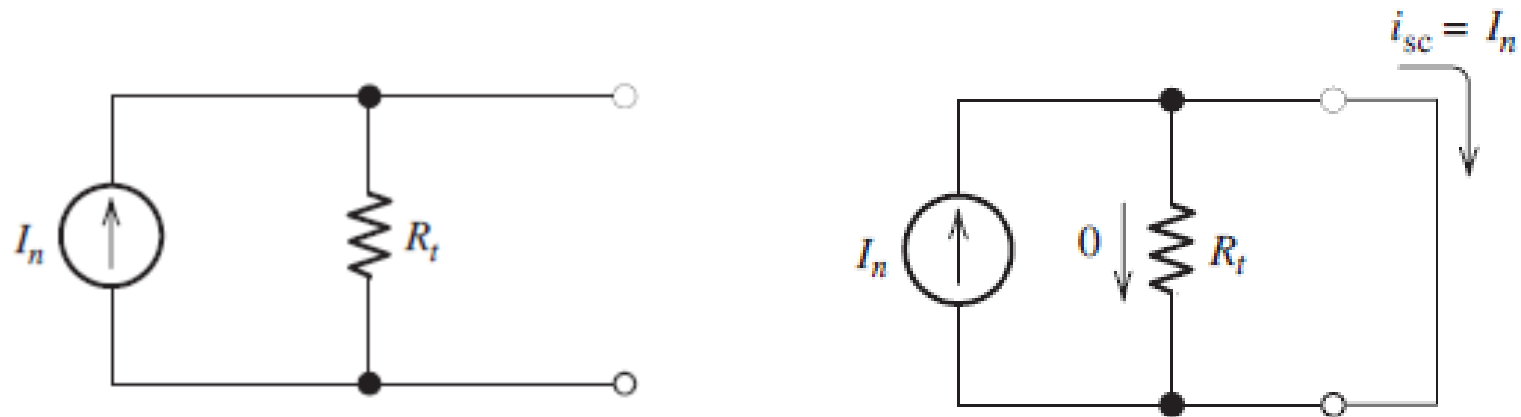
### □ Norton Equivalent Circuit

- ❖ Resistance in the Norton equivalent is the same as the Thévenin resistance



$$I_n = i_{sc}$$

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS


### □ Step-by-Step Thévenin/Norton-Equivalent-Circuit Analysis

- ❖ 1. Perform two of these:
  - ✓ a. Determine the open-circuit voltage  $V_t = V_{oc}$ .
  - ✓ b. Determine the short-circuit current  $I_n = I_{sc}$ .
  - ✓ c. Zero the independent sources and find the Thévenin resistance  $R_t$  looking back into the terminals. Do not zero dependent sources.
- ❖ 2. Use the equation  $V_t = R_t I_n$  to compute the remaining value.
- ❖ 3. The Thévenin equivalent consists of a voltage source  $V_t$  in series with  $R_t$
- ❖ 4. The Norton equivalent consists of a current source  $I_n$  in parallel with  $R_t$



## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
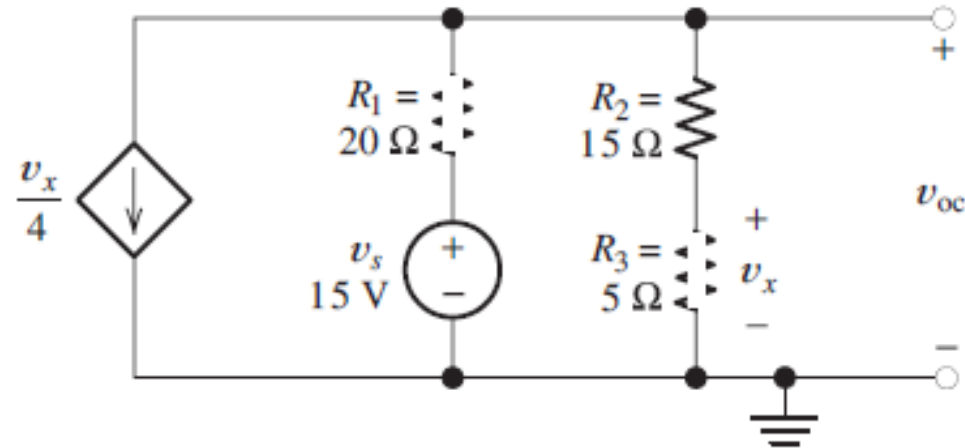
### Example 2.19 Norton Equivalent Circuit



(a) Original circuit under open-circuit conditions

$$\frac{v_x}{4} + \frac{v_{oc} - 15}{R_1} + \frac{v_{oc}}{R_2 + R_3} = 0$$


$$\Rightarrow \frac{0.25v_{oc}}{4} + \frac{v_{oc} - 15}{R_1} + \frac{v_{oc}}{R_2 + R_3} = 0$$

$$v_x = \frac{R_3}{R_2 + R_3} v_{oc} = 0.25v_{oc}$$

$$\Rightarrow v_{oc} = 4.62 \text{ V.}$$


## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
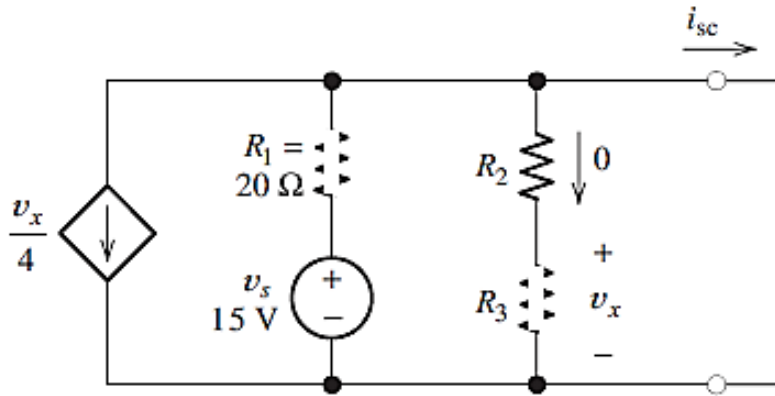
### Example 2.19 Norton Equivalent Circuit



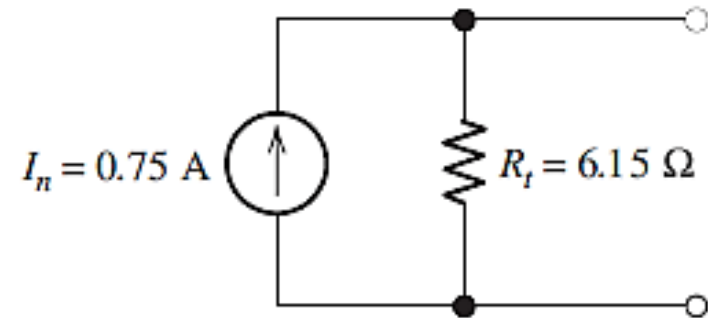(b) Circuit with a short circuit

$$i_{sc} = \frac{v_s}{R_1} = \frac{15\text{ V}}{20\ \Omega} = 0.75\text{ A}$$




(c) Norton equivalent circuit

$$R_t = \frac{v_{oc}}{i_{sc}} = \frac{4.62}{0.75} = 6.15\ \Omega$$


## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

### □ Exercise

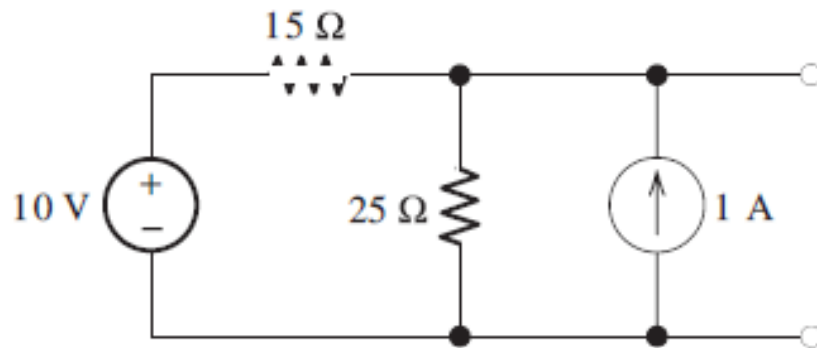

(a)
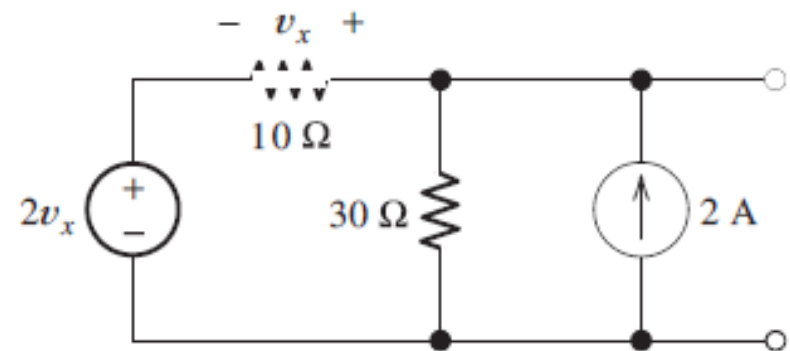
$$I_n = 1.67 \text{ A}, R_t = 9.375 \Omega$$




(b)

$$I_n = 2 \text{ A}, R_t = 15 \Omega$$

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

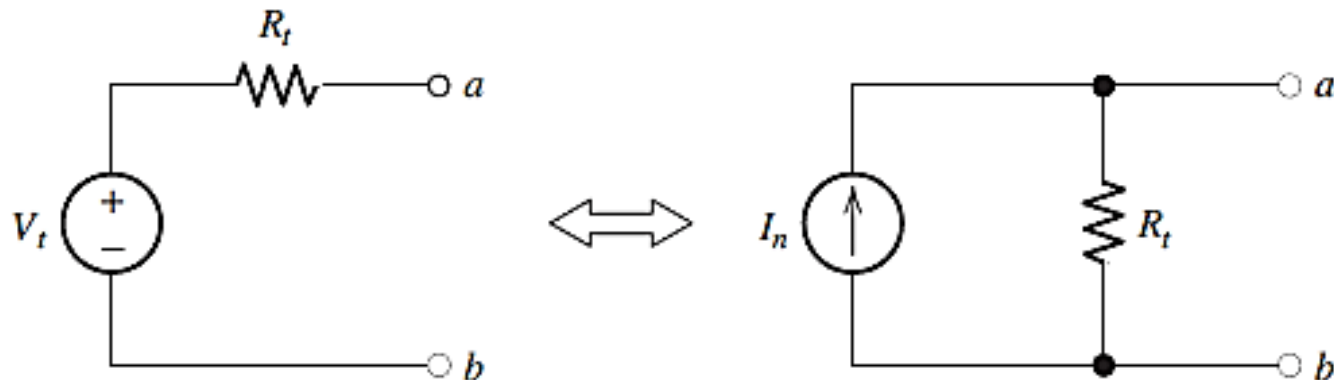
### □ Source Transformations

- ❖ Replace a voltage source in series with a resistance by a Norton equivalent circuit




## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
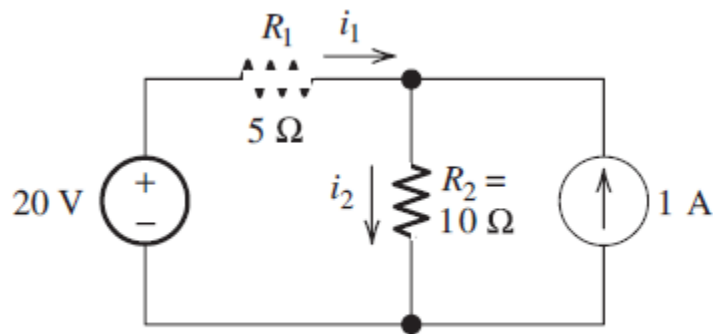
### Example 2.20 Using Source Transformations



(a) Original circuit

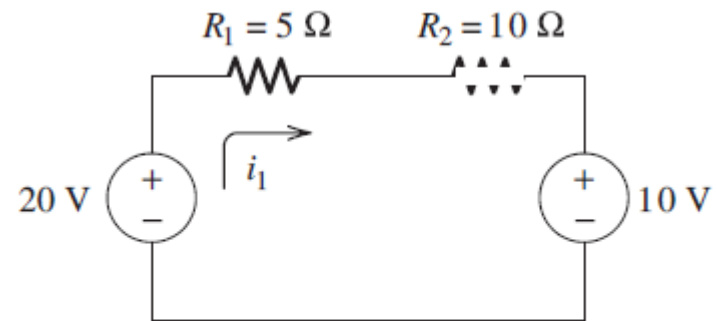

(b) Circuit after transforming the current source into a voltage source

$$R_1 i_1 + R_2 i_1 + 10 - 20 = 0$$


$$i_1 = \frac{10}{R_1 + R_2} = 0.667 \text{ A}$$

$$i_2 = i_1 + 1 = 1.667 \text{ A}$$




## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
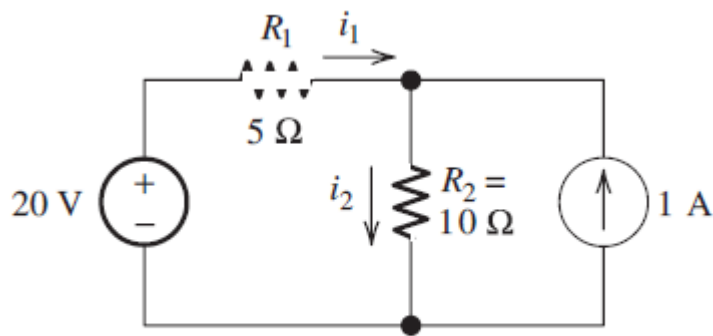
### Example 2.20 Using Source Transformations



(a) Original circuit

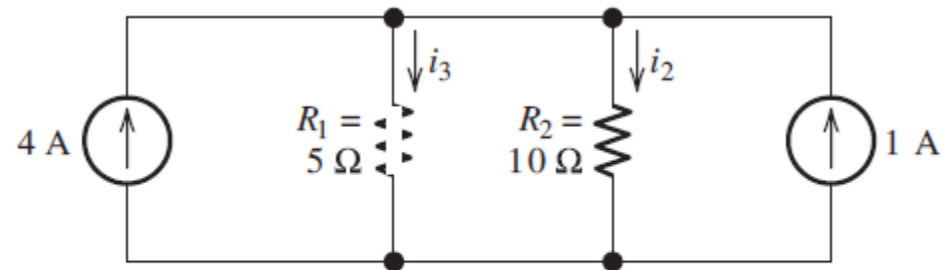


(c) Circuit after transforming the voltage source into a current source

$$i_2 = \frac{R_1}{R_1 + R_2} i_{\text{total}} = \frac{5}{5 + 10} (5) = 1.667 \text{ A}$$

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

### □ Exercise

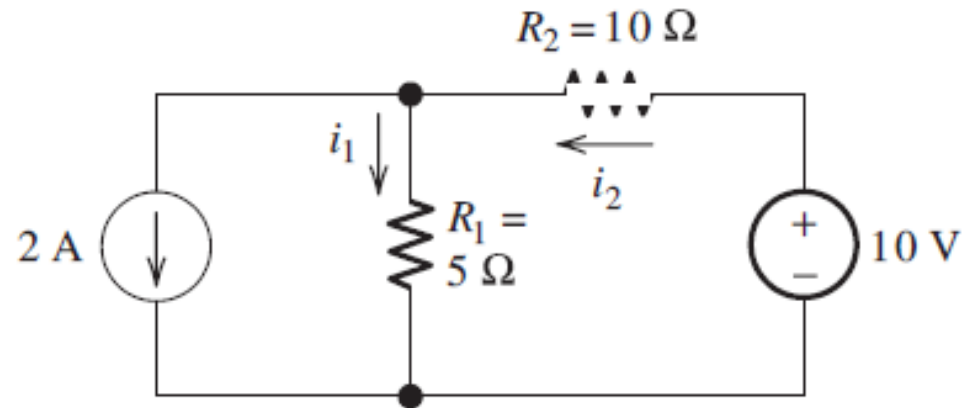


$$i_1 = -0.667 \text{ A}, i_2 = 1.333 \text{ A}.$$

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS
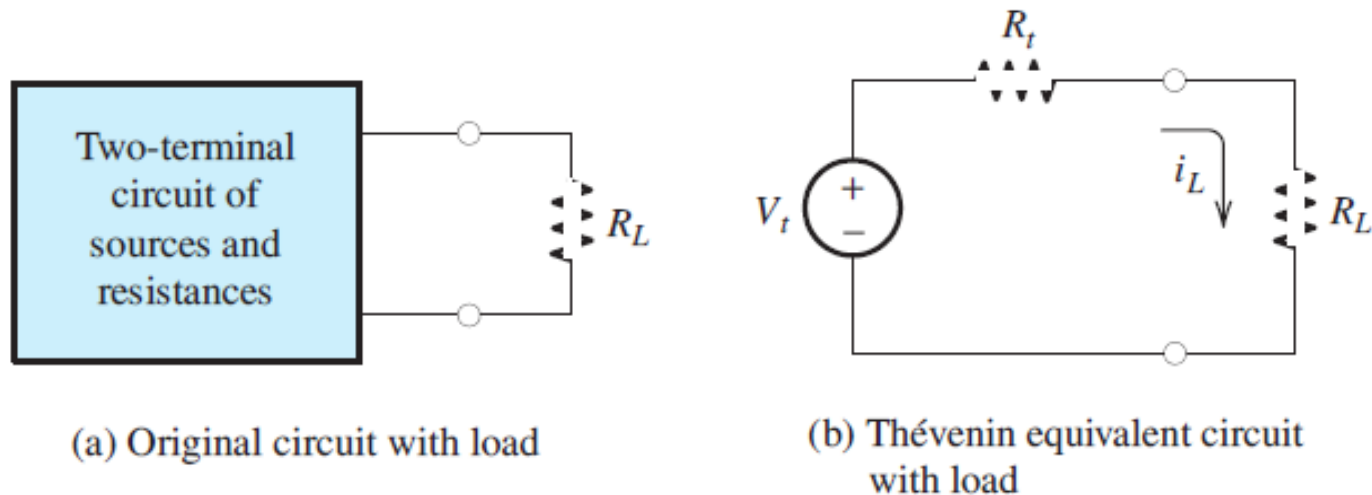
### □ Maximum Power Transfer

- ❖ When maximum possible power is delivered to the load?



## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS

### □ Maximum Power Transfer


$$i_L = \frac{V_t}{R_t + R_L}$$

$$P_L = i_L^2 R_L = \frac{V_t^2 R_L}{(R_t + R_L)^2}$$

$$\frac{dP_L}{dR_L} = \frac{V_t^2 (R_t + R_L)^2 - 2V_t^2 R_L (R_t + R_L)}{(R_t + R_L)^4} = 0$$

$$R_L = R_t$$

$$P_{L \max} = \frac{V_t^2}{4R_t}$$

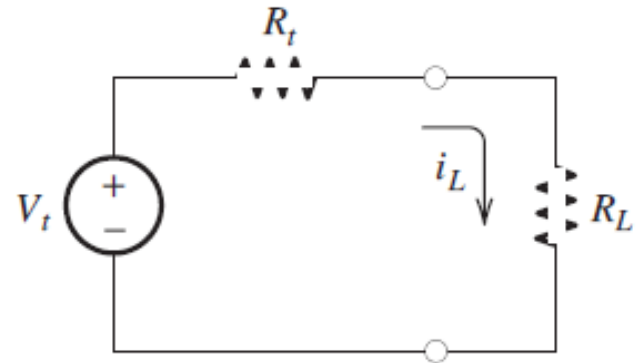

## 2.6 THÉVENIN AND NORTON EQUIVALENT CIRCUITS


### Example 2.21 Determining Maximum Power Transfer

$$R_t = \frac{1}{1/R_1 + 1/R_2} = \frac{1}{1/20 + 1/5} = 4 \Omega$$

$$V_t = v_{oc} = \frac{R_2}{R_1 + R_2}(50) = \frac{5}{5 + 20}(50) = 10 \text{ V}$$

$$R_L = R_t = 4 \Omega$$
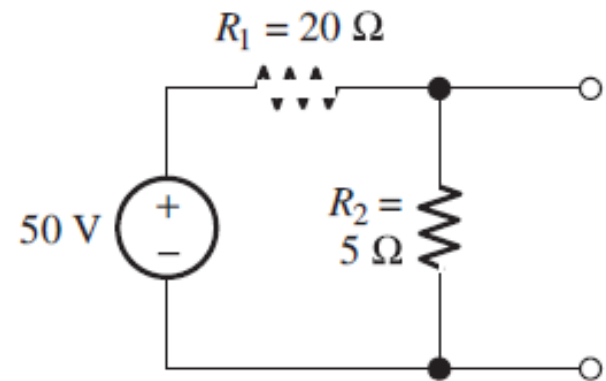
$$P_{L \max} = \frac{V_t^2}{4R_t} = \frac{10^2}{4 \times 4} = 6.25 \text{ W}$$



## 2.7 SUPERPOSITION PRINCIPLE

- For a circuit composed of:
  - ❖ Resistances
  - ❖ Linear dependent sources
  - ❖  $n$  independent sources


- Total response:

$$r_T = r_1 + r_2 + \cdots + r_n$$



## 2.7 SUPERPOSITION PRINCIPLE

□ Example:

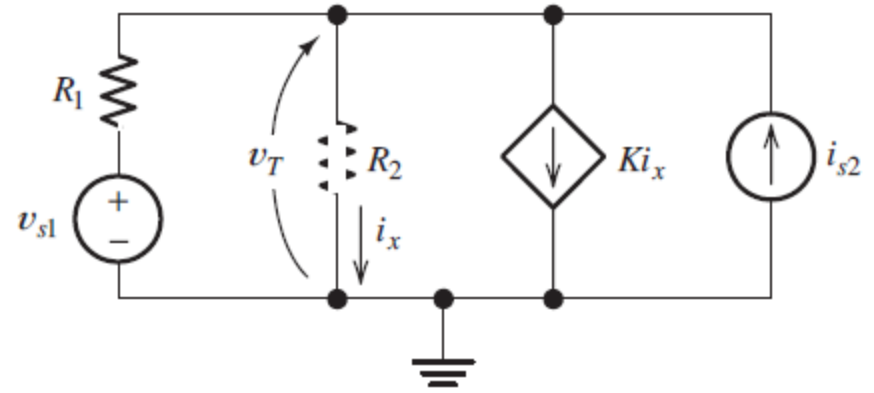

$$\frac{v_T - v_{s1}}{R_1} + \frac{v_T}{R_2} + K i_x = i_{s2}$$

$$i_x = \frac{v_T}{R_2}$$

$$\Rightarrow v_T = \frac{R_2}{R_1 + R_2 + K R_1} v_{s1} + \frac{R_1 R_2}{R_1 + R_2 + K R_1} i_{s2}$$



$$v_1 = \frac{R_2}{R_1 + R_2 + K R_1} v_{s1}$$

$$v_2 = \frac{R_1 R_2}{R_1 + R_2 + K R_1} i_{s2}$$

$$\Rightarrow v_T = v_1 + v_2$$

## 2.7 SUPERPOSITION PRINCIPLE
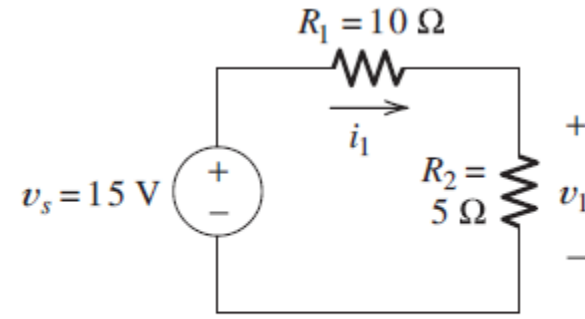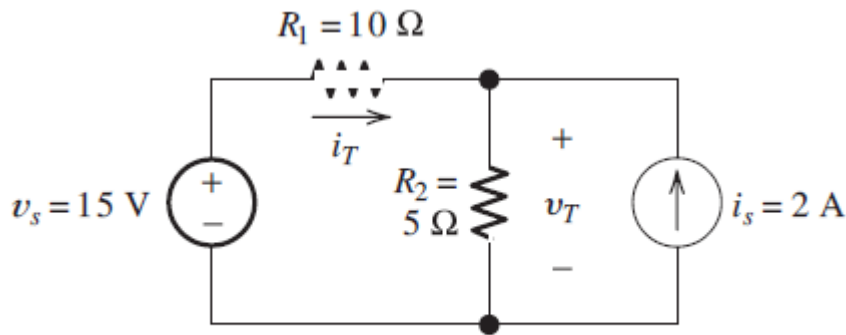
### Example 2.22 Circuit Analysis Using Superposition




$$v_1 = \frac{R_2}{R_1 + R_2} v_s = \frac{5}{5 + 10} (15) = 5 \text{ V}$$




## 2.7 SUPERPOSITION PRINCIPLE
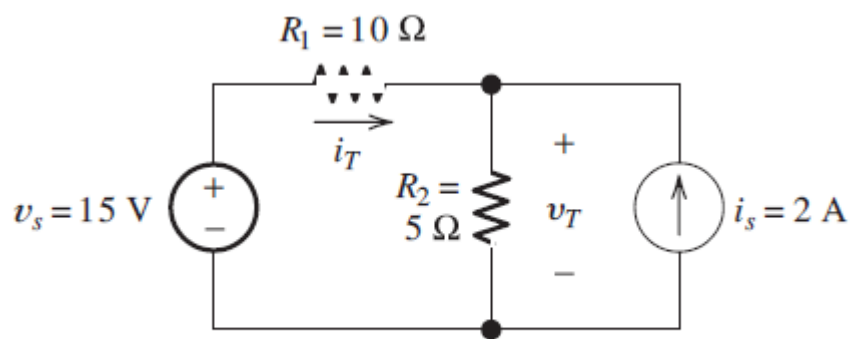
## Example 2.22 Circuit Analysis Using Superposition



(a) Original circuit

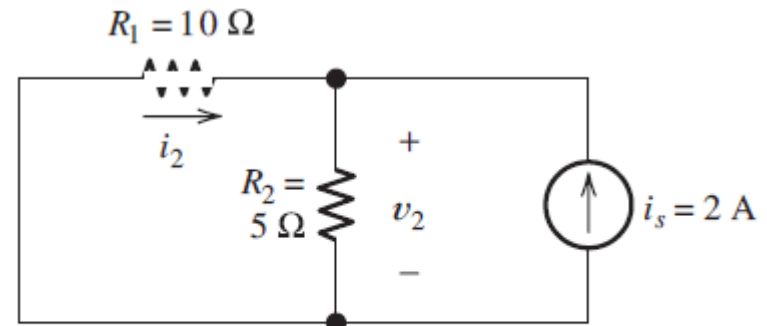

(c) Circuit with only the current source active


$$R_{eq} = \frac{1}{1/R_1 + 1/R_2} = \frac{1}{1/10 + 1/5} = 3.33 \Omega$$

$$v_2 = i_s R_{eq} = 2 \times 3.33 = 6.66 \text{ V}$$

$$\Rightarrow v_T = v_1 + v_2 = 5 + 6.66 = 11.66$$

## 2.7 SUPERPOSITION PRINCIPLE

### □ Exercise

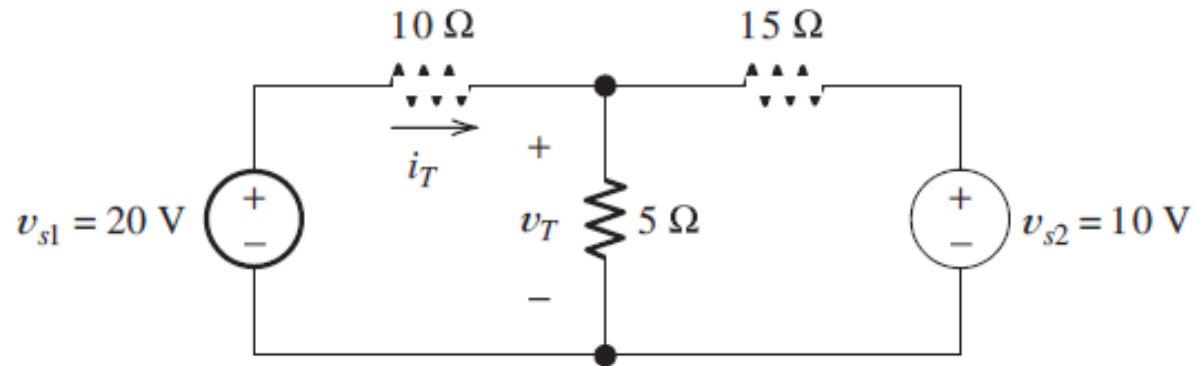


$$v_1 = 5.45 \text{ V}, v_2 = 1.82 \text{ V}, v_T = 7.27 \text{ V},$$

$$i_1 = 1.45 \text{ A}, i_2 = -0.181 \text{ A}, i_T = 1.27 \text{ A}.$$
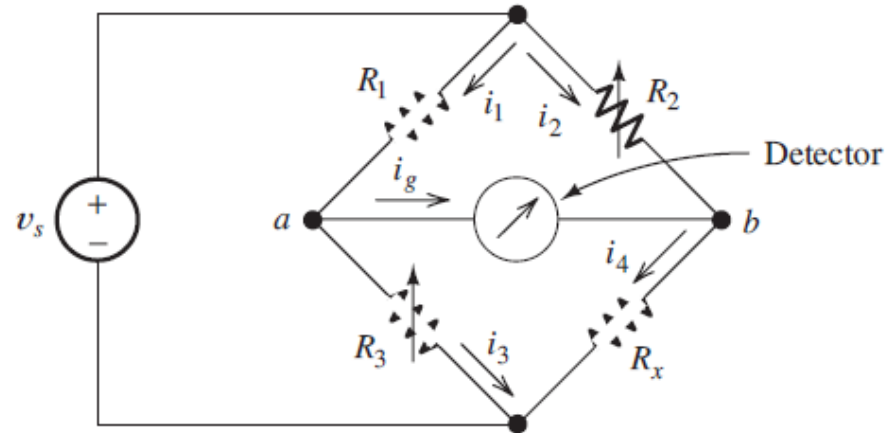
## 2.8 WHEATSTONE BRIDGE

- A circuit used to measure unknown resistances



- ❖ When detector indicates zero current: bridge is **balanced**

$$\frac{R_3}{R_1} = \frac{R_x}{R_2}$$

## EXERCISES

- P2.1
- P2.3
- P2.24
- P2.25
- P2.34
- P2.35
- P2.56
- P2.57
- P2.65
- P2.66
- P2.80
- P2.91
- P2.94
- P2.103
- T2.4
- T2.5
- T2.6

